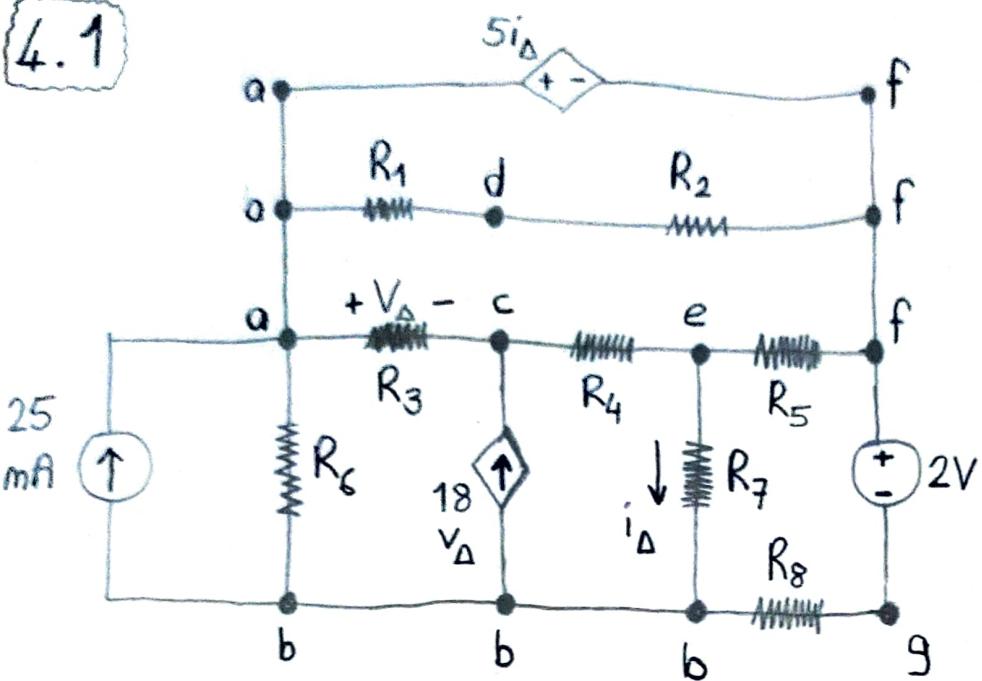




GEEK DAY

4.1



- a)  $\overset{(2)}{a \ominus b}, a-f, a-d, a-f, d-f, a-c, c-e, e-f, f-g, b-g, e-b \Rightarrow 12$  branches
- b) All above except one of the  $a-b$  branches which a path with 25mA curr.  
So there are 11 branches with unknown current.
- c)  $\overset{(2)}{a \ominus b}, a-c, c-e, e-f, c-b, e-b, \overset{(2)}{a \ominus f}, b-f$   
 $\rightarrow$  10 essential branches
- d) Branches above except  $a-b$  branch with 25mA current source. 9 total.
- e)  $a, b, c, d, e, f, g = 7$  nodes
- f)  $a, b, c, e, f = 5$  essential nodes
- g)  $(a-b), (a-b-c), (c-b-e), (e-b-g-f), (a-c-f-d), (a-d-f) = 6$  meshes


4.2

- a) Essential nodes are important to show current changes on branches but writing equations with essential branches is the deciding one on number of equations. Because unknown current number on a circuit is equal to number of essential branches with unknown current. So we need at least 9 equations since there are 9 essential branch with unknown current on this circuit.
- b) a,b,c,e,f nodes are essential ones. We can use them to derive equations using KCL (Kirchhof's Current Law). The equations we will derive from a and b won't make difference since the current going through them are equal. So we can say 4 equations needed
- c)  $\downarrow$   
 $E - (N - 1)$ , this equation shows how many equations can be derived by using KVL (Kirchhof's Voltage Law). E is equal to number of essential branches and N is equal to essential nodes.  
Since we say "must be derived" we can ignore essential branch with known current. So  $E = 9$  and  $N = 5$ , the answer is  $(9 - (5 - 1)) = 5$  equations.
- d) Since there are 2 current sources we can say that they should be avoided because if we can't measure their voltage, we can't use KCL on that mesh.



G E E K D A Y

4.3

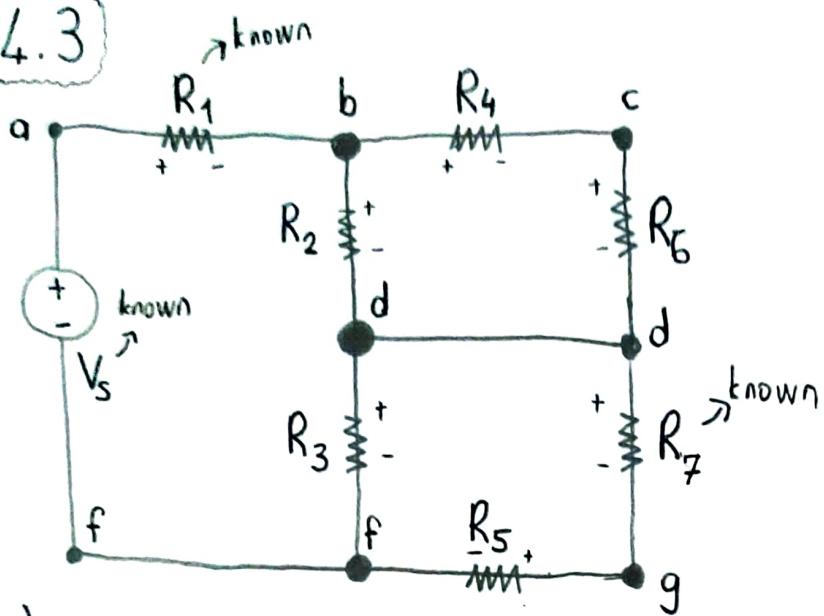

a)  $i_{R_1}, i_{R_2}, i_{R_3}, i_{R_4}, i_{R_5}, i_{R_6}, i_{R_7}, i_{V_s} \Rightarrow 8$  current but...

$(i_{R_1} = i_{V_s}), (i_{R_4} = i_{R_6}), (i_{R_7} = i_{R_5}) \Rightarrow 8 - 3 = 5$  unknown current

b)  $(N-1)$  gives number of equations can be written with KCL.  $N$ , is the number of essential nodes. since there are 3 essential nodes (b, d, f) on the circuit answer is  $\Rightarrow (3-1) = 2$  equations.

c) for node b  $\Rightarrow i_{R_1} = i_{R_2} + i_{R_4}$

for node d  $\Rightarrow i_{R_2} + i_{R_6} = i_{R_3} + i_{R_7}$

d)  $E - (N-1)$ ,  $E = \text{essential branches} = 5$  }  
 $N = \text{essential nodes} = 3$  }  $5 - (3-1) = 3$  equations

e)  $V_s = V_{R_1} + V_{R_2} + V_{R_3}$  or  $V_s = i_{R_1} \cdot R_1 + i_{R_2} \cdot R_2 + i_{R_3} \cdot R_3$

$$V_{R_2} = V_{R_4} + V_{R_6}$$

$$V_{R_3} = V_{R_5} + V_{R_7}$$

4.4

a) for node b  $\Rightarrow 0 = -i_{R_1} + i_{R_2} + i_4$

for node d  $\Rightarrow 0 = -i_{R_2} - i_{R_4} + i_{R_3} + i_{R_7}$

for node f  $\Rightarrow 0 = i_{R_1} - i_{R_3} - i_{R_7}$

b)  $-b = i_{R_1} - i_{R_2} - i_{R_4}$


$+ -d = i_{R_2} + i_{R_4} - i_{R_3} - i_{R_7}$

$-b - d = i_{R_1} - i_{R_3} - i_{R_7} = f //$



# GEEK DAY

4.11

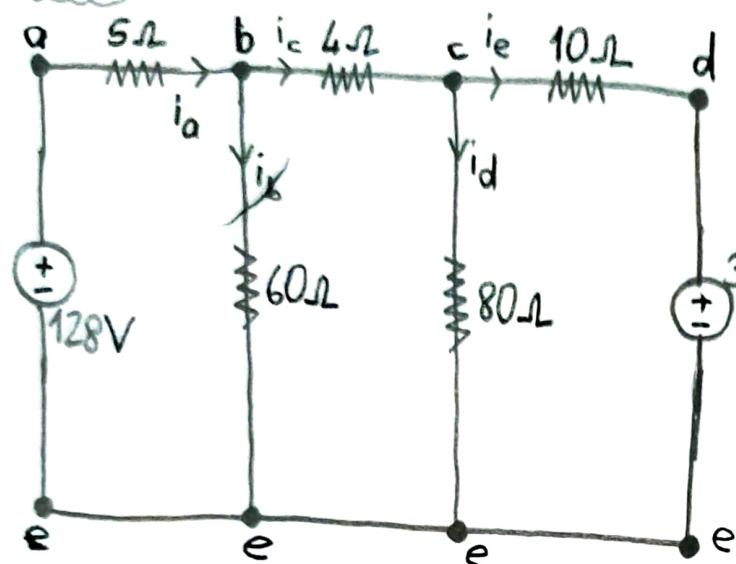

\* essential nodes = b, c, e

$$\begin{aligned} * \text{needed equation} &= N-1 \\ &= 3-1 \\ &= 2 \end{aligned}$$

\* e node is reference

a) for node b  $\Rightarrow \frac{V_b - 128}{5} + \frac{V_b}{60} + \frac{V_b - V_c}{4} = 0$

for node c  $\Rightarrow \frac{V_c - V_b}{4} + \frac{V_c}{80} + \frac{V_c - 320}{10} = 0$

$$\begin{aligned} b \Rightarrow 28V_b - 15V_c &= 1536 \\ c \Rightarrow 29V_c - 20V_b &= 2560 \end{aligned} \quad \left\{ \begin{array}{l} V_b = 162V \\ V_c = 200V \end{array} \right.$$


$$\begin{aligned} i_a &= \frac{128 - 162}{5} = -6.8A \\ i_e &= \frac{200 - 320}{10} = -12A \end{aligned}$$

b) For 128V source  $\Rightarrow P = V \cdot i = 128 \cdot (-6.8) = -870.4W$  (absorbs)

for 320V source  $\Rightarrow P = V \cdot i = -320 \cdot (-12) = 3840W$


↑  
develops  
power

IA


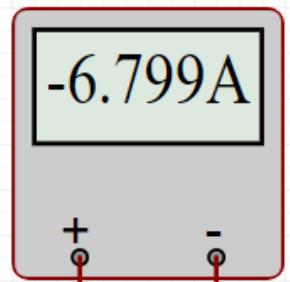


Question 4.11


IE

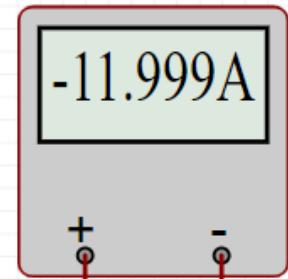

POWER

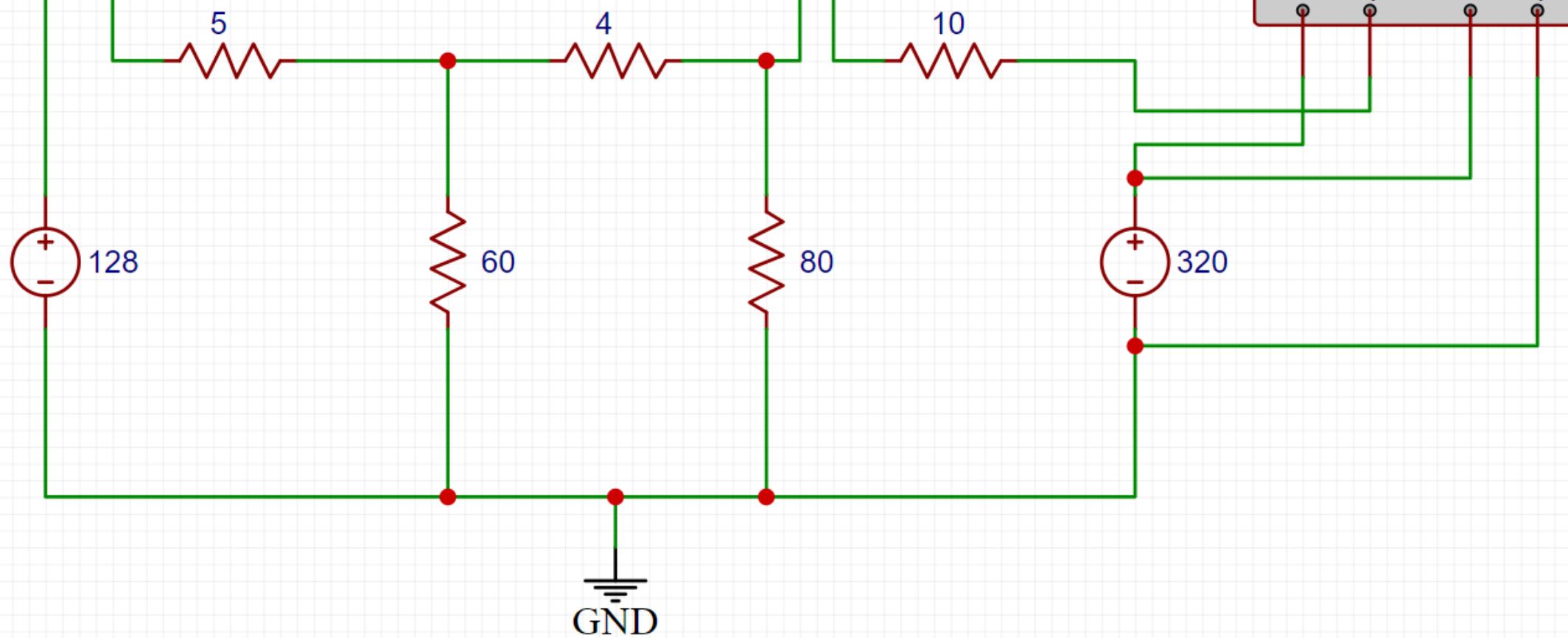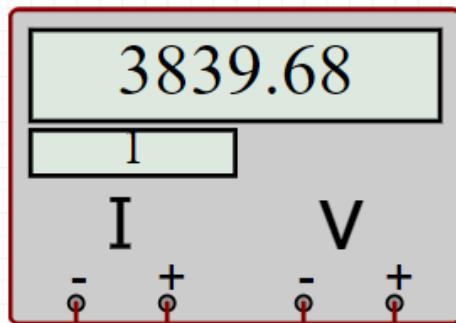

4.12

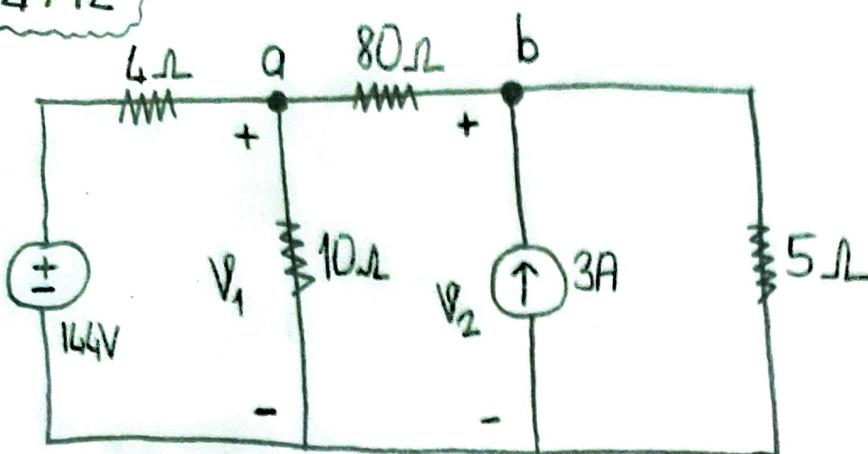

$$* \frac{V_1 - 144}{4} + \frac{V_1}{10} + \frac{V_1 - V_2}{80} = 0 \quad (\text{for } a)$$

$$* 20V_1 - 2880 + 8V_1 + V_1 - V_2 = 0$$

$$* V_2 = 29V_1 - 2880 \quad ① \dots$$

$$* \frac{V_2 - V_1}{80} - 3 + \frac{V_2}{5} = 0$$

$$* V_2 - V_1 - 240 + 16V_2 = 0$$

$$* V_1 = 17V_2 - 240 \quad ② \dots$$

$$* V_2 = 29(100) - 2880$$

$$V_2 = 2900 - 2880$$

$$V_2 = 20V$$


$$V_1 = 17(29V_1 - 2880) - 240$$

$$V_1 = 493V_1 - 48960 - 240$$

$$492V_1 = 49200$$

$$V_1 = 100V$$


Question 4.12

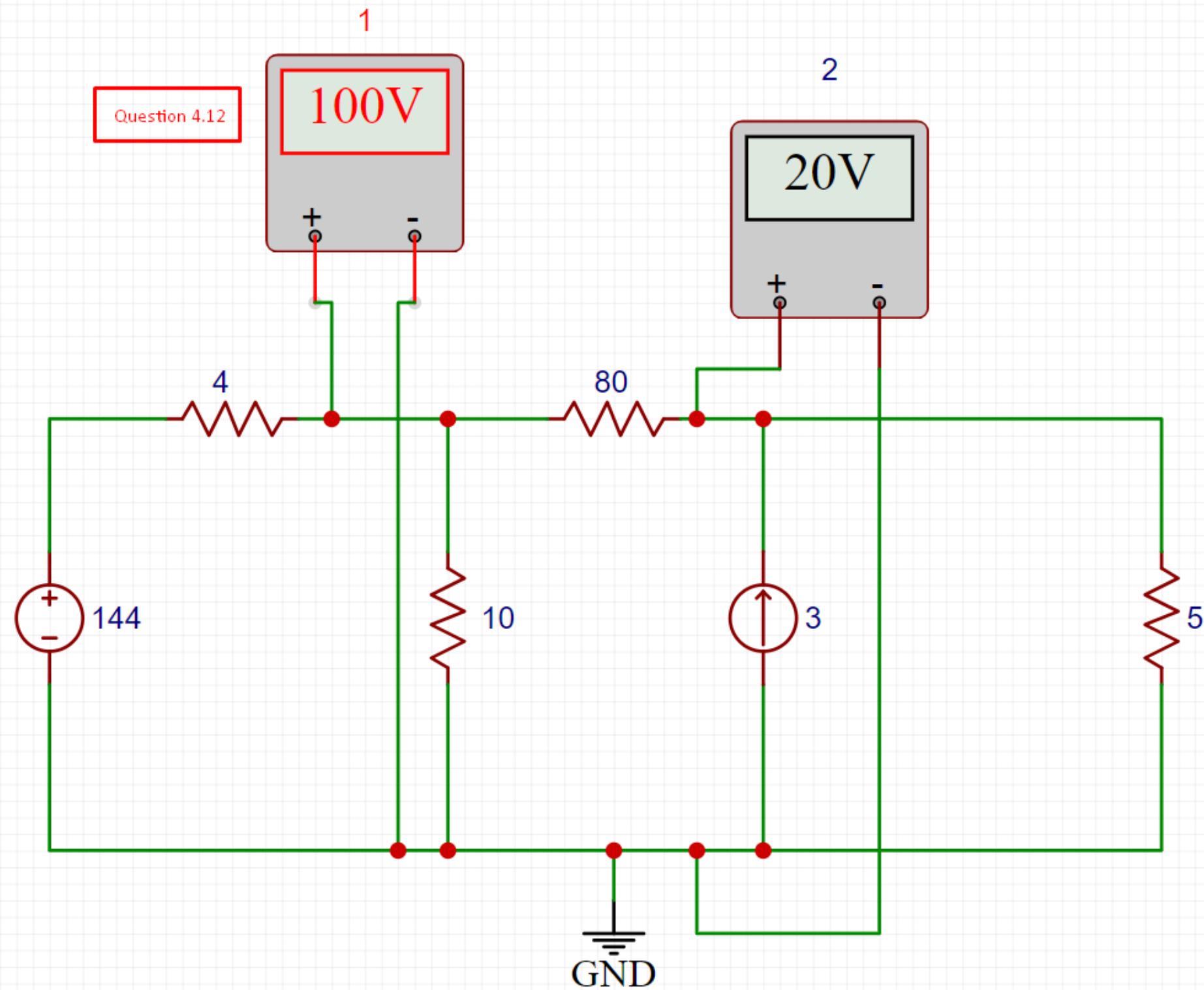



GEEK DAY

4.15

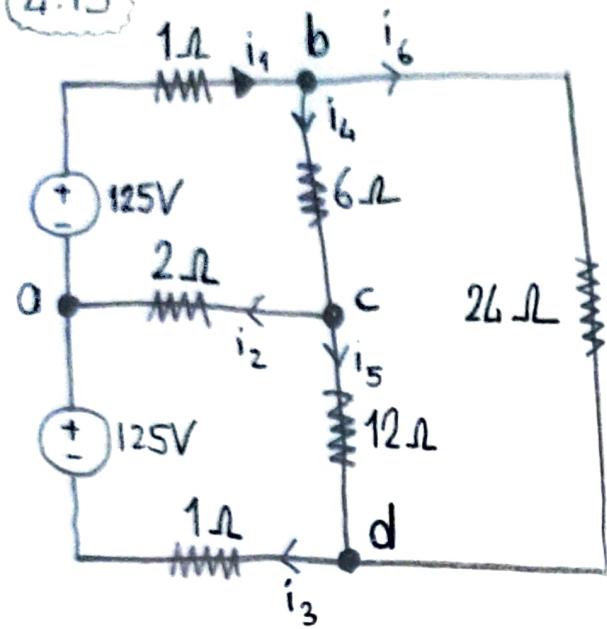

$$① \quad 29V_b - 4V_c - V_d = 3000$$

$$② \quad 2V_b - 9V_c + V_d = 0$$

$$\underline{31V_b - 13V_c = 3000} \quad \text{...}(x)$$

$$③ \quad 54V_b - 243V_c + 27V_d = 0$$

$$④ \quad V_b + 2V_c - 27V_d = -3000$$

$$\underline{55V_b - 241V_c = -3000} \quad \text{...}(y)$$

$$a) \text{ for } b \Rightarrow \frac{V_b - 125}{1} + \frac{V_b - V_d}{24} + \frac{V_b - V_c}{6} = 0$$

$$\Rightarrow 24V_b - 3000 + V_b - V_d + 4V_b - 4V_c = 0$$

$$\Rightarrow 29V_b - 4V_c - V_d = 3000 \quad \text{...}(1)$$

$$\text{for } c \Rightarrow \frac{V_c}{2} + \frac{V_c - V_b}{6} + \frac{V_c - V_d}{12} = 0$$

$$\Rightarrow 6V_c + 2V_c - 2V_b + V_c - V_d = 0$$

$$\Rightarrow 2V_b - 9V_c + V_d = 0 \quad \text{...}(2)$$

$$\text{for } d \Rightarrow \frac{V_d - 125}{1} + \frac{V_d - V_c}{12} + \frac{V_d - V_b}{24} = 0$$

$$\Rightarrow 24V_d - 3000 + 2V_d - 2V_c + V_d - V_b = 0$$

$$\Rightarrow V_b + 2V_c - 27V_d = -3000 \quad \text{...}(3)$$

$$x+y = 86V_b - 254V_c = 0 \Rightarrow \frac{V_b \cdot 63}{127} = V_c$$

$$V_b = 101V \text{ (rounded)}$$

$$V_c = 11V \text{ (rounded) for easy calculation}$$

$$V_d = -107V \text{ (rounded)}$$

$$i_1 = \frac{125 - V_b}{1} = \frac{125 - 101}{1} = 24A$$

$$i_2 = \frac{V_c}{2} = \frac{11}{2} = 5,5A$$

$$i_3 = \frac{V_d - (-125)}{1} = \frac{-107 + 125}{1} = 18V$$

$$i_4 = \frac{V_b - V_c}{6} = \frac{101 - 11}{6} = 15V$$

$$i_5 = \frac{V_c - V_d}{12} = \frac{11 - (-107)}{12} = \frac{118}{12} = 9,8V$$

$$i_6 = \frac{V_b - V_d}{24} = \frac{101 - (-107)}{24} = \frac{208}{24} = 8,7V$$

b)  $P = V_1 \cdot i_1 + V_3 \cdot i_3$  (developed)

$$= 125 \cdot 24 + 125 \cdot 18$$

$$= 3000 + 2250$$

$$= 5250W$$


$$P = (R_1 \cdot i_1) \cdot i_1 + (R_2 \cdot i_2) \cdot i_2 + \dots + (R_6 \cdot i_6) \cdot i_6$$

$$= 24^2 + 11 \cdot (5,5)^2 + 18^2 + 90 \cdot 15 + 118 \cdot (9,8) + 208 \cdot (8,7)$$


$$= 576 + 60,5 + 324 + 1350 + 1158 + 1802$$

$$= 5250W$$

Question 4.15

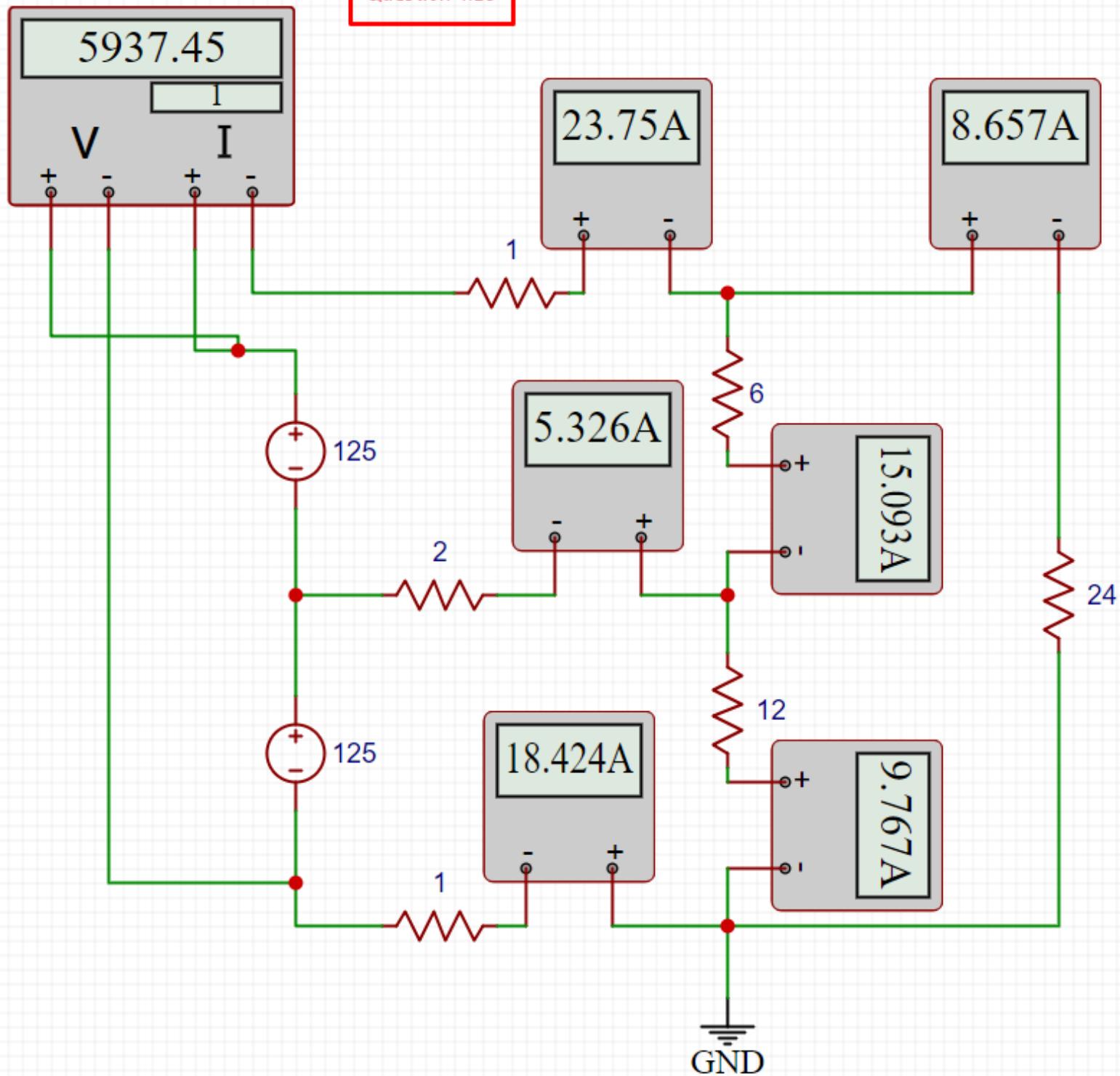

4.24

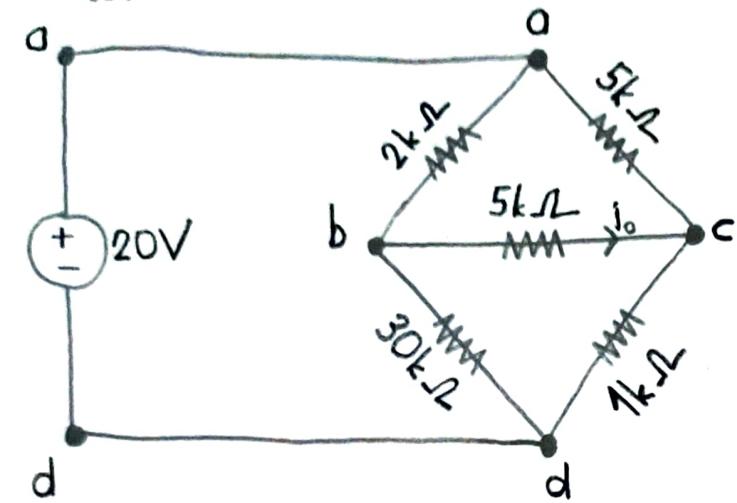

$$* \text{ for } b \Rightarrow \frac{V_b - 20}{2k} + \frac{V_b - V_c}{5k} + \frac{V_b}{30k} = 0 \quad \left\{ 11V_b - 3V_c = 150 \right. \quad (\times 7)$$


$$* \text{ for } c \Rightarrow \frac{V_c - 20}{5k} + \frac{V_c - V_b}{5k} + \frac{V_c}{1k} = 0 \quad \left\{ 7V_c - V_b = 20 \quad (\times 3) \right.$$

$$\begin{aligned} * 77V_b - 21V_c &= 1050 \\ 21V_c - 3V_b &= 60 \end{aligned} \quad \left\{ \begin{aligned} 74V_b &= 1110 \\ V_b &= 15V \\ V_c &= 5V \end{aligned} \right.$$


$$* i_o = \frac{V_b - V_c}{R} = \frac{15 - 5}{5k} = \boxed{2mA}$$

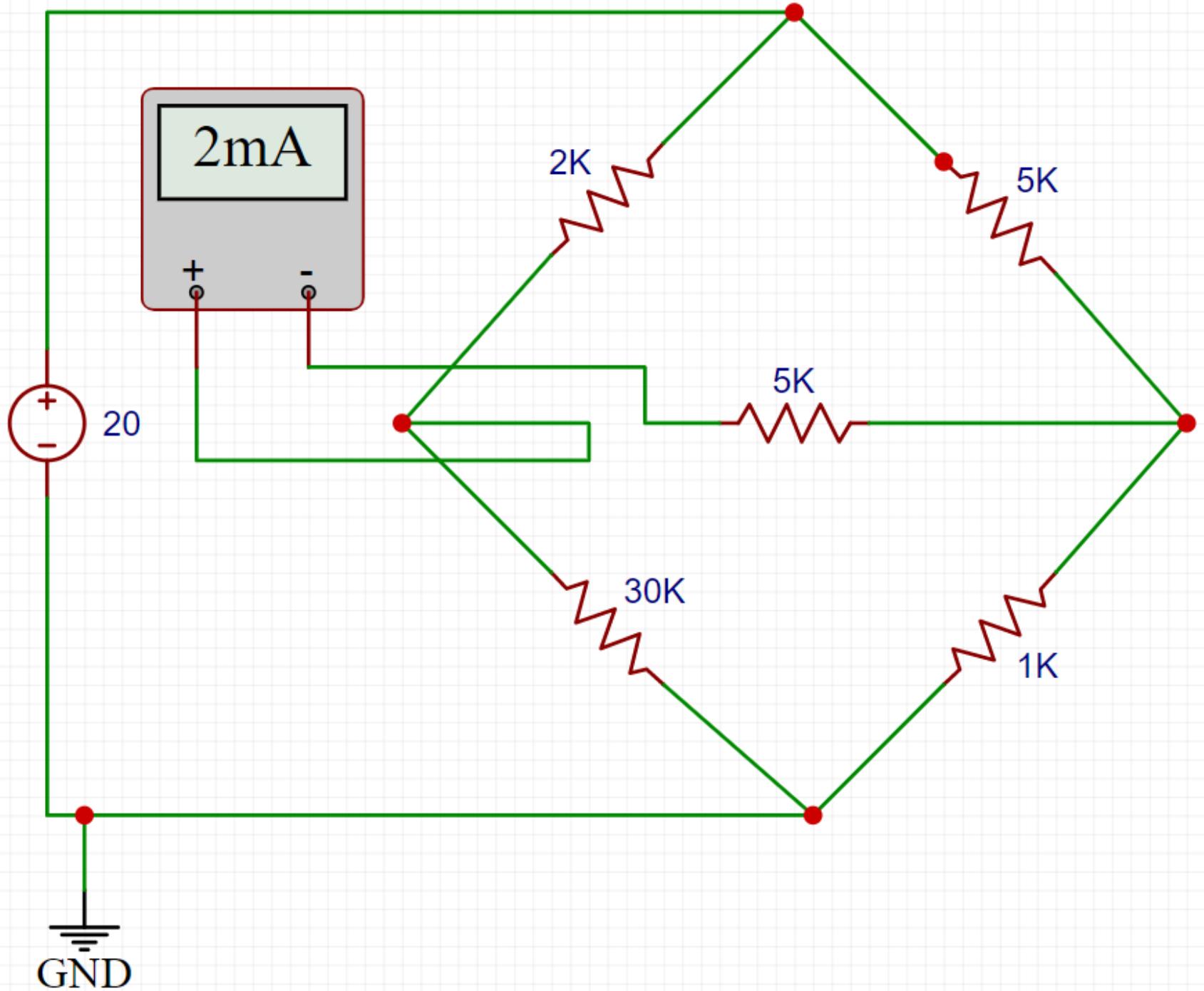Question 4.24

$I_o$   $\downarrow$   $\downarrow$   
V<sub>CC</sub> +5V X



4.27

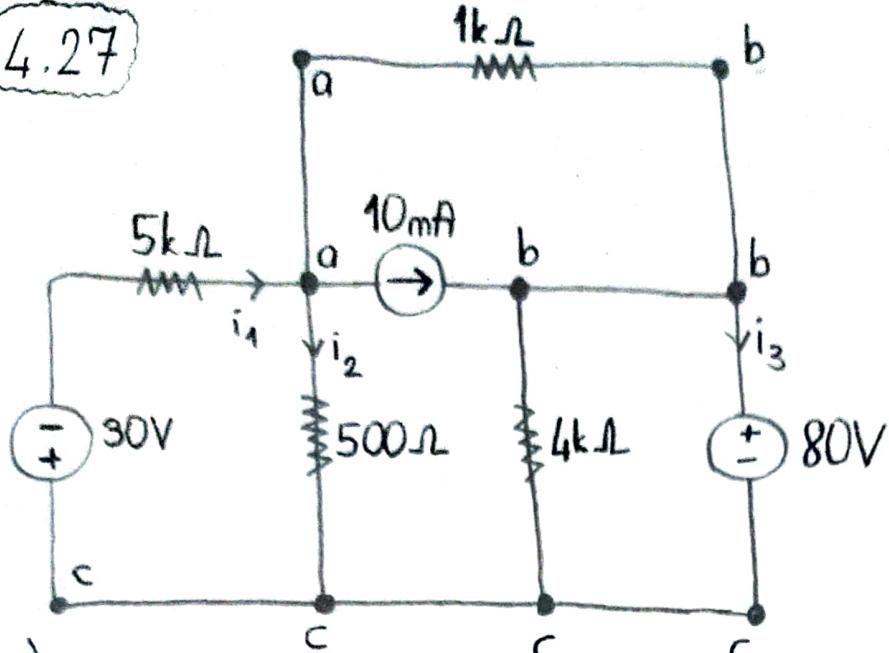

a)

$$* \text{ for node } a \Rightarrow \frac{V_a + 30}{5k} + \frac{V_a}{0,5k} + 0,01 + \frac{V_a - 80}{1k} = 0 \quad (\times 5k)$$

$$\Rightarrow 16V_a = 320, \quad V_a = 20V$$

$$* i_1 = -\frac{20+30}{5k} = -0,01A = -10mA$$


$$* i_2 = \frac{20}{0,5k} = 0,04A = 40mA$$

$$* i_3 = \frac{20-80}{1k} + 0,01 - \frac{80}{4k} = -0,07A = -70mA$$


$$\begin{aligned} b) \text{ developed power} \Rightarrow P &= 30V \cdot (-i_1) + 80V \cdot (-i_3) + 60V \cdot (10mA) \\ &= 0,3 + 5,6 + 0,6 \\ &= 6,5W \end{aligned}$$

$$\begin{aligned} \text{consumed power} \Rightarrow P &= (i_1^2 \cdot 5k) + (i_2^2 \cdot 0,5k) + \left(\frac{80}{4k}\right)^2 \cdot 4k + \left(\frac{60}{1k}\right)^2 \cdot 1k \\ &= 6,5W \end{aligned}$$

Question 4.27

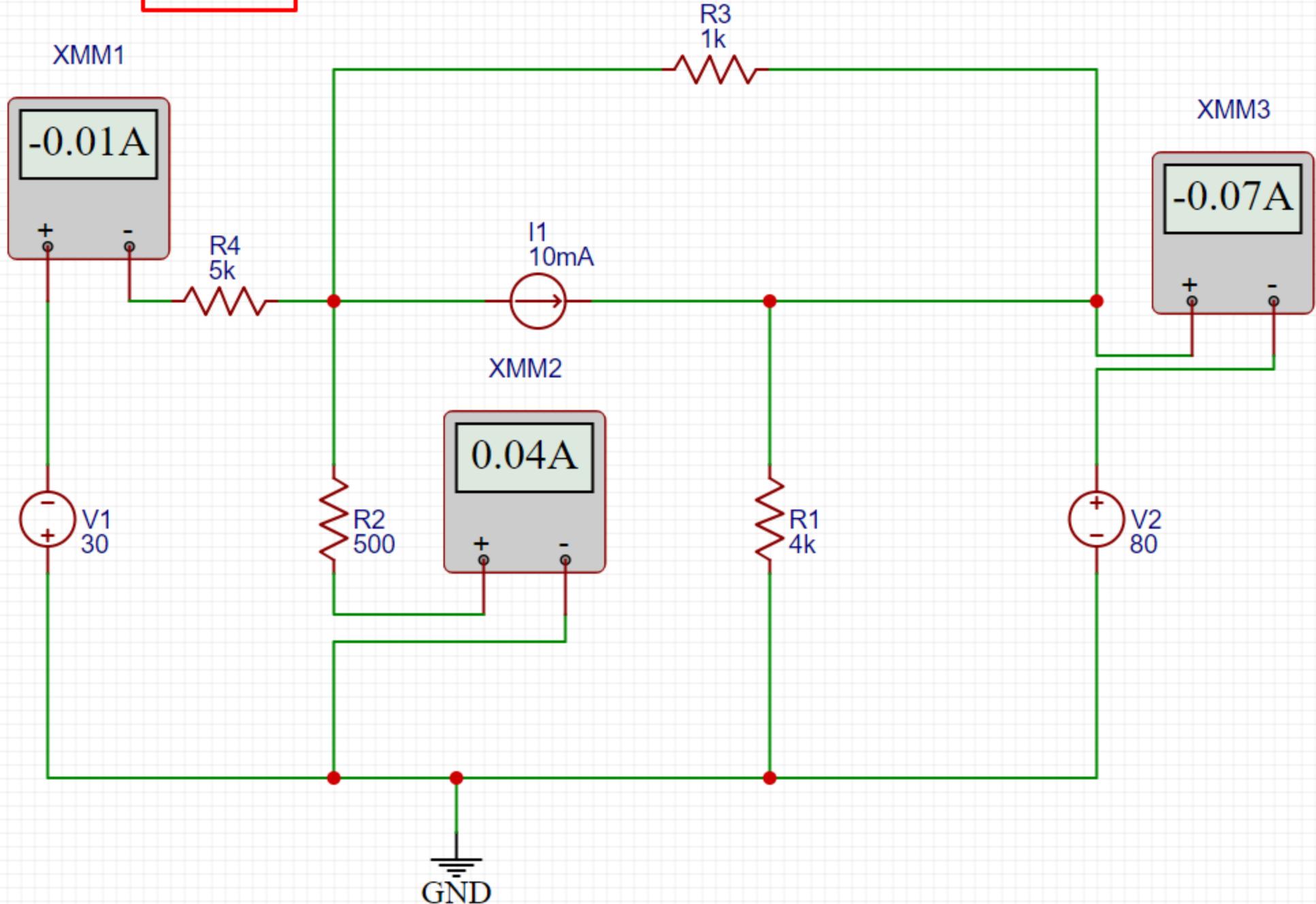

4.30

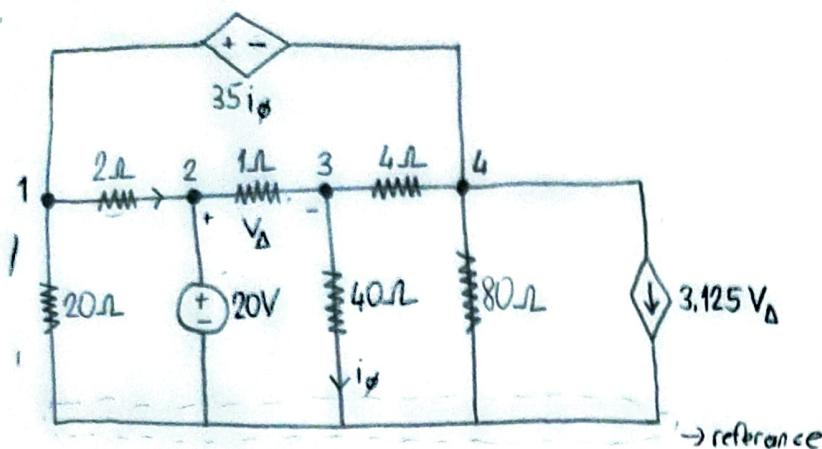

\* 1 and 4 nodes are supernode.

$$* V_1 - V_4 = 35i_\phi \dots \textcircled{1}$$

$$* V_2 = 20V \dots \textcircled{2}$$

$$* V_3 = 20 - V_\Delta \dots \textcircled{3}$$

\* node-voltage method for node 3

$$\rightarrow -\frac{V_\Delta}{1} + \frac{20 - V_\Delta}{40} + \frac{20 - V_\Delta - V_4}{4} = 0 \quad (\times 40)$$

$$\rightarrow -40V_\Delta + 20 - V_\Delta + 200 - 10V_\Delta - 10V_4 = 0$$

$$\rightarrow -51V_\Delta - 10V_4 + 220 = 0 \dots \textcircled{4}$$

\* node-voltage method for nodes 1 and 4 (since they are supernodes)

$$\rightarrow \frac{V_1}{20} + \frac{V_1 - 20}{2} + \frac{V_4 - (20 - V_\Delta)}{4} + \frac{V_4}{80} + 3.125V_\Delta = 0 \quad (\times 80)$$

$$\rightarrow 4V_1 + 40V_1 - 800 + 20V_4 + 20V_\Delta - 400 + V_4 + 250V_\Delta = 0$$

$$\rightarrow 44V_1 + 21V_4 + 270V_\Delta = 1200 \dots \textcircled{5}$$

\*  $i_\phi$  equation on node 3

$$\rightarrow \frac{20 - V_\Delta}{40} = i_\phi \rightarrow (20 - V_\Delta) \cdot 35 = 40(V_1 - V_4) \rightarrow 8V_1 - 8V_4 + 7V_\Delta = 140 \dots \textcircled{6}$$

\* unknowns  $\rightarrow V_\Delta, V_1, V_4$  equation  $\rightarrow \textcircled{4}, \textcircled{5}, \textcircled{6}$

$$x = \begin{bmatrix} 0 & -10 & -51 \\ 44 & 21 & 270 \\ 8 & -8 & 7 \end{bmatrix} \quad y = \begin{bmatrix} -220 \\ 1200 \\ 140 \end{bmatrix} \quad A = \begin{bmatrix} V_1 \\ V_4 \\ V_\Delta \end{bmatrix}$$

\* power developed by 20V

$$\rightarrow P = V \cdot i \quad \text{where } V = 20$$


$$\begin{aligned} i &= \frac{V_2 - V_1}{2} + \frac{V_\Delta}{1} \\ &= \frac{20 + 20.25}{2} + 10 \end{aligned}$$

$$= 30.125A$$


$$\rightarrow P = 20 \cdot (30.125) \\ = 602.5W$$

$$\begin{aligned} V_\Delta &= 10V & V_4 &= -29V \\ V_1 &= -20.25V & i_\phi &= 0.25A \end{aligned}$$

Question 4.30

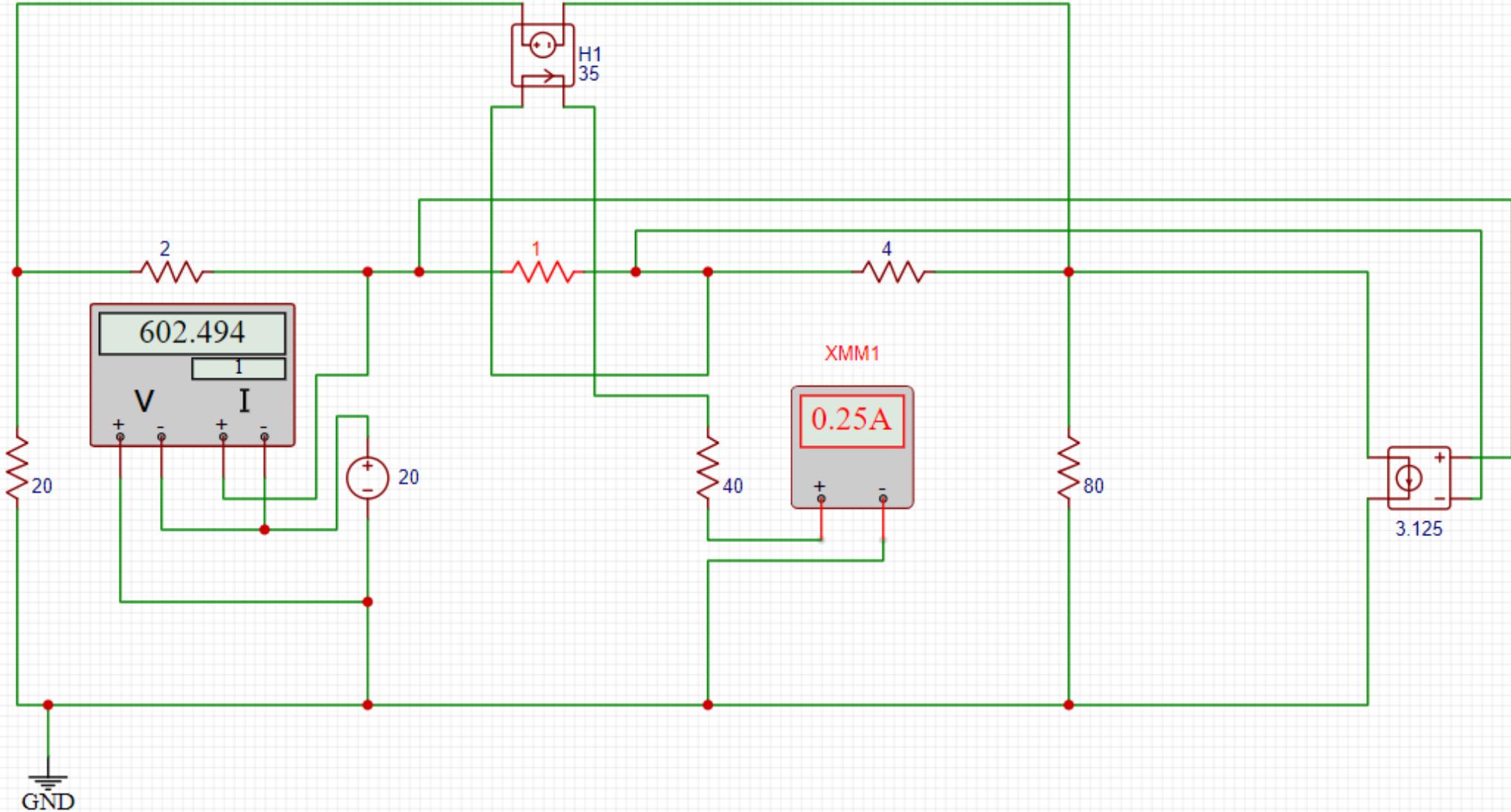

4.36

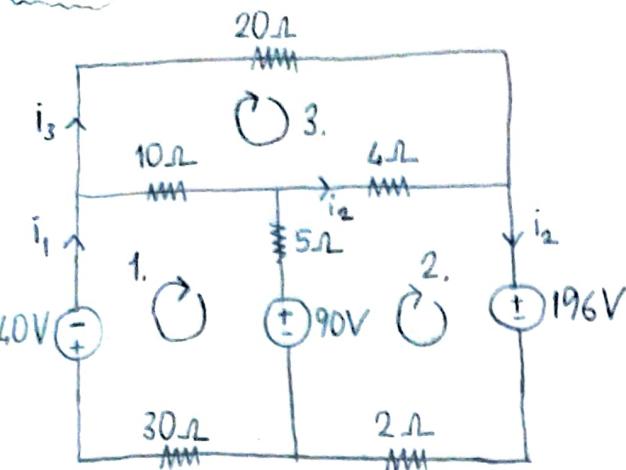for mesh 1 (KVL)

$$* -40 + 10(i_1 - i_3) + 5(i_1 - i_2) - 90 + 30i_1 = 0$$

$$-40 + 10i_1 - 10i_3 + 5i_1 - 5i_2 - 90 + 30i_1 = 0$$

$$45i_1 - 5i_2 - 10i_3 = 130 \dots \textcircled{1}$$

for mesh 2 (KVL)

$$* 90 + 5(i_2 - i_1) + 4(i_2 - i_3) - 196 + 2i_2 = 0$$

$$90 + 5i_2 - 5i_1 + 4i_2 - 4i_3 - 196 + 2i_2 = 0$$

$$-5i_1 + 11i_2 - 4i_3 = +106 \dots \textcircled{2}$$

for mesh 3 (KVL)

$$* 10(i_3 - i_1) + 20i_3 + 4(i_3 - i_2) = 0$$

$$10i_3 - 10i_1 + 20i_3 + 4i_3 - 4i_2 = 0$$

$$-10i_1 - 4i_2 + 34i_3 = 0 \dots \textcircled{3}$$

matrix

$$\begin{bmatrix} 45 & -5 & -10 \\ -5 & 11 & -4 \\ -10 & -4 & +34 \end{bmatrix} = x, \quad y = \begin{bmatrix} 130 \\ 106 \\ 0 \end{bmatrix}, \quad A = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

$$i_1 = 5A$$

$$i_2 = 13A$$

$$i_3 = 3A$$

a)  $2748W$  developedb)  $P_{dev} = P_{dis}$ powerfor -40V

$$P = V_i \cdot i_1 \quad V_i = -40V$$

$$i_1 = 5A$$

$$P = -40 \cdot 5$$

$= -200W$  (developed power)

for -90V

$$P = V_i \cdot i \quad i = i_1 - i_2$$

$$= -90 \cdot (-8) \quad = 5 - 13$$

$$= +720W \text{ (absorbs power)}$$

for -192V

$$P = V_i \cdot i \quad V_i = -192$$

$$= (-192) \cdot 13 \quad i = 13A$$

$= -2548W$  (developed power)

total developed

$$200 + 2548 = 2748W$$

total dissipated  $i_1^2 \cdot 30 = 750W$ 

$$(i_1 - i_3)^2 \cdot 10 = 40W$$

$$(i_1 - i_2)^2 \cdot 5 = 64.5 = 320W$$

$$(i_2 - i_3)^2 \cdot 4 = 100.4 = 400W$$


$$i_3^2 \cdot 2Q = 9.20 = 180W$$

$$i_2^2 \cdot 2 = 169.2 = 338W$$


$$i_1^2 \cdot 2 = 90.8 = 720W$$

$\left. \begin{array}{l} 2748W \\ \text{dissipated} \end{array} \right\}$

## Question 4.36

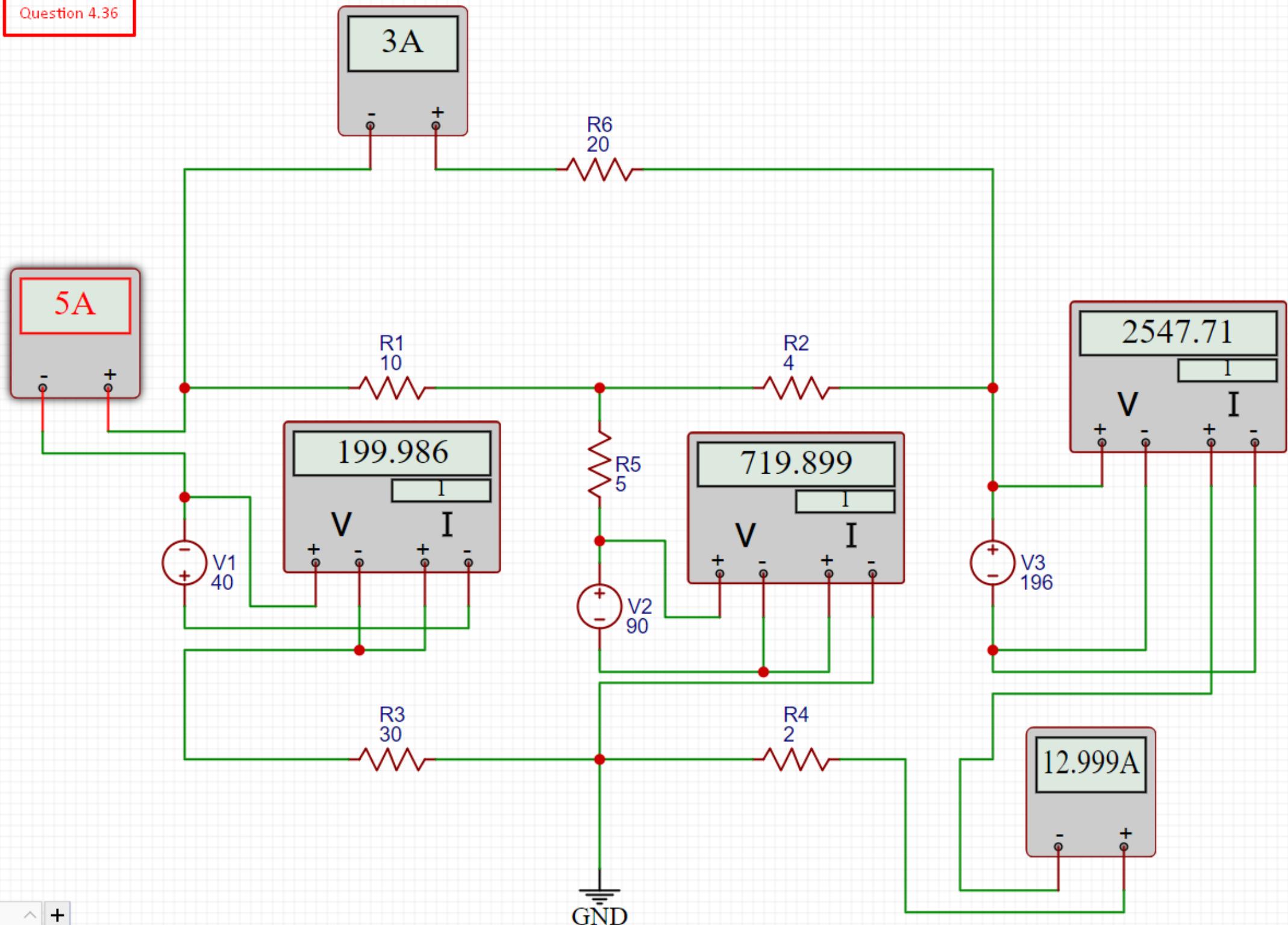

4.39

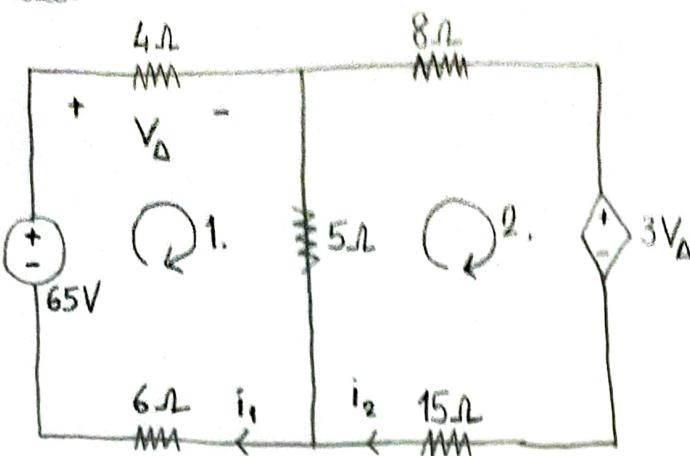for mesh 1 (KVL)

$$* 65 - V_\Delta + (i_1 - i_2) \cdot 5 + 6i_1 = 0$$

$$65 - V_\Delta + 5i_1 - 5i_2 + 6i_1 = 0$$

$$11i_1 - 5i_2 - V_\Delta = -65 \dots \textcircled{1}$$

power dissipated in the 15Ω resistor

$$\begin{aligned} P &= V \cdot i = i \cdot R \cdot i = i^2 \cdot R \\ &= (1)^2 \cdot 15 \end{aligned}$$

$$\begin{aligned} R &= 15 \Omega \\ i &= i_2 = 1A \end{aligned}$$

$$P = 15W \text{ dissipated}$$

for mesh 2 (KVL)

$$* 5(i_2 - i_1) + 8i_2 - 3V_\Delta + 15i_2 = 0$$

$$5i_2 - 5i_1 + 8i_2 - 3V_\Delta + 15i_2 = 0$$

$$-5i_1 + 28i_2 - 3V_\Delta = 0 \dots \textcircled{2}$$

 $V_\Delta$  equation

$$-V_\Delta = R \cdot i_1$$

$$-V_\Delta = 4 \cdot i_1$$

equation  $\textcircled{1}$  and  $\textcircled{2}$ 

$$* 11i_1 - 5i_2 - V_\Delta = -65 \quad * -5i_1 + 28i_2 - 3V_\Delta = 0$$

$$11i_1 - 5i_2 + 4i_1 = -65 \quad -5i_1 + 28i_2 + 12i_1 = 0$$

$$15i_1 - 5i_2 = -65 \quad (x4) \quad 7i_1 + 28i_2 = 0$$


$$60i_1 - 20i_2 = -260 \quad \cancel{i_1 + 4i_2 = 0} \quad (x5)$$

$$5i_1 + 20i_2 = 0 \quad i_1 = -4A$$


$$65i_1 = -260 \quad i_2 = 1A$$

$$i_1 = -4A$$

Question 4.39

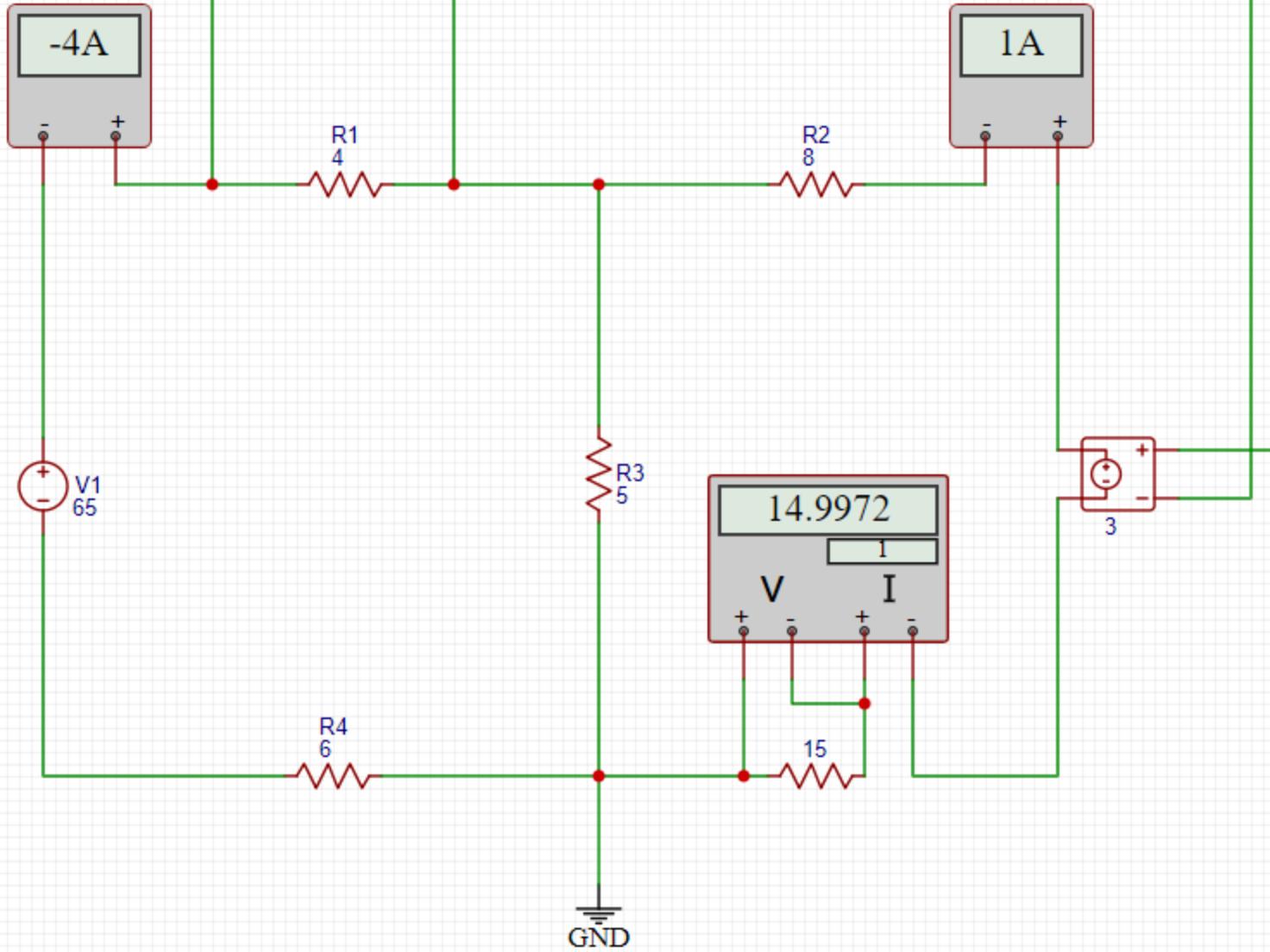

4.46

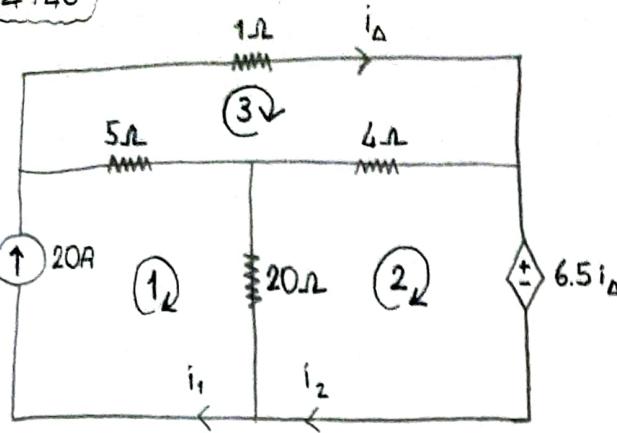for mesh 1

$$i_1 = 20A$$

for mesh 2

$$* 20(i_2 - 20) + 4(i_2 - i_\Delta) + 6.5i_\Delta = 0$$

$$20i_2 - 400 + 4i_2 + 2.5i_\Delta = 0$$

$$24i_2 + 2.5i_\Delta = 400 \dots \textcircled{1}$$

for mesh 3

$$* 5(i_\Delta - 20) + i_\Delta + 4(i_\Delta - i_2) = 0$$

$$5i_\Delta - 100 + i_\Delta + 4i_\Delta - 4i_2 = 0$$

$$-4i_2 + 10i_\Delta = 100 \dots \textcircled{2}$$

equations (1) and (2)

$$* 24i_2 + 2.5i_\Delta = 400$$

$$-4i_2 + 10i_\Delta = 100 \quad (\times 6)$$

$$* 24i_2 + 2.5i_\Delta = 400$$

$$-24i_2 + 60i_\Delta = 600$$

$$\underline{+} \quad 62.5i_\Delta = 1000$$

$$i_\Delta = 16A$$

$$i_1 = 20A$$

$$i_2 = 15A$$

$$i_\Delta = 16A$$

total power developed in the circuit

for 20A (KVL)

$$* -V + 5.4 + 20(20 - i_2) = 0$$

$$-V + 20 + 400 - 20.15 = 0$$

$$-V + 420 - 300 = 0$$

$$V =$$

$$* P = V.i$$

$$= -120, 20$$

= -2400W developed


for  $6.5i_\Delta$

$$* P = V.i \quad V = 6.5 \cdot 16 = 104$$


$$P = 104 \cdot 15 \quad i = 15A$$

$$= 1560W \text{ consumed}$$

Question 4.46

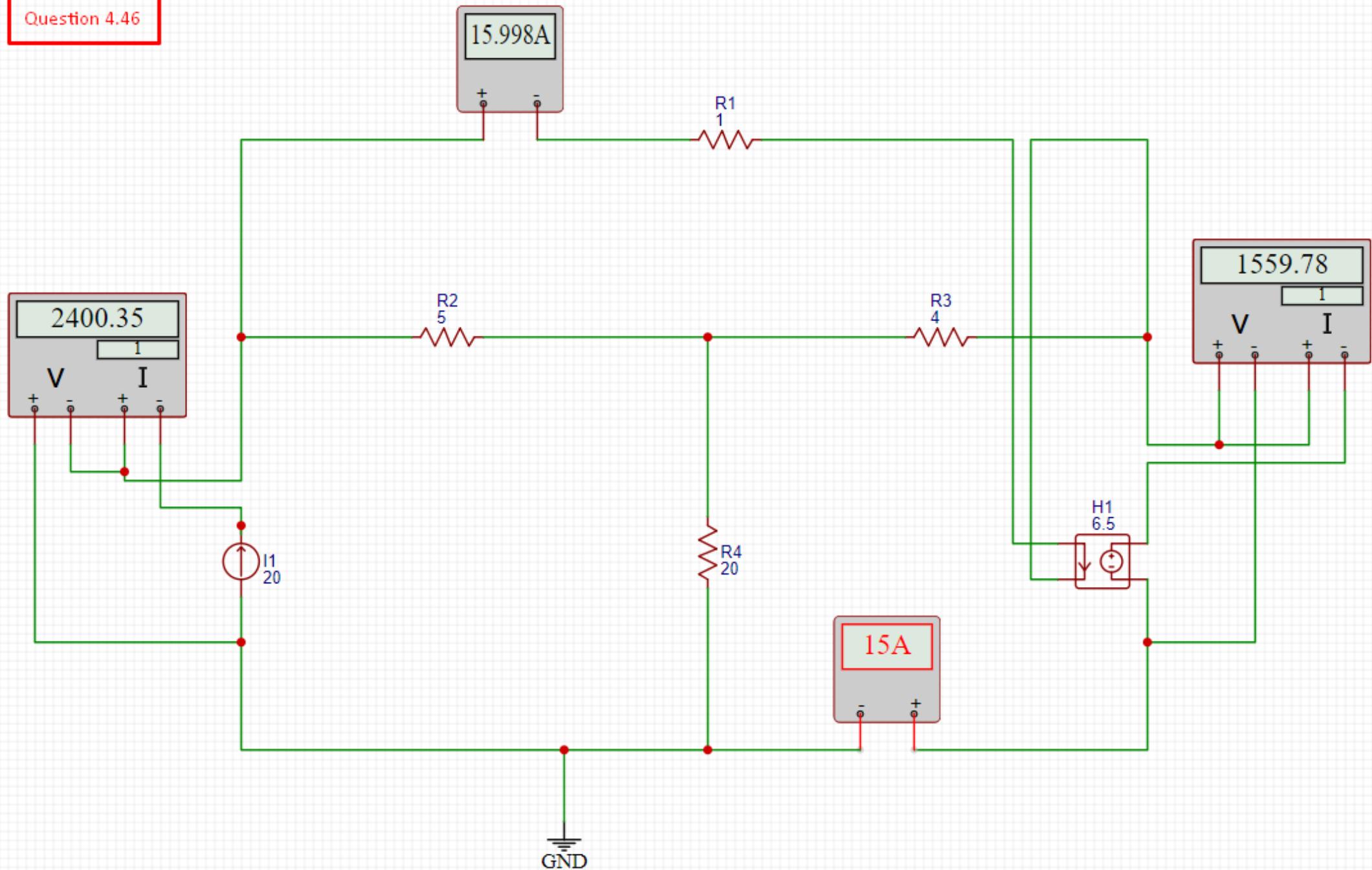

4.47

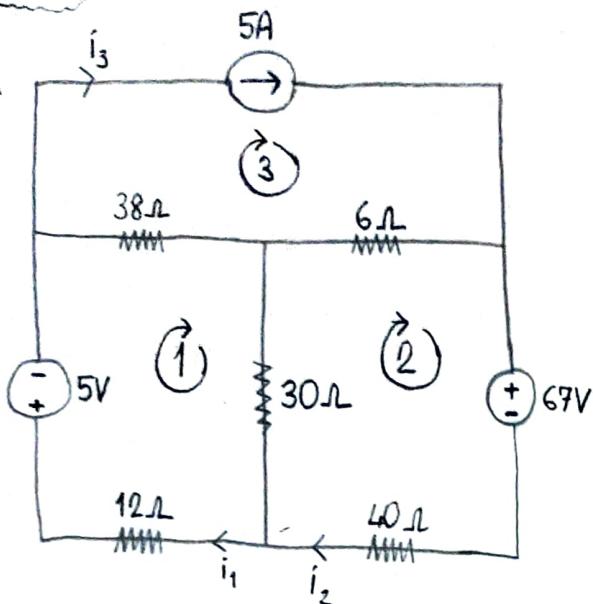For mesh 1

$$\begin{aligned} * +5 + 38(i_1 - 5) + 30(i_1 - i_2) + 12i_1 &= 0 \\ +5 + 38i_1 - 190 + 30i_1 - 30i_2 + 12i_1 &= 0 \\ 80i_1 - 30i_2 &= 185 \dots \textcircled{1} \quad (\times 3) \end{aligned}$$

For mesh 2

$$\begin{aligned} * 30(i_2 - i_1) + 6(i_2 - 5) + 67 + 40i_2 &= 0 \\ 30i_2 - 30i_1 + 6i_2 - 30 + 67 + 40i_2 &= 0 \\ -30i_1 + 76i_2 &= -37 \dots \textcircled{2} \quad (\times 8) \end{aligned}$$

equation ① and ②

$$\begin{aligned} * 240i_1 - 90i_2 &= 555 \\ -240i_1 + 608i_2 &= -296 \\ 518i_2 &= 259 \\ i_2 &= 0,5 \text{ A} \end{aligned}$$

$$* i_1 = 2,5 \text{ A}$$

$$i_2 = 0,5 \text{ A} //$$

voltage of 5A current source (KVL)

$$\begin{aligned} -V_x + 6(5 - i_2) + 38(5 - i_1) &= 0 \\ -V_x + 6(4,5) + 38(2,5) &= 0 \\ V_x &= 27 + 95 \\ V_x &= 122 \text{ V} // \end{aligned}$$

$$a) P = -V_x \cdot i \quad V_x = 122 \text{ V}$$

$$\begin{aligned} i &= 5 \text{ A} \\ P &= -122,5 \\ &= -610 \text{ W (delivers)} \end{aligned}$$

$$b) P_1 = 5 \cdot (2,5) \\ = 12,5 \text{ W (absorbs)}$$


$$\begin{aligned} P_2 &= 67 \cdot (0,5) \\ &= 33,5 \text{ W (absorbs)} \end{aligned}$$

$$\begin{aligned} P_3 &= -122,5 \\ &= -610 \text{ W (delivers)} \end{aligned}$$


total power delivered to the circuit

$$\begin{aligned} c) P_1 + P_2 + 38(2,5)^2 + 12(2,5)^2 + 30(2)^2 + 40(0,5)^2 + 6(4,5)^2 \\ (12,5) + (33,5) + (237,5) + 75 + 120 + 10 + 121,5 &= P_{\text{dis}} \\ P_{\text{diss}} &= 610 \text{ W} \\ ) &= \\ P_{\text{dev}} &= 610 \text{ W} \end{aligned}$$

Question 4.47

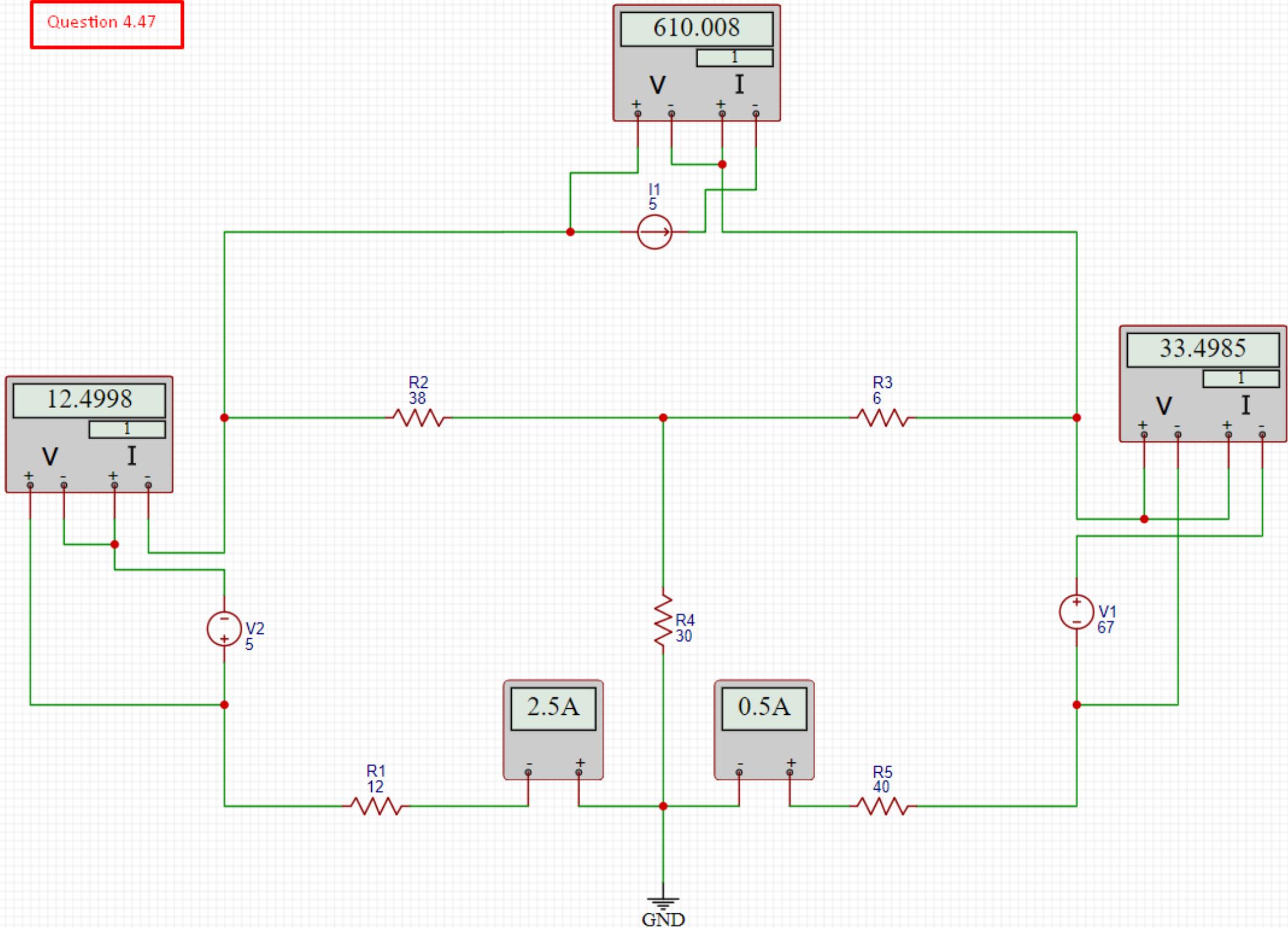

4.54

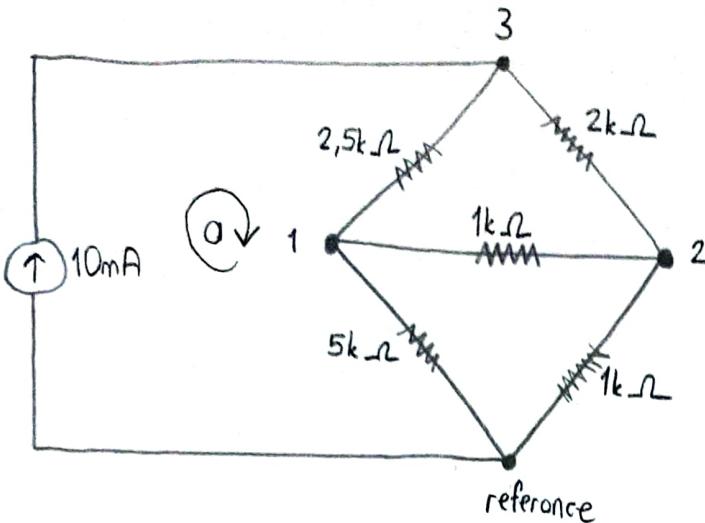

a) I would recommend node-voltage method since it is easy to write equations rather than mesh-current method in this kind of questions.

b) for node 1 (KCL)

$$* \frac{V_1 - V_3}{2.5k} + \frac{V_1 - V_2}{1k} + \frac{V_1}{5k} = 0 \quad (\times 5k)$$

$$2V_1 - 2V_3 + 5V_1 - 5V_2 + V_1 = 0$$

$$8V_1 - 5V_2 - 2V_3 = 0 \quad \dots \dots \dots \textcircled{1}$$

for node 2 (KCL)

$$* \frac{V_2 - V_3}{2k} + \frac{V_2 - V_1}{1k} + \frac{V_2}{1k} = 0 \quad (\times 2k)$$

$$V_2 - V_3 + 2V_2 - 2V_1 + 2V_2 = 0$$

$$-2V_1 + 5V_2 - V_3 = 0 \quad \dots \dots \dots \textcircled{2}$$

for node 3

$$* -10\text{mA} + \frac{V_3 - V_1}{2.5k} + \frac{V_3 - V_2}{2k} = 0 \quad (\times 10k)$$

$$-100 + 4V_3 - 4V_1 + 5V_3 - 5V_2 = 0$$

$$-4V_1 - 5V_2 + 9V_3 = 100 \quad \dots \dots \dots \textcircled{3}$$

metris

$$\begin{bmatrix} 8 & -5 & -2 \\ -2 & +5 & -1 \\ -4 & -5 & +9 \end{bmatrix} = x, \quad y = \begin{bmatrix} 0 \\ 0 \\ 100 \end{bmatrix}, \quad A = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \Rightarrow$$

$$\begin{bmatrix} 0 \\ 0 \\ 100 \end{bmatrix}$$

power dissipated in 1kΩ

$$p = V \cdot i$$

$$V = V_1 - V_2 = 10 - 8 = 2V$$

$$i = \frac{V}{R} = \frac{2}{1k} = 2\text{mA}$$

$$= 4\text{mW}$$

c) yes, I would change since I take the bottom node of the circuit as a reference. I would've need to write an equation for that but since I know the voltage values applying mesh-current method is a lot easier,

d) for mesh a

$$-V_a + (V_3 - V_1) + (V_1) = 0$$

$$V_a = (20 - 10) + (10)$$

$$V_a = 20V$$

power delivered by 10mA current source


$$p = V \cdot i \quad V = 20$$

$$= 20 \cdot 10\text{mA} \quad i = 10\text{mA}$$


$$= 200\text{mW} = 0.2\text{W}$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \Rightarrow \begin{array}{l} V_1 = 10V \\ V_2 = 8V \\ V_3 = 20V \end{array}$$

Question 4.54






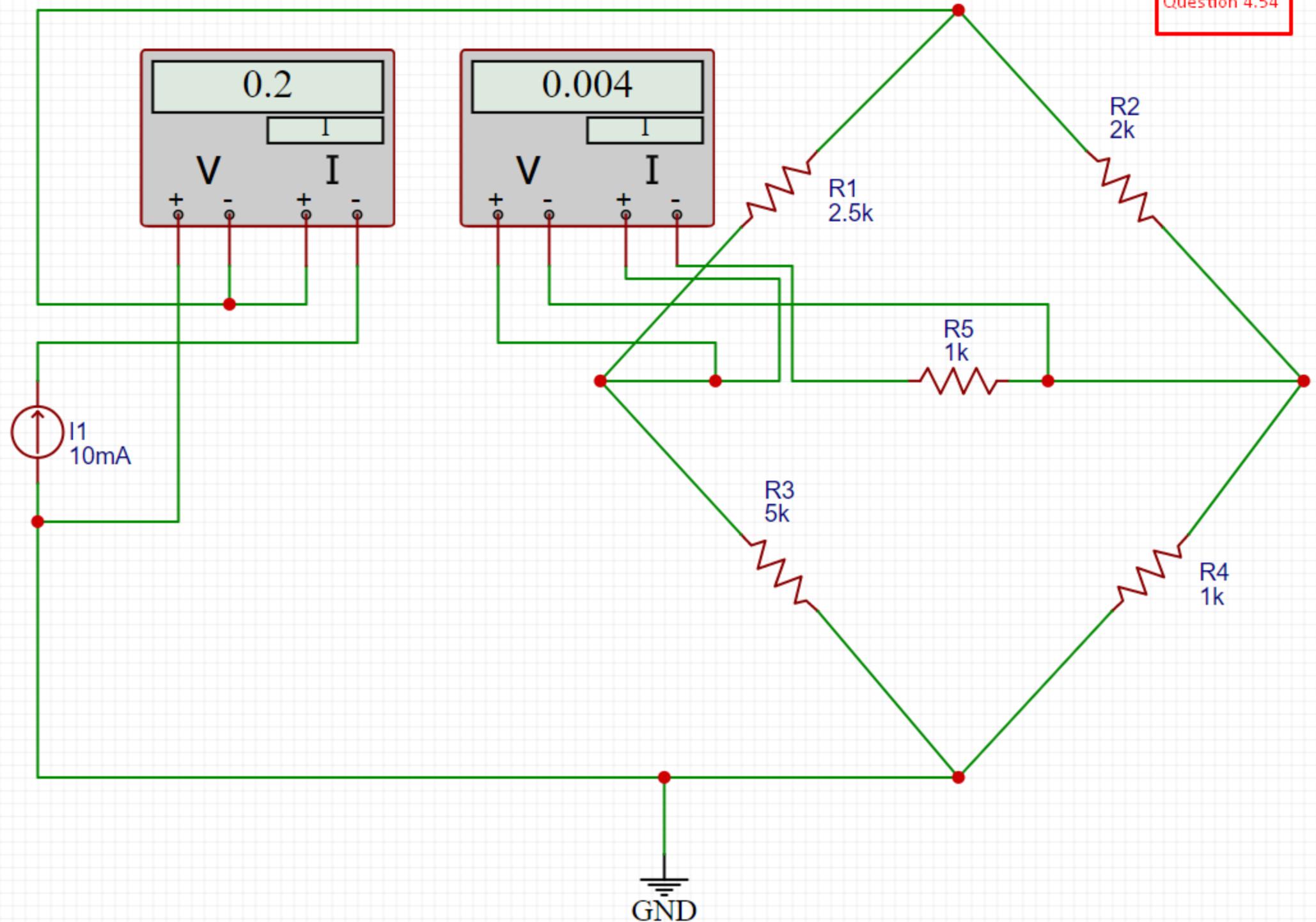


4.59

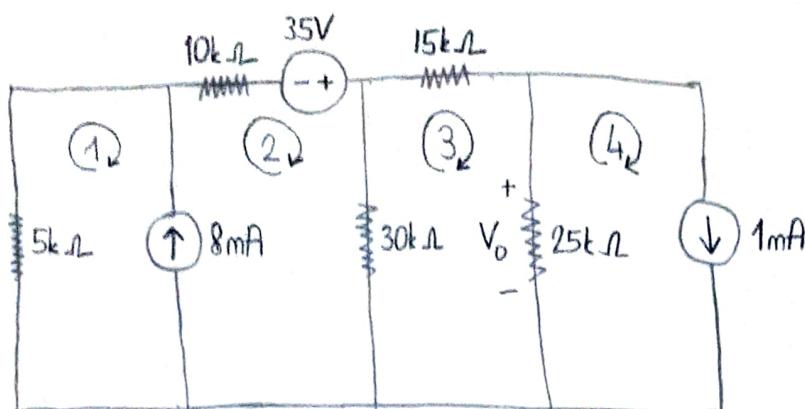

a)

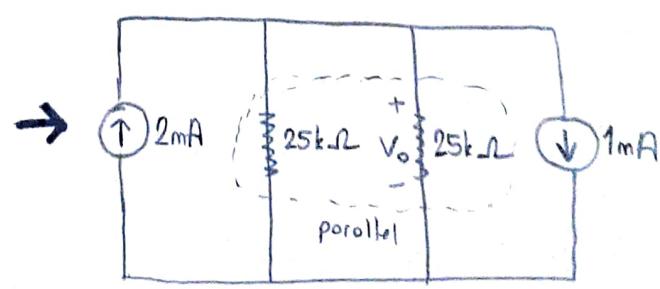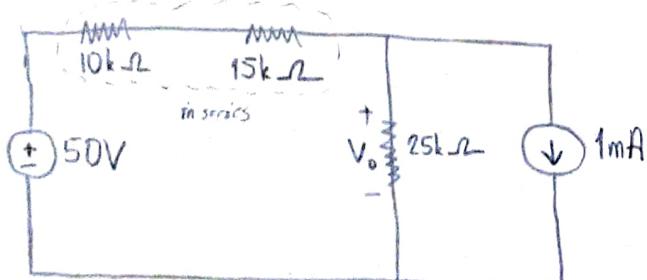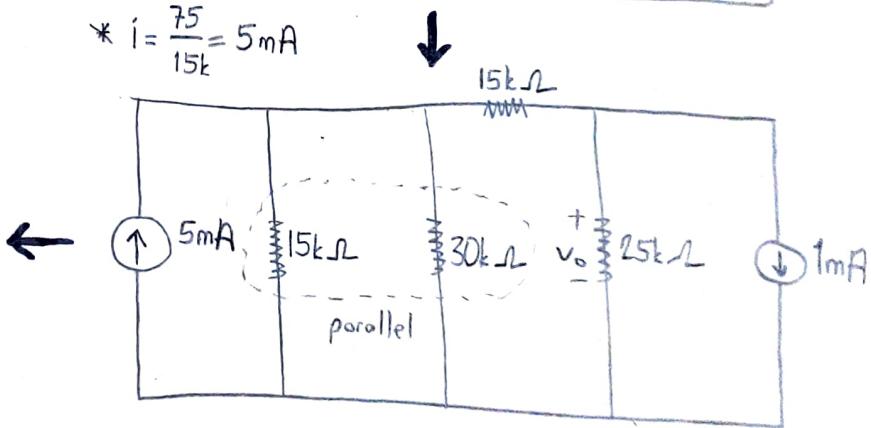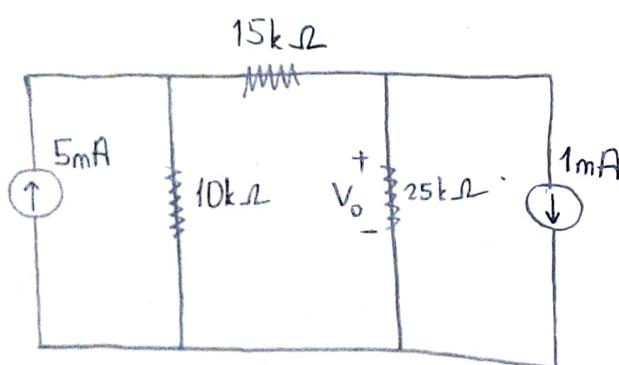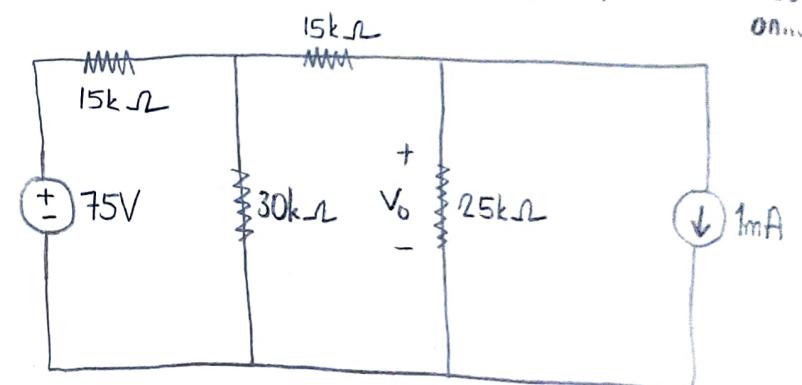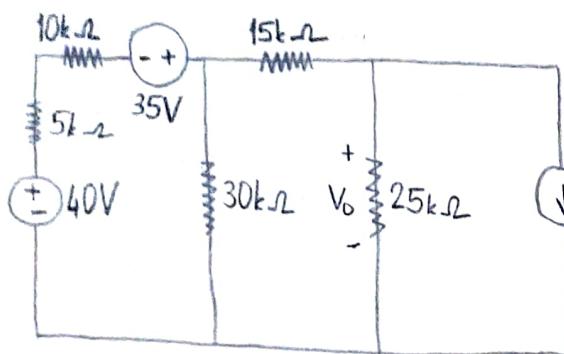\* We can transform  $5\text{k}\Omega$  resistor and  $8\text{mA}$  current source to a voltage source since they are parallel. And so




$$R = 12,5\text{k}\Omega$$

$$V_o = R \cdot i$$

$$\begin{aligned} i &= (2\text{mA} - 1\text{mA}) \\ &= 1\text{mA} \end{aligned}$$
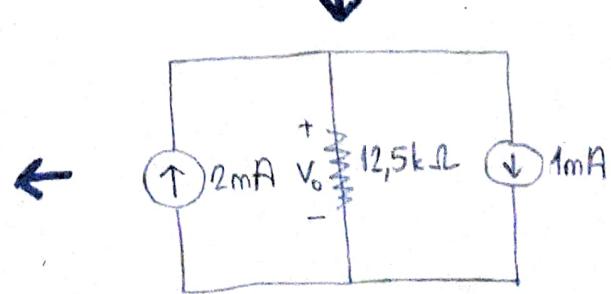
$$\begin{aligned} V_o &= 12,5\text{k}\Omega \cdot 1\text{mA} \\ V_o &= 12,5\text{V} \end{aligned}$$





b) for mesh 1-2 (supermesh)

$$* 5k(i_1) + 10k(i_2) - 35 + 30k(i_2 - i_3) = 0$$

$$5k(i_1) + 40k(i_2) - 30k(i_3) = 35$$

$$1k(i_1) + 8k(i_2) - 6k(i_3) = 7 \dots \textcircled{1}$$

$$* i_2 - i_1 = 8\text{mA} \dots \textcircled{2}$$

for mesh 3

$$* 30k(i_3 - i_2) + 15k(i_3) + 25k(i_3 - 1\text{mA}) = 0$$

$$0 - 30k(i_2) + 70k(i_3) = 25 \dots \textcircled{3}$$

matrix

$$\begin{bmatrix} 1k & 8k & -6k \\ -1k & 1k & 0 \\ 0 & -30k & 70k \end{bmatrix} = x, y = \begin{bmatrix} 7 \\ 8 \\ 25 \end{bmatrix}, A = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}, \begin{array}{l} i_1 = -5,33\text{mA} \\ i_2 = 2,67\text{mA} \\ i_3 = 1,5\text{mA} \end{array}$$



answer

$$* V_o = R \cdot i \quad R = 25k \Omega$$


$$V_o = 25k \cdot \frac{1}{2} \text{mA}$$
$$i = i_3 - 1\text{mA}$$
$$= 1,5 - 1$$
$$= 0,5\text{mA}$$

$$V_o = 12,5V$$

Question 4.59

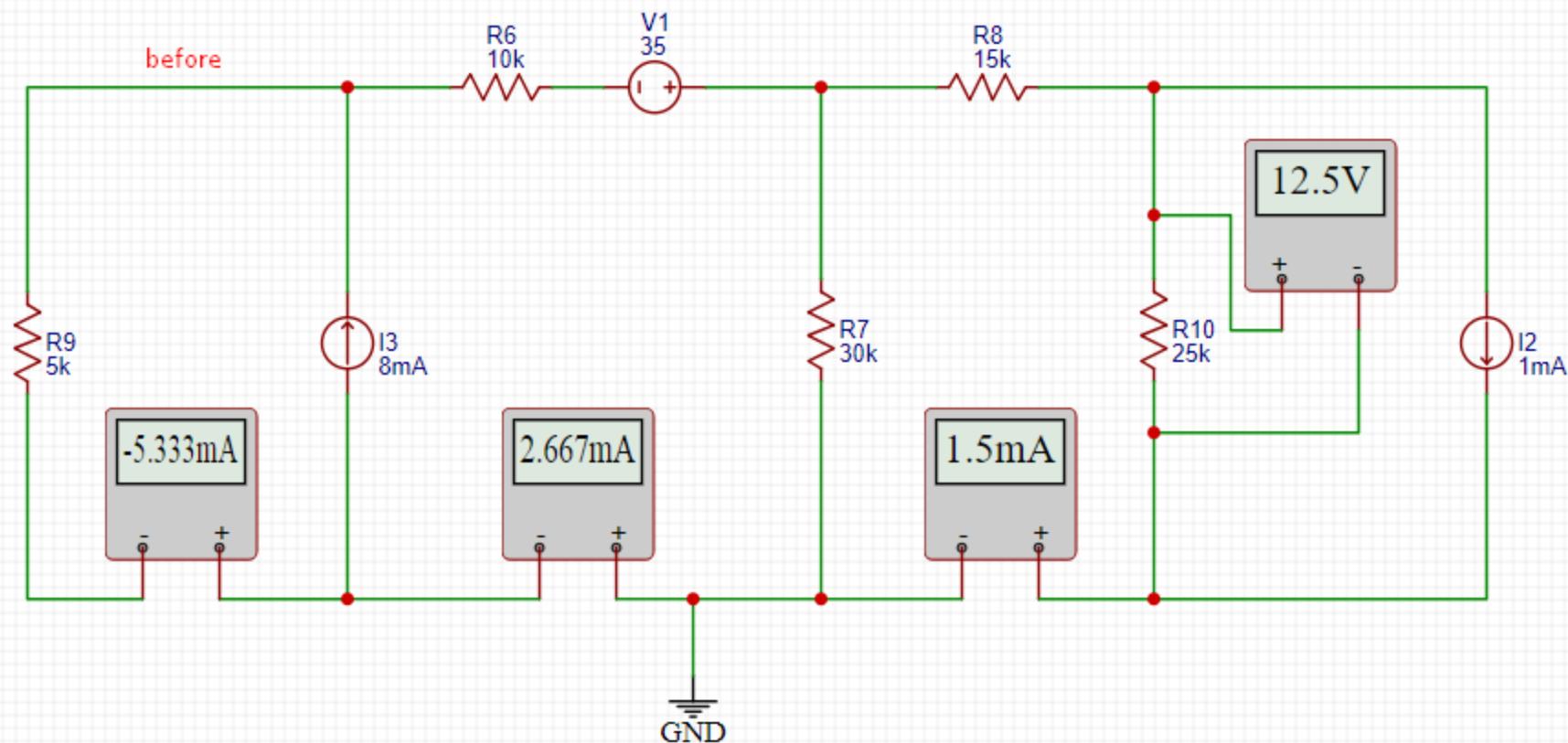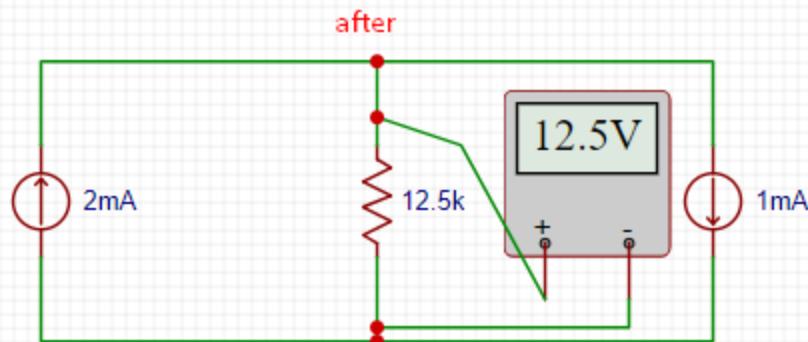

4.64

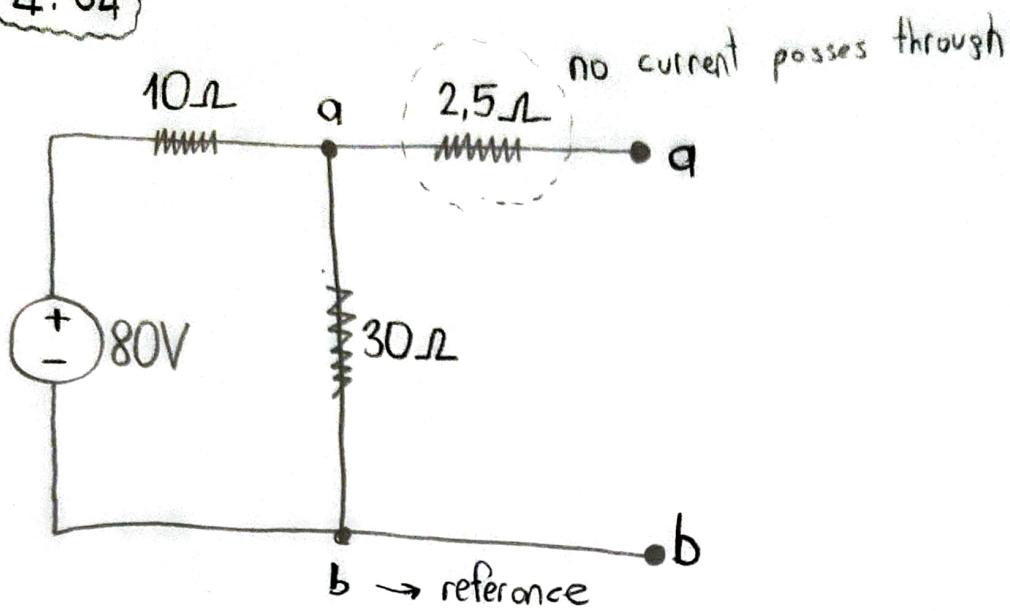

for node a (KCL)


$$* \frac{V_a - 80}{10} + \frac{V_a}{30} = 0 \quad (\times 30)$$

$$3V_a - 240 + V_a = 0$$


$$4V_a = 240$$

$$V_a = 60V$$

Question 4.64

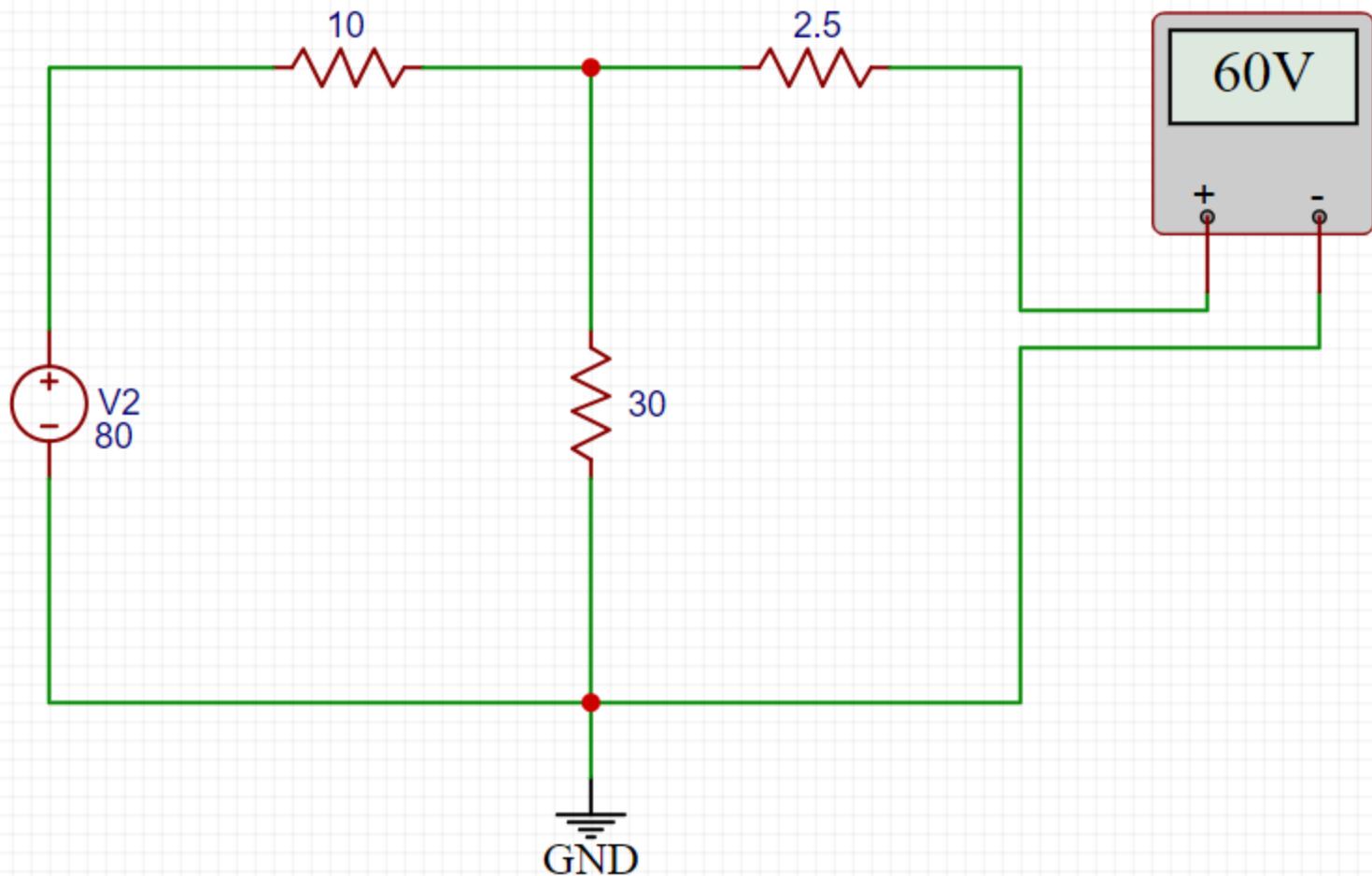

4.78

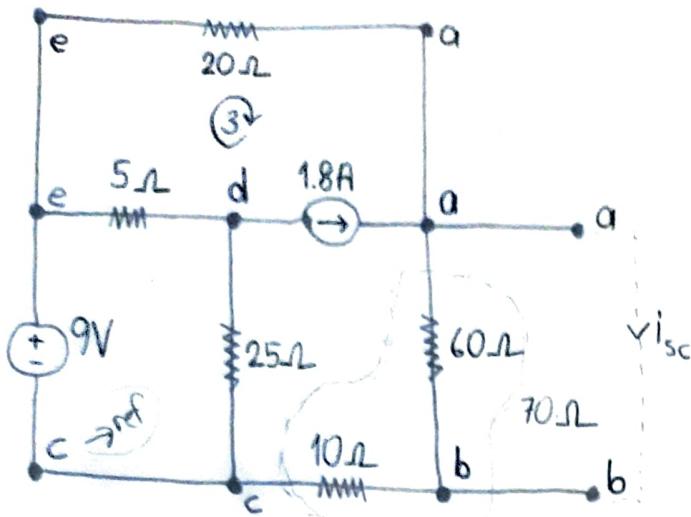

a)

for node a (KCL)

$$*\frac{V_a}{70} + \frac{V_a - 9}{20} - 1.8 = 0 \quad (\times 140)$$

$$2V_a + 7V_a - 63 - 252 = 0$$

$$9V_a = 315, \quad V_a = 35V$$

$$\underline{V_{Th}}$$

$$* V_{Th} = V_a - V_b$$

$$*\frac{30}{10} \quad \frac{35}{x} \quad \left. \right\} x = 5V = V_b$$

$$* V_{Th} = 35 - 5 = \underline{\underline{30V}}$$

$$\underline{i_{sc}}$$

\* no current flow through  $60\Omega$ .

for node a

$$\frac{V_a - 9}{20} + \frac{V_a}{10} - 1.8 = 0 \quad (\times 20)$$

$$V_a - 9 + 2V_a - 36 = 0$$

$$3V_a = 45$$

$$V_a = 15V$$

$$i_{sc} = \frac{V_a}{10}$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$

$$i_{sc} = 1.5A$$


$$R_{Th} = 20\Omega$$



b) after we remove independent sources  $10\Omega$  resistance and  $20\Omega$  resistance becomes connected in series.  $60\Omega$  resistance stays parallel to them. So  $R_{Th}$  is:

$$\begin{aligned} R_{Th} &= (20+10//60) \\ &= \frac{30 \cdot 60}{30+60} \\ &= \frac{30 \cdot 60}{90} = 20\Omega \end{aligned}$$


$$R_{Th} = 20\Omega$$

Question 4.78

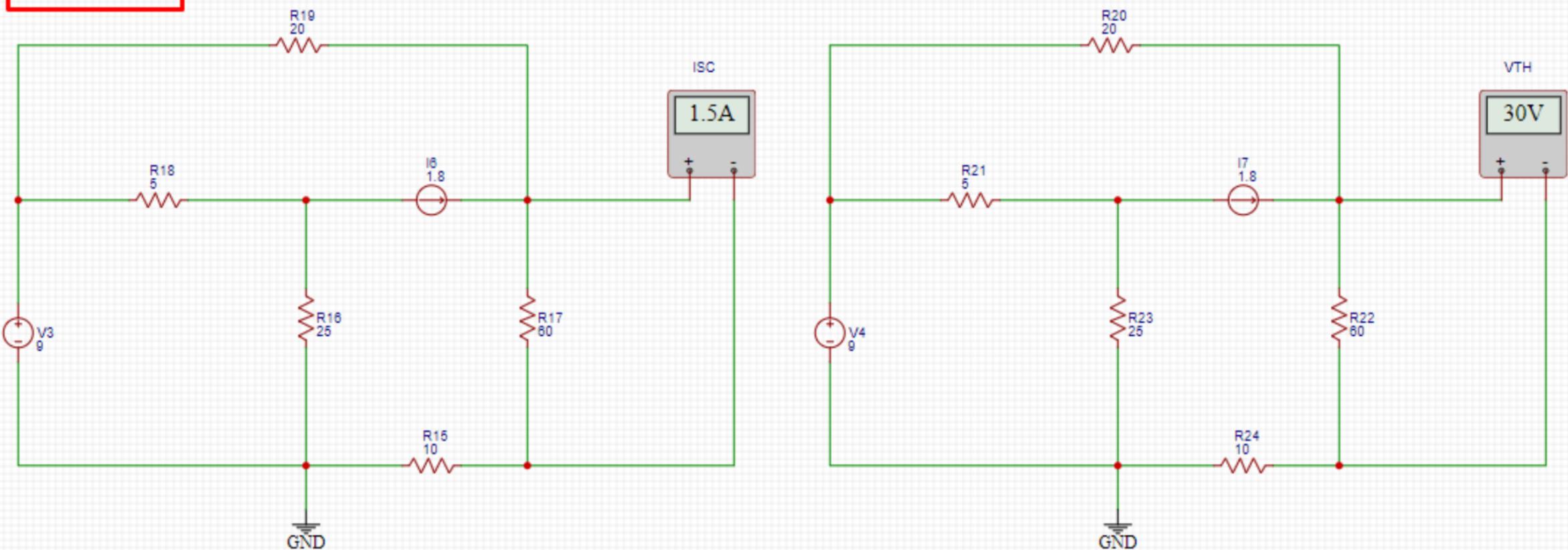

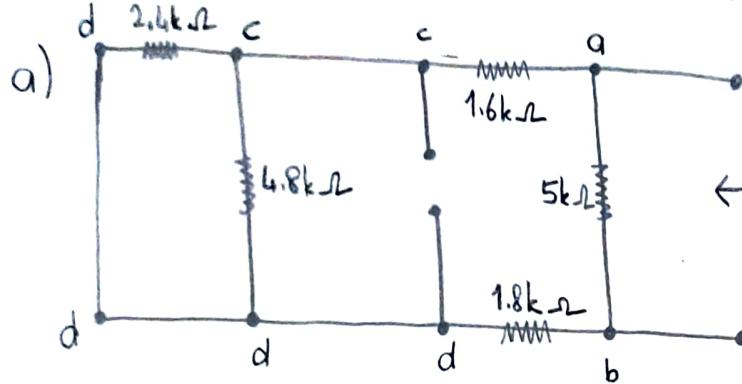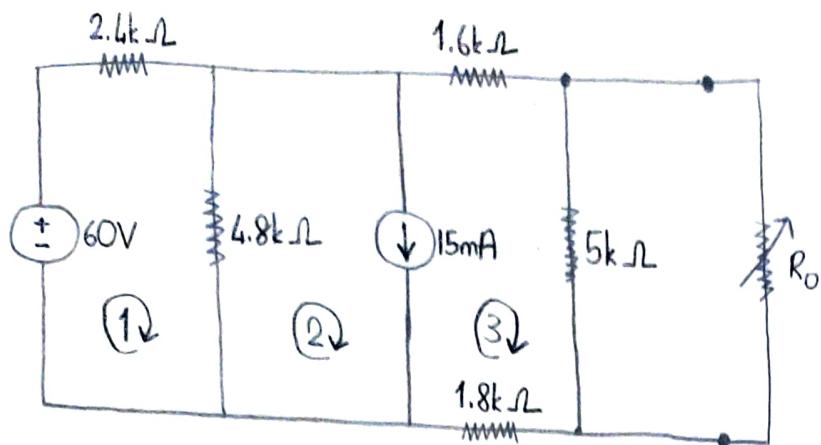

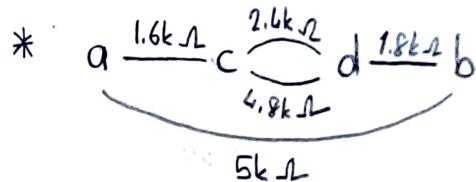\* To get maximum value of  $R_o$  we need to get  $R_{Th}$ .



$$* R_{Th} = \frac{1.6k\Omega \cdot 1.8k\Omega}{4.8k\Omega + 5k\Omega} = \frac{5k \cdot 5k}{10k} = 2.5k\Omega$$

$$P_{max} = 2.5k \cdot (1.6mA)^2$$

$$P_{max} = 6.4 \text{ mW}$$

b) for mesh 1

$$* -60 + 2.4k(i_1) + 4.8k(i_1 - i_2) = 0$$

$$7.2k(i_1) - 4.8k(i_2) = 60, \dots \textcircled{1}$$

for supermesh 2-3

$$* 4.8k(i_2 - i_1) + 1.6k(i_3) + 5k(i_3) + 1.8k(i_3) = 0$$

$$-4.8k(i_1) + 4.8k(i_2) + 8.4k(i_3) = 0, \dots \textcircled{2}$$



for 15mA source

$$* i_2 - i_3 = 15mA = 0.015A$$


matrix

$$x = \begin{bmatrix} 7.2k & -4.8k & 0 \\ -4.8k & 4.8k & +8.4k \\ 0 & 1k & -1k \end{bmatrix}, y = \begin{bmatrix} 60 \\ 0 \\ 15 \end{bmatrix}, A = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} \Rightarrow \begin{array}{l} i_1 = 19.4mA \\ i_2 = 16.6mA \\ i_3 = 1.6mA \end{array} \quad \left| \begin{array}{l} V_{Th} = i_3 \cdot R \\ V_{Th} = 1.6mA \cdot 5k\Omega \\ V_{Th} = 8V \end{array} \right.$$

Question 4.82

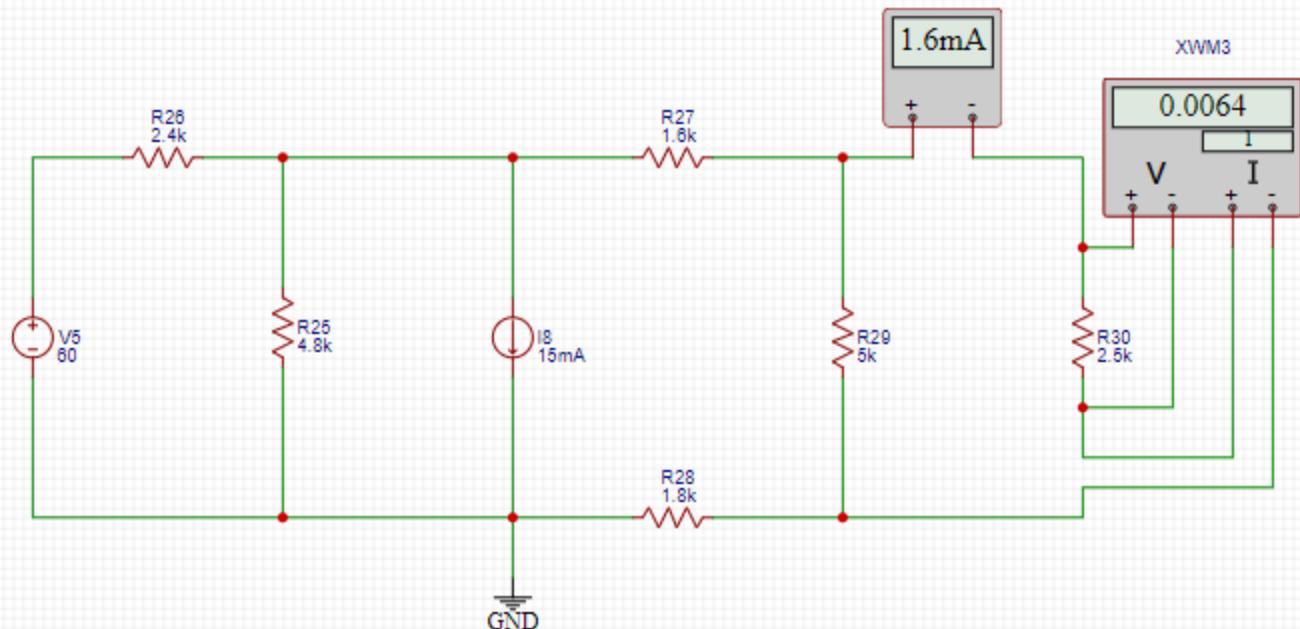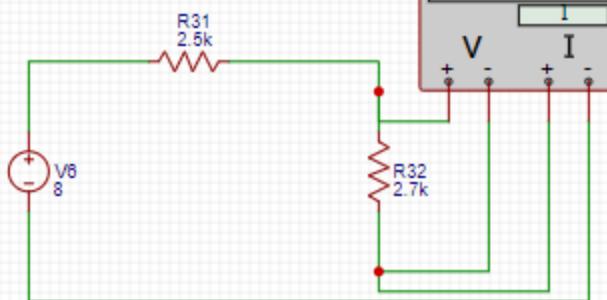


4.95

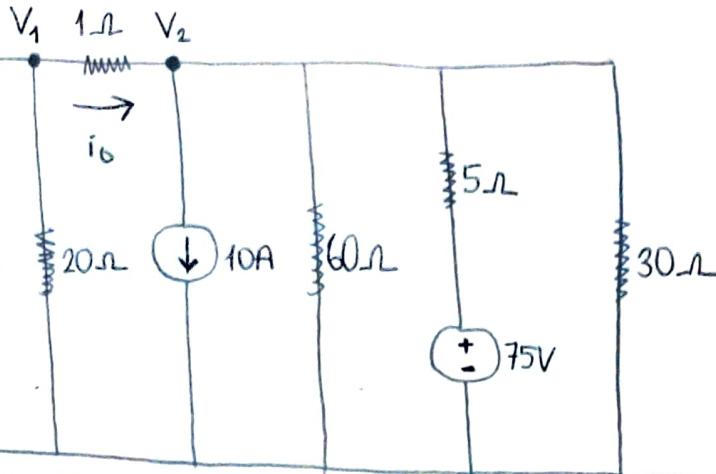

$$\begin{aligned} * i_o &= i_o' + i_o'' + i_o''' \\ &= -2.4 + 1.6 + 4.8 \end{aligned}$$

$$* i_o = 4A$$

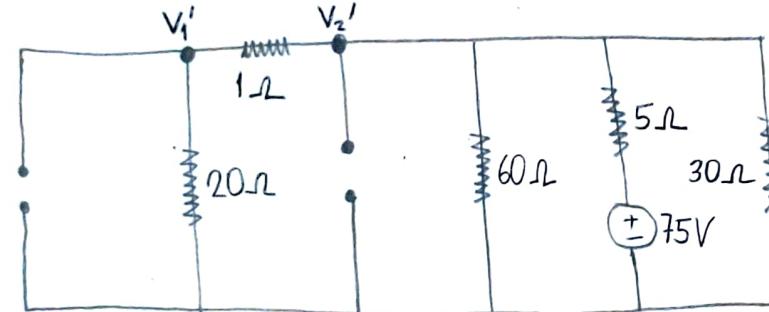\* First I'll remove 6A source and 10A source



$$\begin{aligned} * V_1' &= 48V \\ V_2' &= 50.4V \end{aligned}$$

$$* i_o' = (V_1' - V_2') / R = -2.4A_{\parallel}$$

for node  $V_1'$

$$* \frac{V_1' - V_2'}{1} + \frac{V_1'}{20} = 0$$

$$* 21V_1' - 20V_2' = 0 \dots (1)$$


for node  $V_2'$

$$* \frac{V_2' - V_1'}{1} + \frac{V_2'}{60} + \frac{V_2' - 75}{5} + \frac{V_2'}{30} = 0$$

$$* 60V_2' - 60V_1' + V_2' + 12V_2' - 900 + 2V_2^2 = 0$$

$$* -60V_1' + 75V_2' = 900 \dots (2)$$

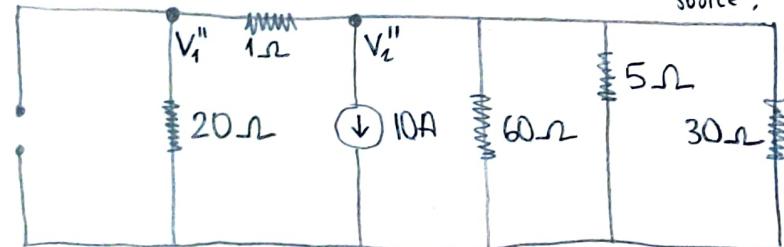\* Second I'll remove 6A current source and 75V source



$$\begin{aligned} * V_1'' &= -32V \\ V_2'' &= -33.6V \end{aligned}$$

$$* i_o'' = (V_1'' - V_2'') / R = 1.6A_{\parallel}$$

for Node  $V_1''$

$$* \frac{V_1'' - V_2''}{1} + \frac{V_1''}{20} = 0 \Rightarrow 21V_1'' - 20V_2'' = 0 \dots (1)$$


for node  $V_2''$

$$* \frac{V_2'' - V_1''}{1} + 10 + \frac{V_2''}{60} + \frac{V_2''}{5} + \frac{V_2''}{30} = 0$$

$$* 60V_2'' - 60V_1'' + 600 + V_2'' + 12V_2'' + 2V_2^2 = 0$$

$$* -60V_1'' + 75V_2'' = -600 \dots (2)$$

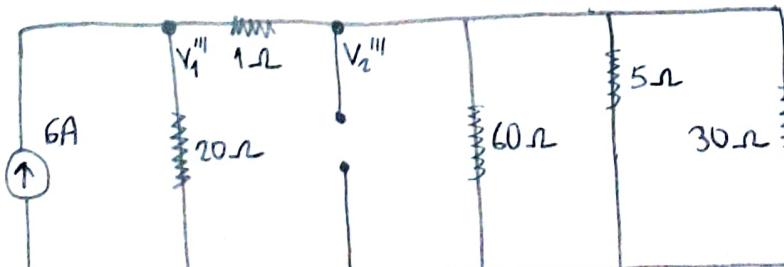\* Lastly I'll remove 10A source and 75V source



$$* V_1''' = 24V$$

$$* i_o''' = (V_1''' - V_2''') / R$$

$$V_2''' = 19.2V \quad = 4.8A_{\parallel}$$

for node  $V_1'''$

$$* \frac{V_1''' - V_2'''}{1} + \frac{V_1'''}{20} - 6 = 0 \quad (\times 20)$$

$$* 21V_1''' - 20V_2''' = 120 \dots (1)$$

for node  $V_2'''$

$$* \frac{V_2''' - V_1'''}{1} + \frac{V_2'''}{60} + \frac{V_2'''}{5} + \frac{V_2'''}{30} = 0 \quad (\times 60)$$

$$* -60V_1''' + 75V_2''' = 0 \dots (2)$$

