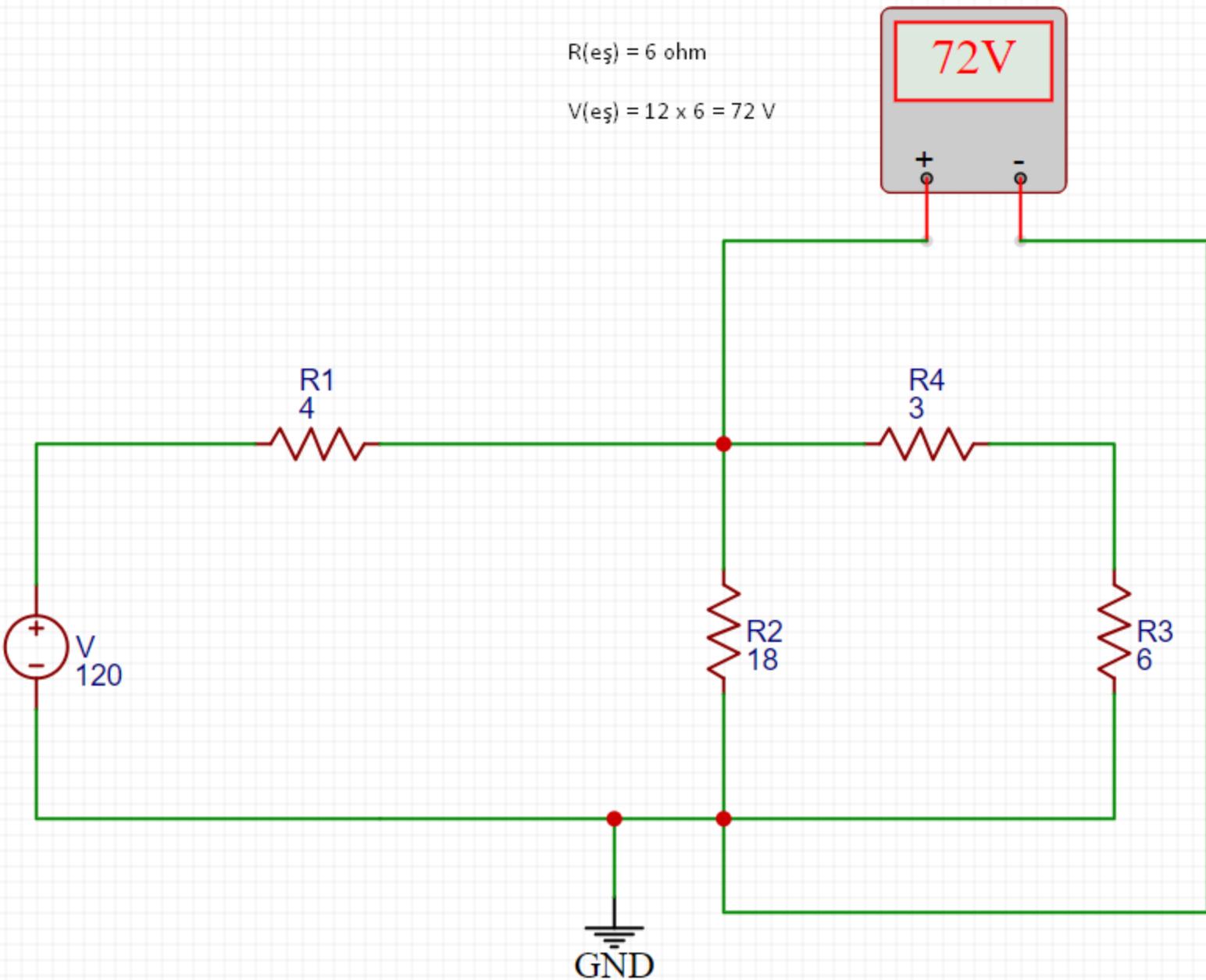


31)

XMM1




31)

IX

i_x değeri = 11.999A


i_y değeri = ?

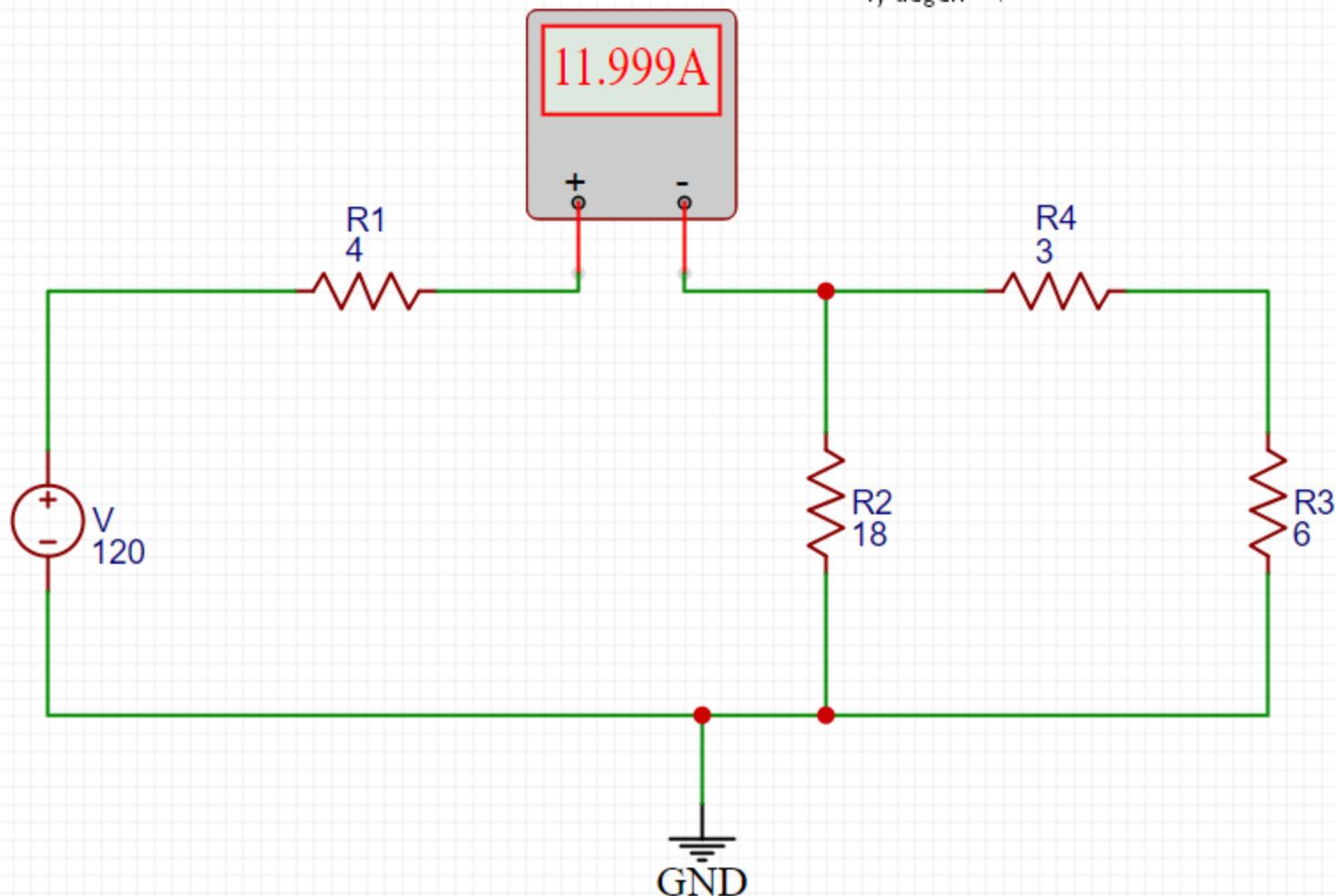


31)

$$i_x = 11.999 \text{ A}$$
$$i_y = 11.999 \text{ A}$$

$$i_x == i_y$$

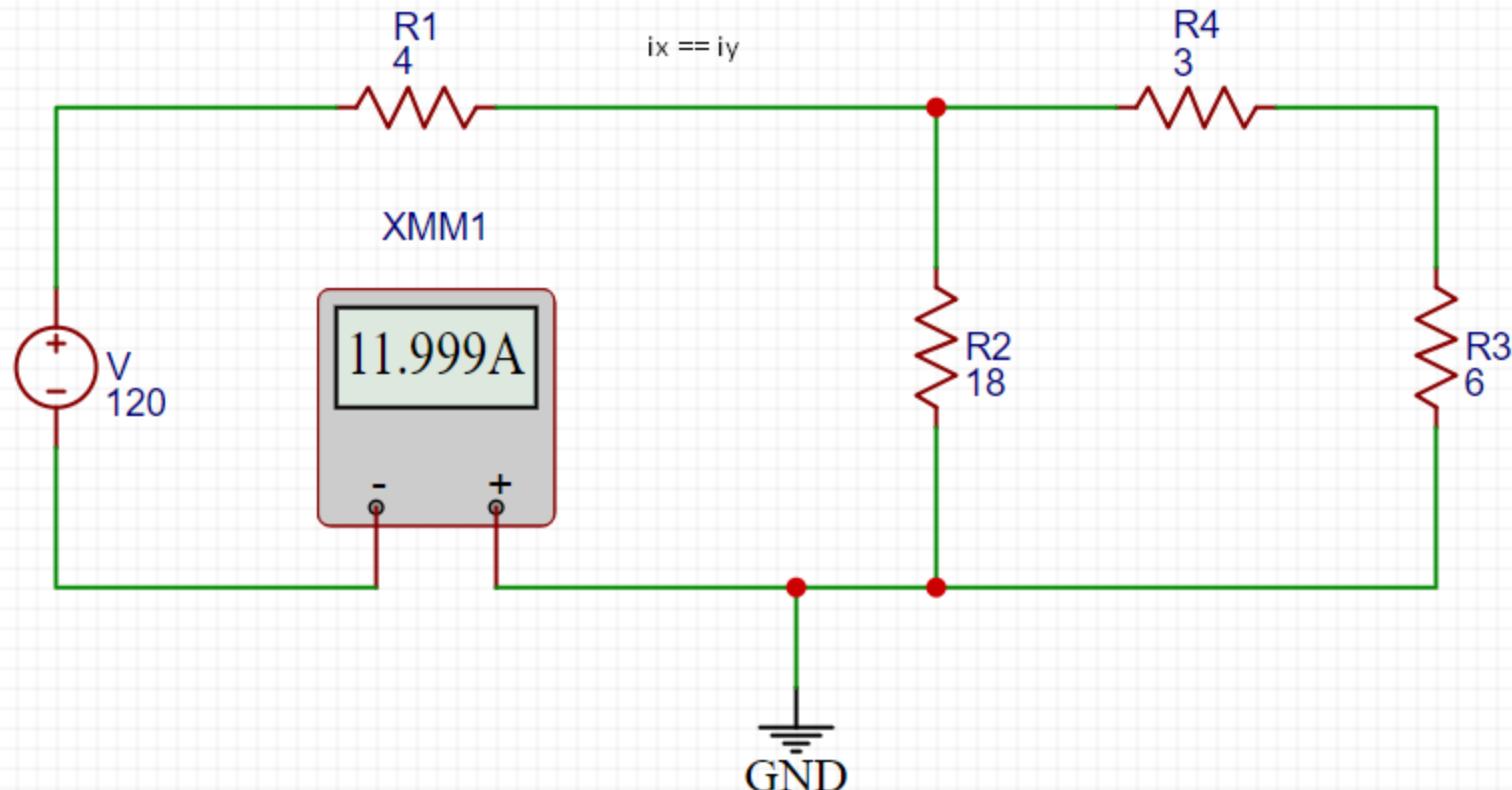

• 3.1

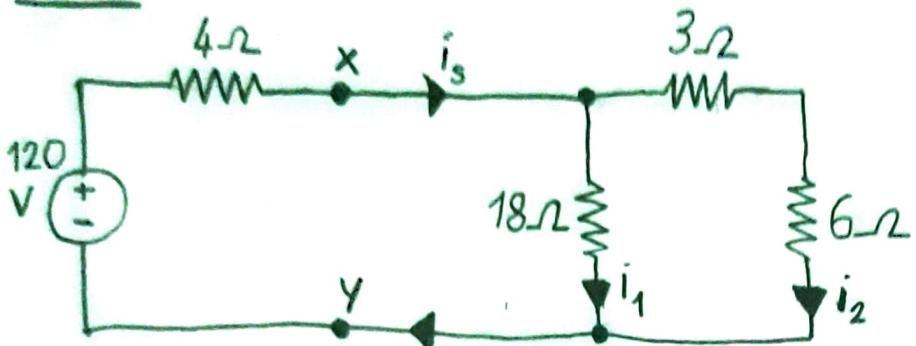

$$R_{es} = 10\Omega$$

$$V_{es} = 120V$$

$$i_s = 12A$$


$$i_1 = 4A \quad i_2 = 8A$$

a) current flows through x and y junctions must be equal according to K.C.L.


$$i_x = i_s = \frac{V_{es}}{R_{es}} = \frac{120}{10} = 12A$$

$$i_x = i_y$$

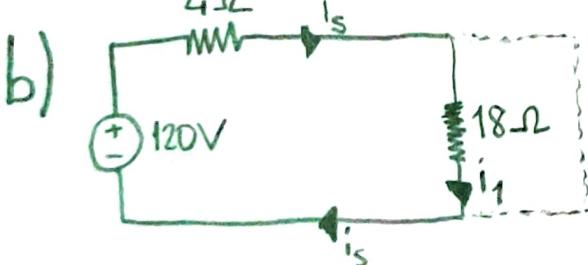
$$i_y = i_1 + i_2 = \frac{V_{xy}}{R_1} + \frac{V_{xy}}{R_2} = \frac{72}{18} + \frac{72}{9} = 12A$$


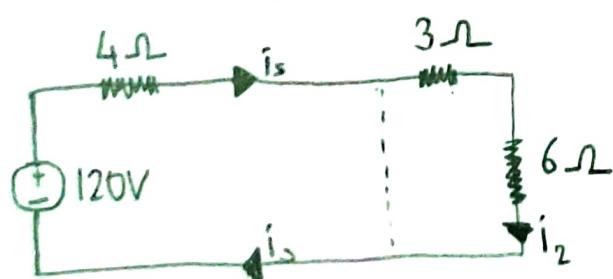
$$\begin{aligned} 120V &= i_s \cdot R_s + i_1 \cdot R_1 \\ &= 12 \cdot 4 + 4 \cdot 18 \\ &= 48 + 72 = 120V_{//} \end{aligned}$$


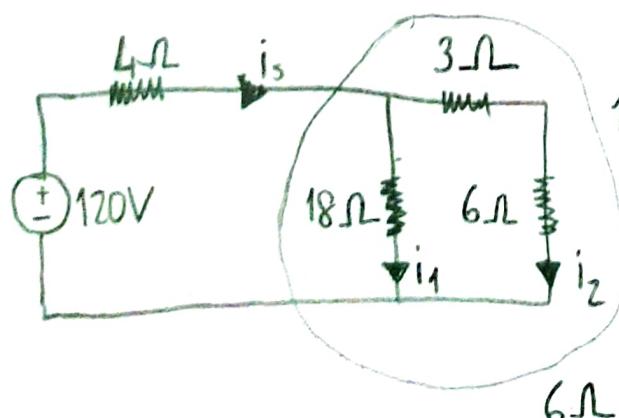
$$\begin{aligned} 120V &= i_s \cdot R_s + i_2 \cdot (R_2 + R_3) \\ &= 12 \cdot 4 + 8 \cdot (3 + 6) \\ &= 48 + 72 = 120V_{//} \end{aligned}$$



$$\begin{aligned} 120V &= i_s \cdot R_s + i_s \cdot R_{es} \\ &= 12 \cdot 4 + 12 \cdot 6 \\ &= 48 + 72 \\ &= 120V_{//} \end{aligned}$$



$$V_s = 120V$$

$$R_s = 10\Omega$$

$$i_s = 12A$$

$$i_1 = 4A \quad i_2 = 8A$$

a) For R_1

$$\begin{aligned} V_1 &= i_s \cdot R_1 \\ &= 12 \cdot 4 \\ &= 48V \end{aligned}$$

$$\begin{aligned} P_1 &= -V_1 \cdot i_s \\ &= -48 \cdot 12 \\ &= -576W \end{aligned}$$

For R_2

$$\begin{aligned} V_2 &= i_1 \cdot R_2 \\ &= 4 \cdot 18 \\ &= 72V \\ P_2 &= -V_2 \cdot i_1 \\ &= -72 \cdot 4 \\ &= -288W \end{aligned}$$

For R_3

$$\begin{aligned} V_3 &= i_2 \cdot R_3 \\ &= 8 \cdot 3 \\ &= 24V \\ P_3 &= -V_3 \cdot i_2 \\ &= -24 \cdot 8 \\ &= -192W \end{aligned}$$

For R_4

$$\begin{aligned} V_4 &= i_2 \cdot R_4 \\ &= 8 \cdot 6 \\ &= 48V \\ P_4 &= -V_4 \cdot i_2 \\ &= -48 \cdot 8 \\ &= -384W \end{aligned}$$

b) $P_s = V_s \cdot i_s$

$$\begin{aligned} &= 120 \cdot 12 \\ &= 1440W \end{aligned}$$

c) $P_s + (P_1 + P_2 + P_3 + P_4) = 0$

$$P_s = -(P_1 + P_2 + P_3 + P_4)$$


$$1440 = -(-576 - 288 - 192 - 384)$$

$$1440 = -(-1440)$$


$$1440 = 1440 //$$

3.2


VOLTMETER

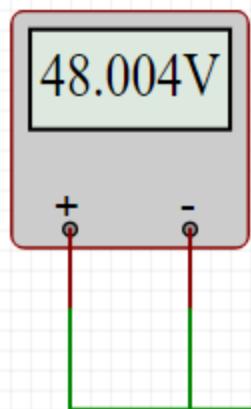


AMPERMETER

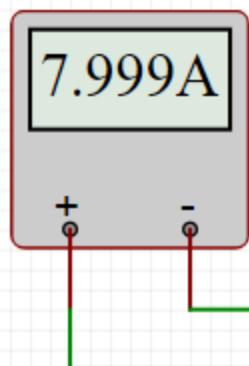


For R4

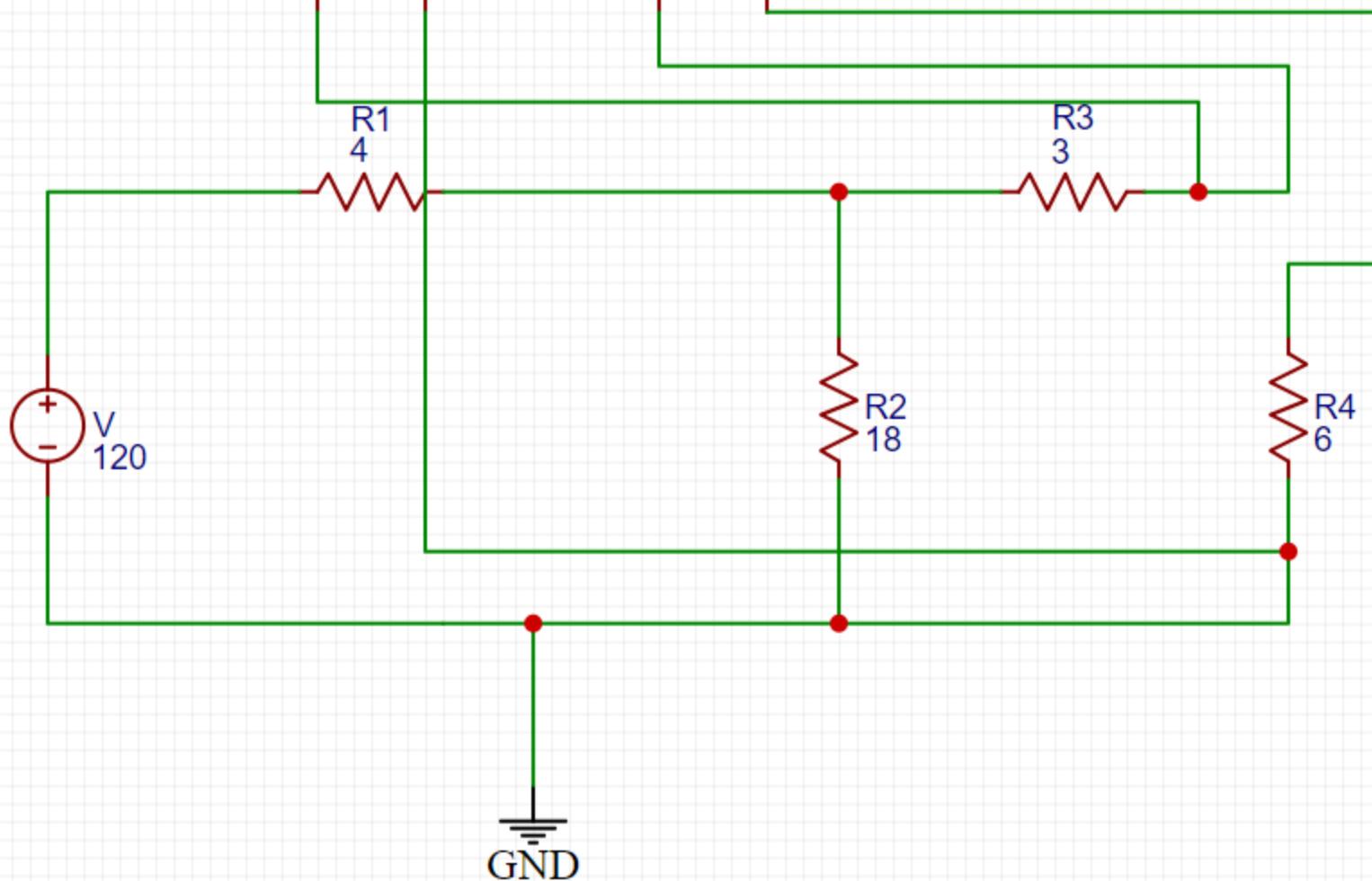

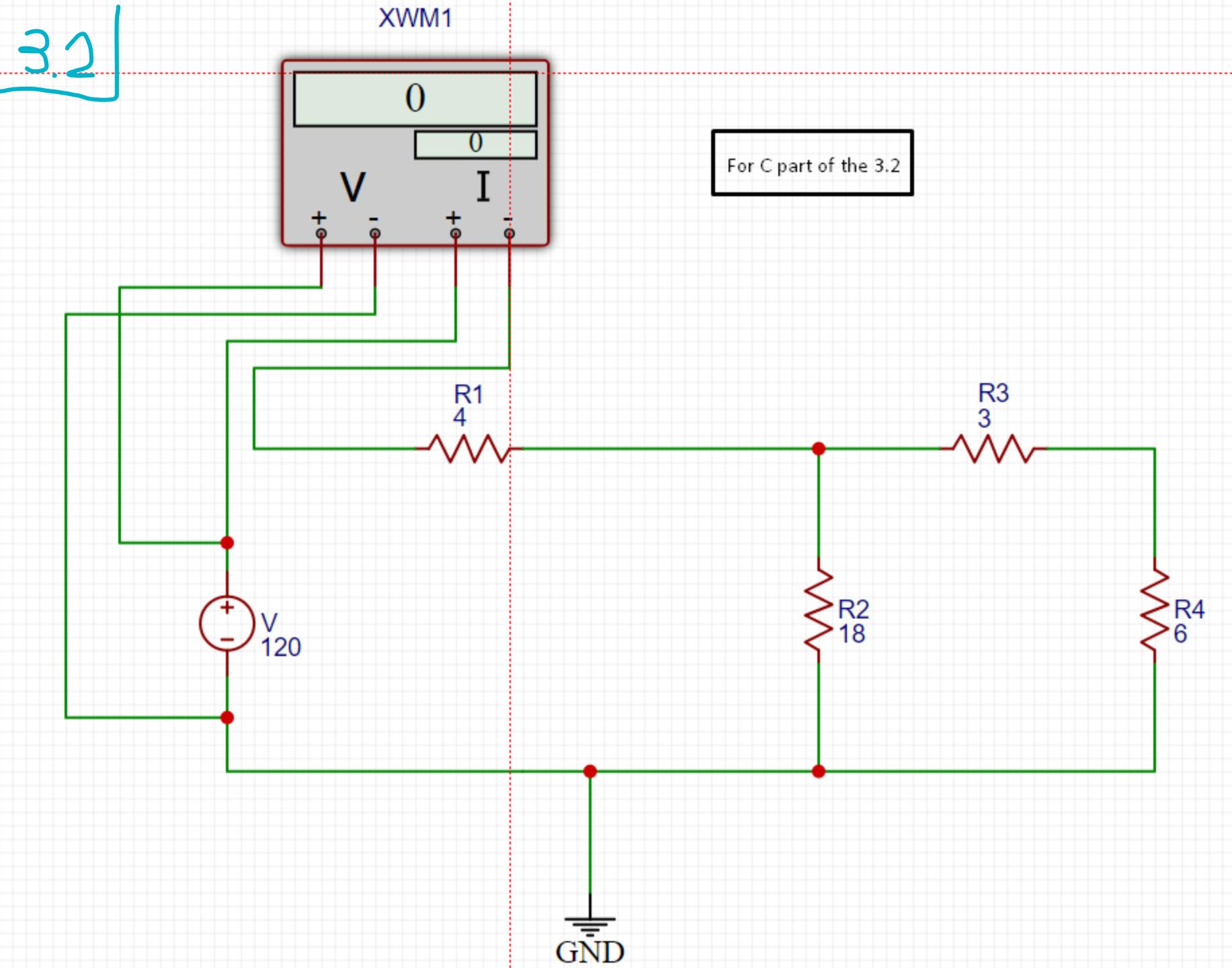

3.2


VOLTMETER

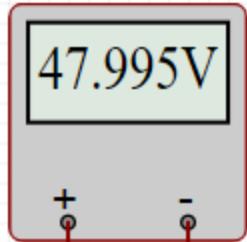

AMPERMETER




FOR R1

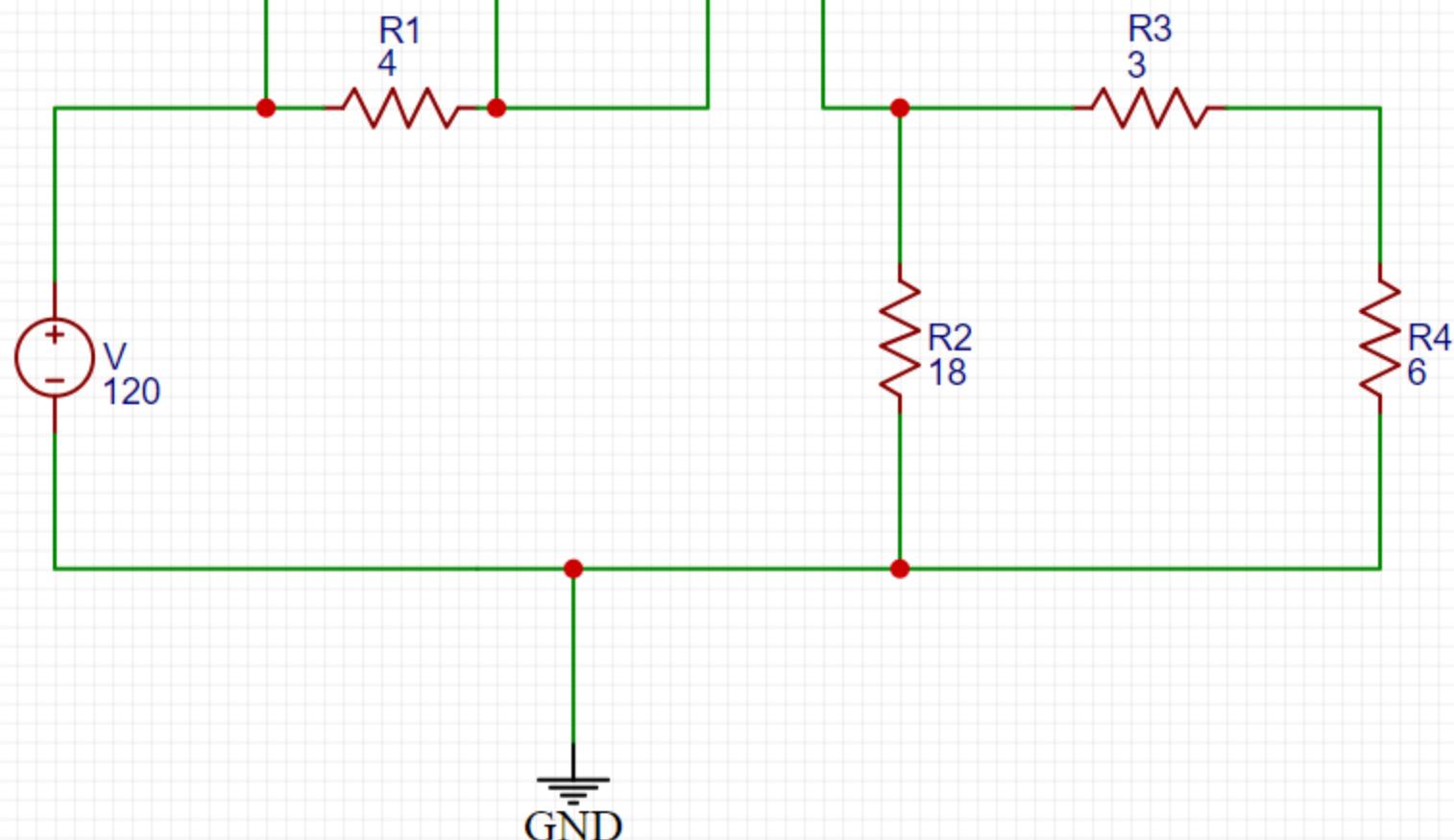


32


VOLTMETER

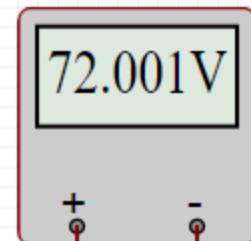

AMPERMETER

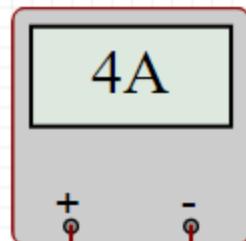


For R2

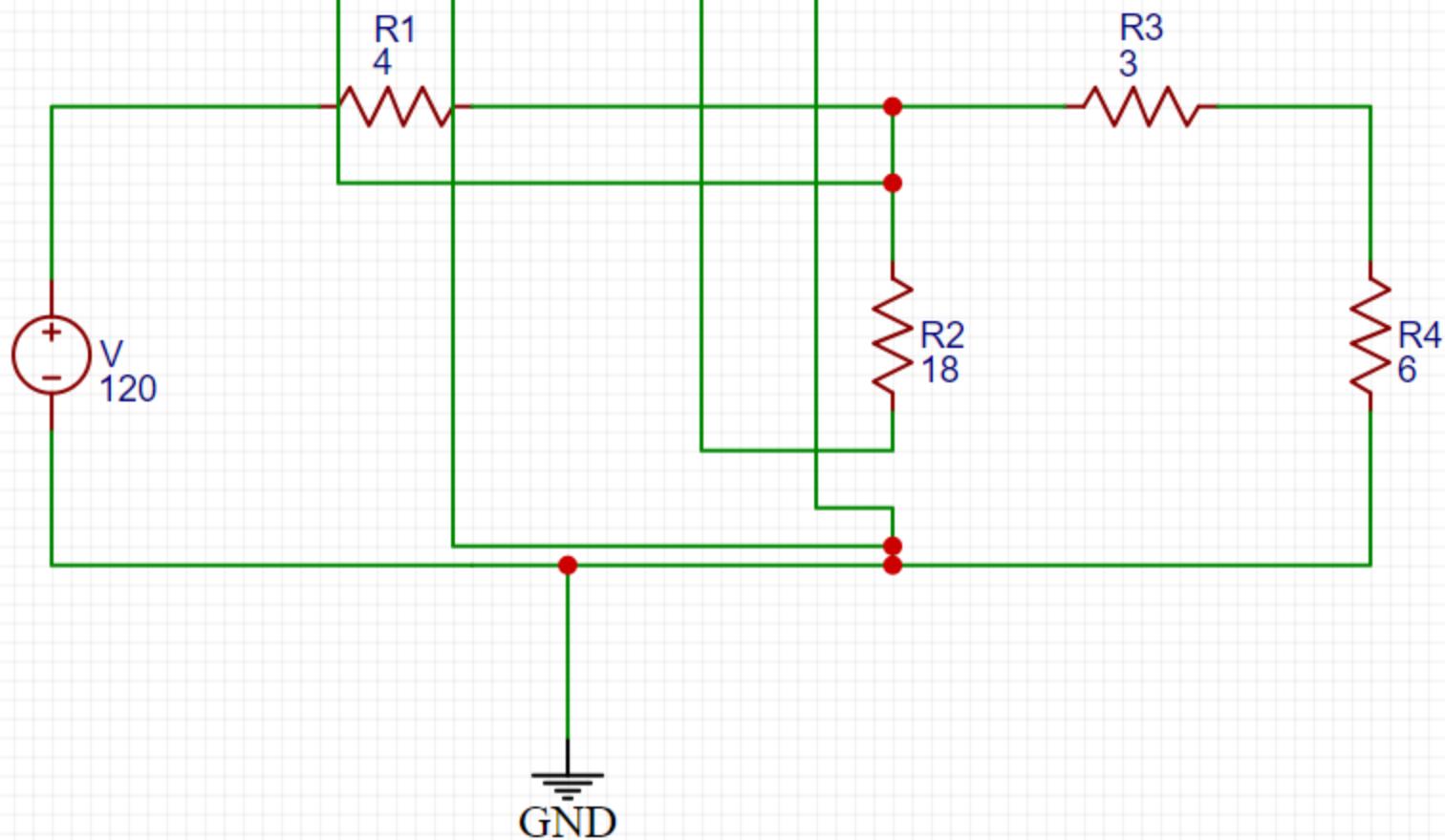

32


VOLTMETER

AMPERMETER

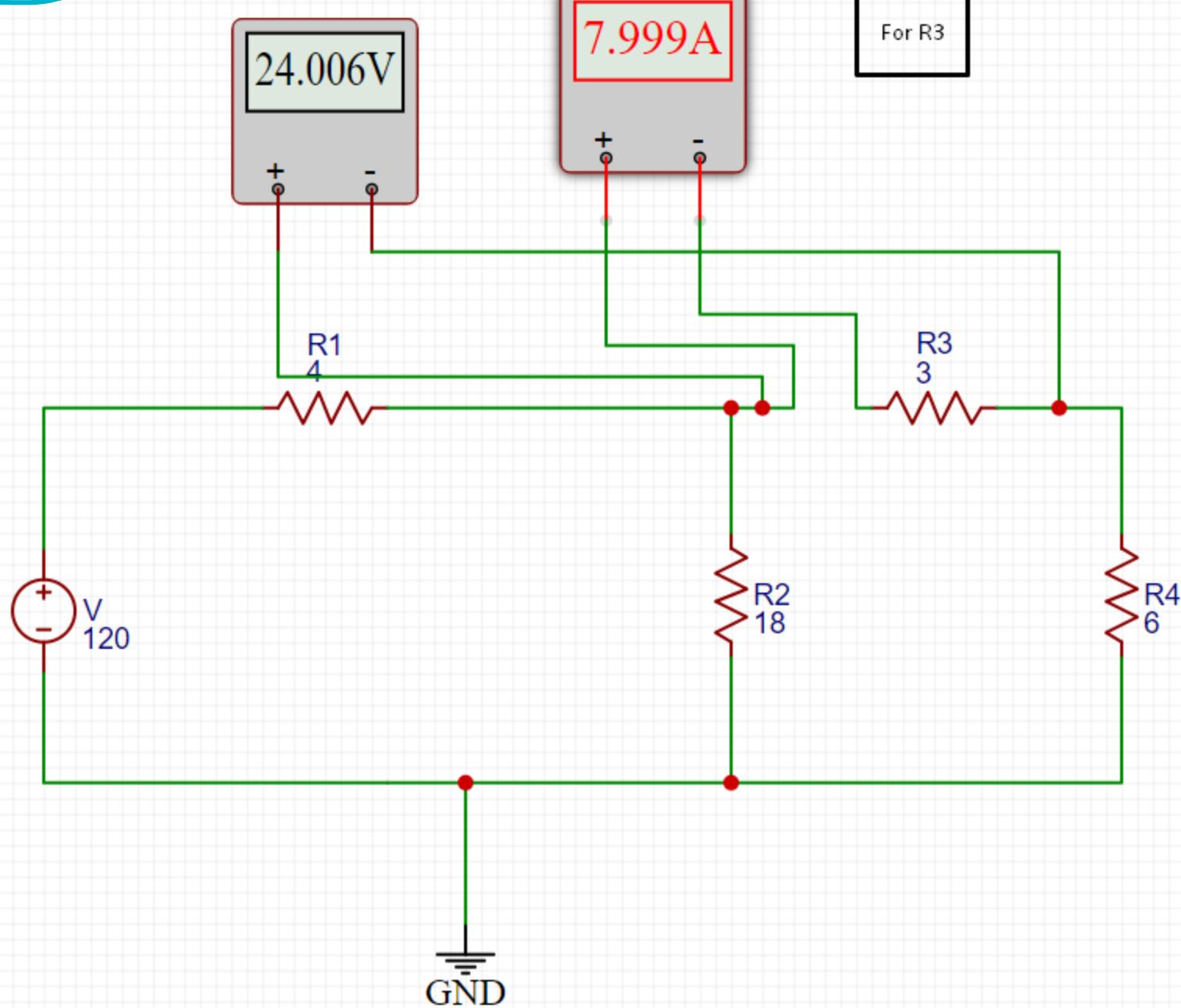


3.2


VOLTMETER

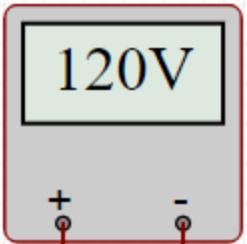

AMPERMETER

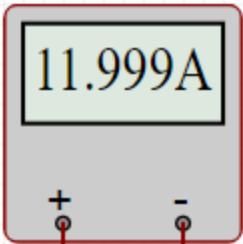

For 120V

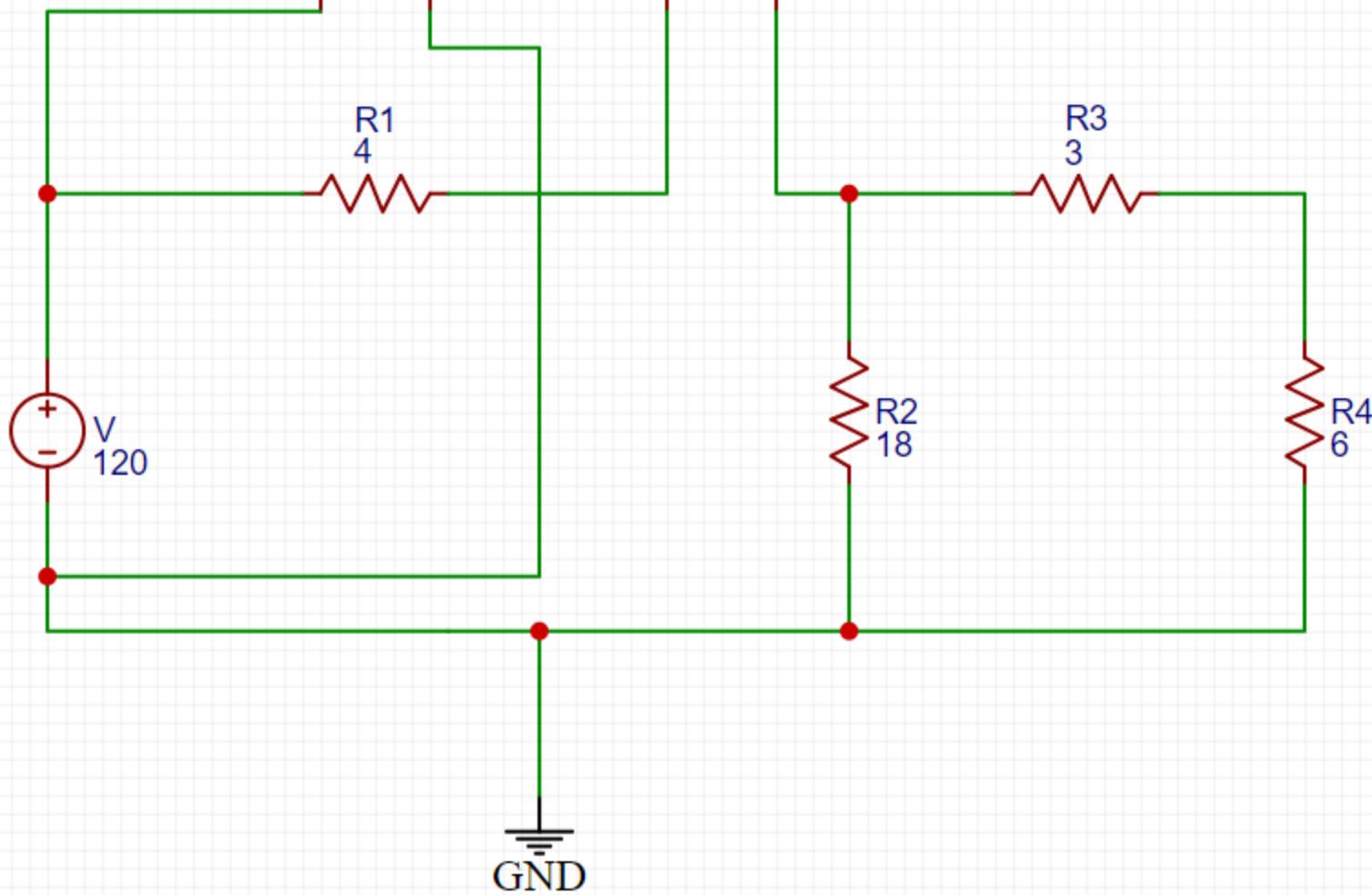
$$P = 120 * 12$$
$$p = 1400W$$



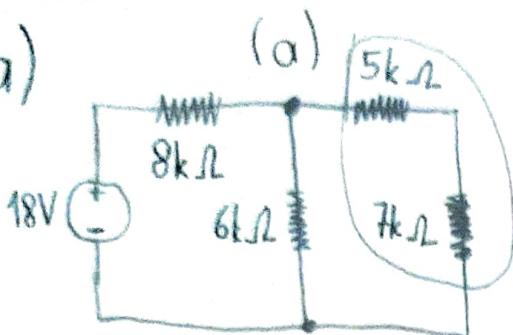
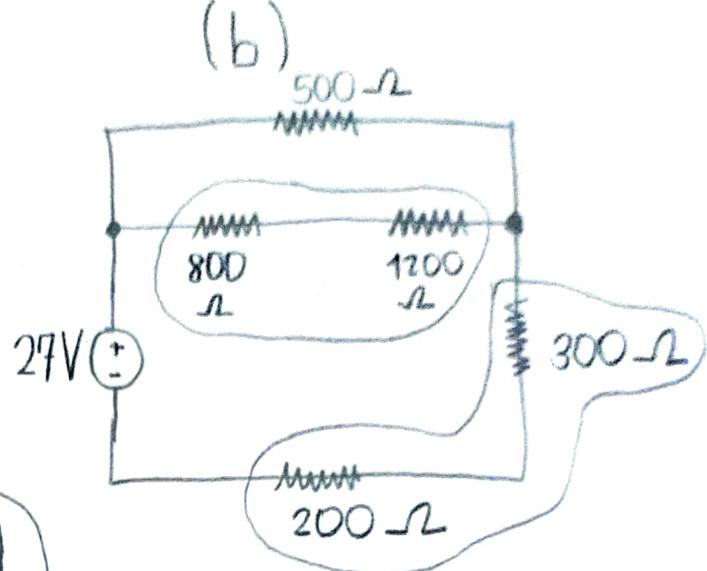
GEEK DAY

• 3.3


a)




(b)




(c)

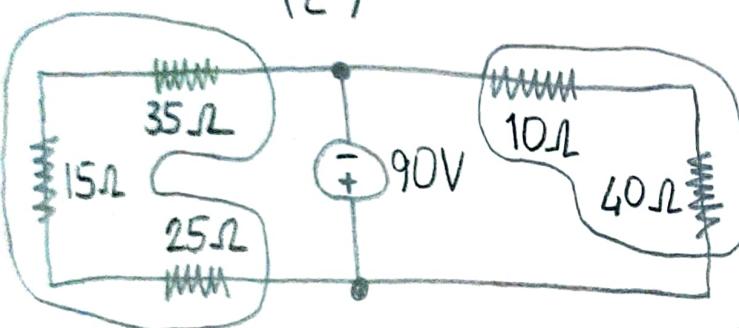


(d)

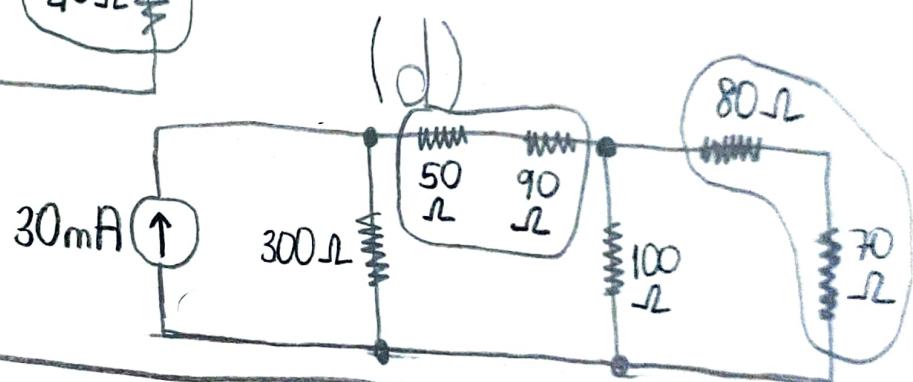


b)

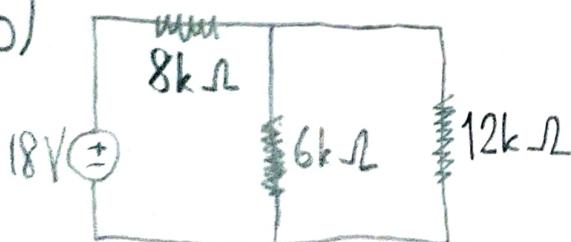


(b)

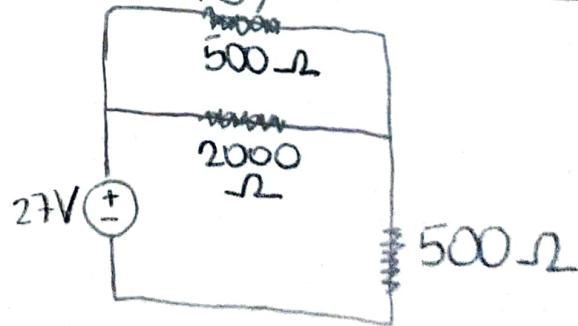

(c)

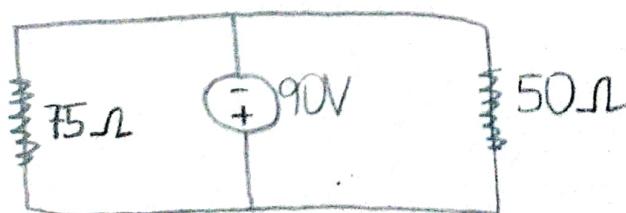


(d)

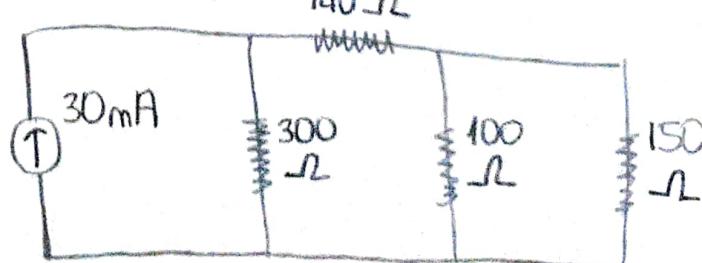

• 3.4


a)

(a)

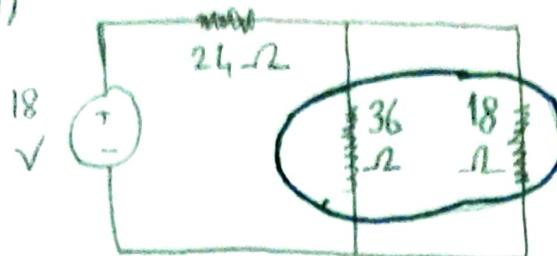


seri → pink
parallel → blue


(b)

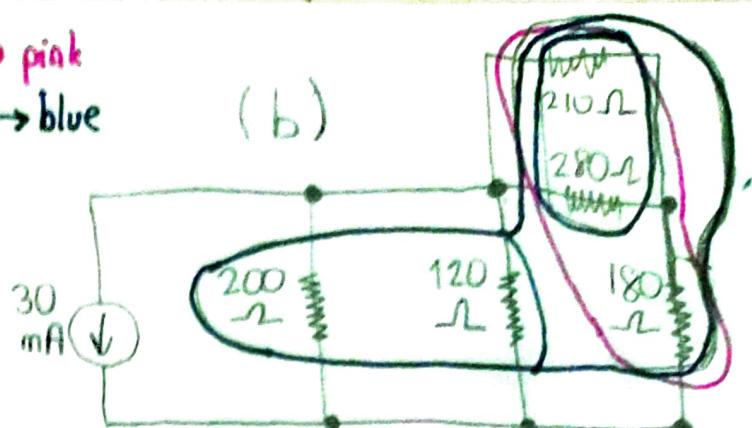

(c)

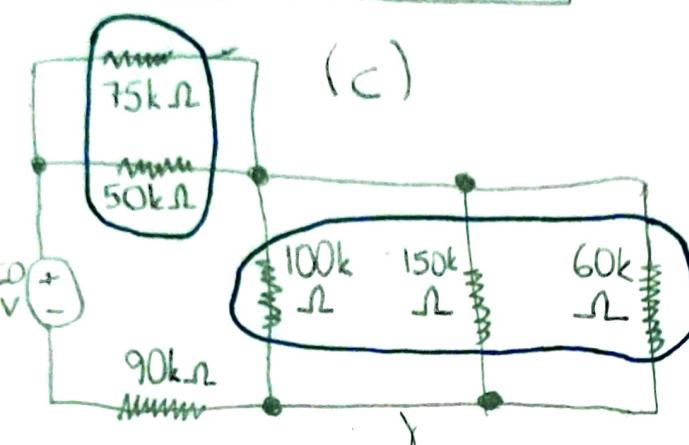

(d)

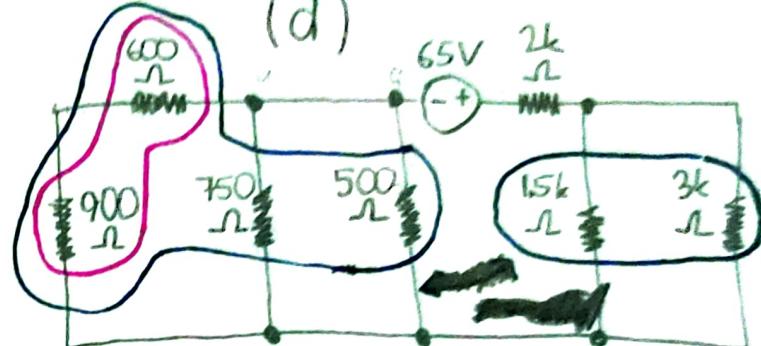

b)

(a)




$$\frac{1}{R} = \frac{1}{36} + \frac{1}{18}$$

$$\frac{1}{R} = \frac{3}{36}$$

$$R = 12\Omega$$

(b)

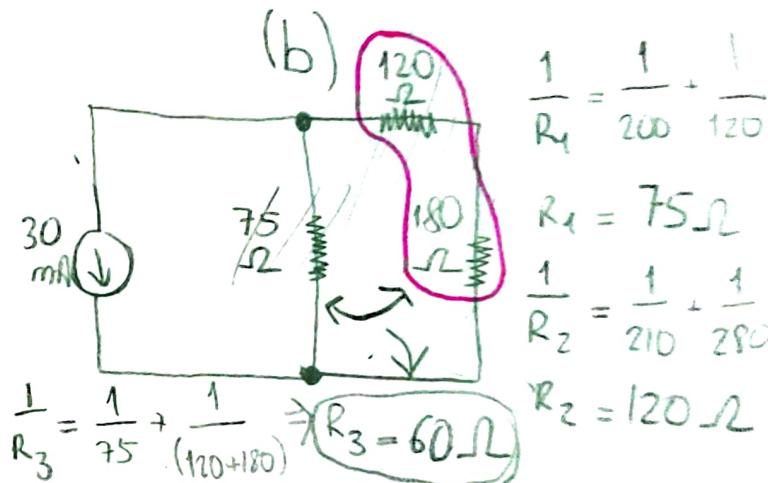


$$\frac{1}{R_1} = \frac{1}{200} + \frac{1}{120}$$

$$R_1 = 75\Omega$$

$$\frac{1}{R_2} = \frac{1}{210} + \frac{1}{280}$$

$$R_2 = 120\Omega$$

(c)

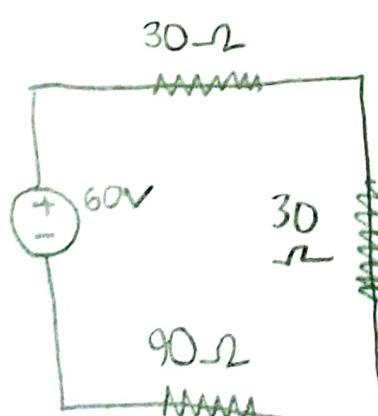


$$\frac{1}{R_1} = \frac{1}{30} + \frac{1}{50}$$

$$R_1 = 30\Omega$$

$$\frac{1}{R_2} = \frac{1}{100} + \frac{1}{150} + \frac{1}{60}$$

$$R_2 = 30\Omega$$

(d)

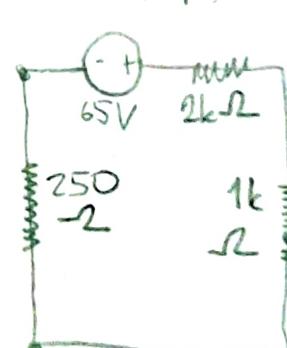

$$\frac{1}{R_1} = \frac{1}{15k} + \frac{1}{3k}$$

$$R_1 = 1k\Omega$$

$$\frac{1}{R_2} = \frac{1}{(900+600)} + \frac{1}{750} + \frac{1}{500}$$

$$\frac{1}{R_2} = \frac{6}{1500}$$


$$R_2 = 250\Omega$$



GEEK DAY

• 3.5

a)

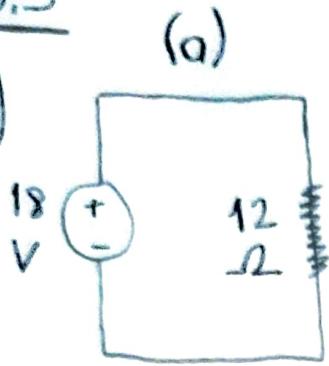


$$\rightarrow R_1 = 5 + 7 \\ = 12 \Omega$$

$$\rightarrow \frac{1}{R_2} = \frac{1}{6} + \frac{1}{12}$$

$$R_2 = 4 \Omega$$

$$\rightarrow R_{\text{res}} = 4 + 8 \\ = 12 \Omega \parallel$$

(b)

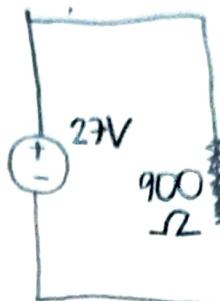


$$\rightarrow R_1 = 800 + 1200 \\ = 2000 \Omega$$

$$\rightarrow \frac{1}{R_2} = \frac{1}{500} + \frac{1}{2000}$$

$$R_2 = 400 \Omega$$

$$\rightarrow R_{\text{res}} = 400 + 300 + 200 \\ = 900 \Omega \parallel$$

(c)

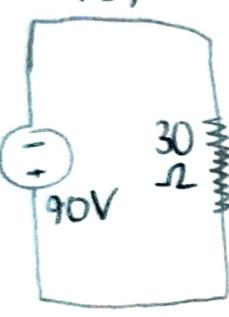


$$\rightarrow R_1 = 35 + 15 + 25 \\ = 75 \Omega$$

$$\rightarrow R_2 = 10 + 60 \\ = 50 \Omega$$

$$\rightarrow \frac{1}{R_{\text{res}}} = \frac{1}{50} + \frac{1}{75}$$

$$R_{\text{res}} = 30 \Omega \parallel$$

(d)

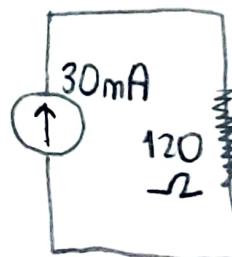

$$\rightarrow R_1 = 80 + 70 = 150 \Omega$$

$$\rightarrow \frac{1}{R_2} = \frac{1}{150} + \frac{1}{100}$$

$$R_2 = 60 \Omega$$

$$\rightarrow R_3 = 60 + 50 + 90 = 200$$

$$\rightarrow \frac{1}{R_{\text{res}}} = \frac{1}{200} + \frac{1}{300}$$

b) For (a)

$$i_a = \frac{V_a}{R_a} = \frac{18}{12} = 1.5A$$

$$P_a = V_a \cdot i_a \\ = 18 \cdot (1.5A) \\ = 27W \parallel$$

For (d)

$$V_d = i_d \cdot R_d = (0.030) \cdot 120 \\ = 3.6V$$

$$P_d = V_d \cdot i_d = (3.6) \cdot (0.030) = 0.108W \parallel$$

For (b)

$$i_b = \frac{V_b}{R_b} = \frac{27}{900}$$

$$P_b = V_b \cdot i_b \\ = \frac{27 \cdot 27}{900}$$


$$= 0.81W \parallel$$

For (c)

$$i_c = \frac{V_c}{R_c} = \frac{90}{30} = 3A$$

$$P_c = V_c \cdot i_c \\ = 90 \cdot 3 \\ = 270W \parallel$$

• 3.8

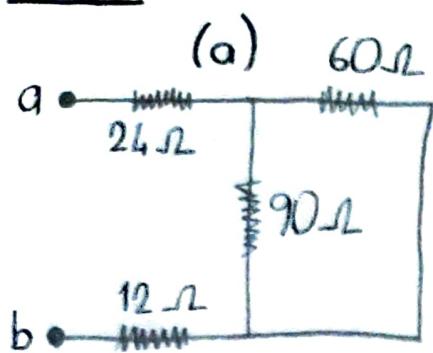


$$\rightarrow \frac{1}{R_1} = \frac{1}{60} + \frac{1}{90}$$

$$R_1 = 36 \Omega$$

$$\rightarrow R_{ab} = 24 + 36 + 12 \\ = 72 \parallel$$

(b)

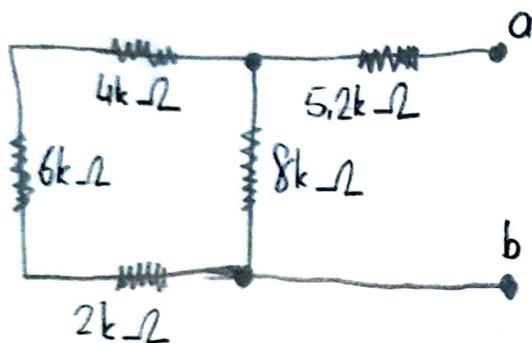


$$\rightarrow R_1 = 4k + 6k + 2k \\ = 12k \Omega$$

$$\rightarrow \frac{1}{R_2} = \frac{1}{12k} + \frac{1}{8k}$$

$$R_2 = \frac{24}{5} k \Omega = 4,8 k \Omega$$

$$\rightarrow R_{\text{res}} = 5,2k + 4,8k \\ = 10k \Omega$$

(c)

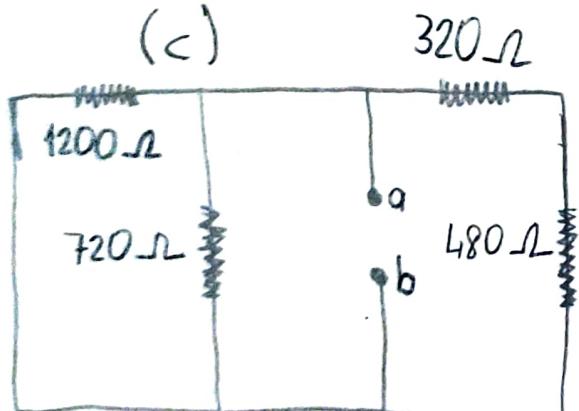


$$\rightarrow R_1 = 320 + 480 \\ = 800 \Omega$$

$$\rightarrow \frac{1}{R_{\text{res}}} = \frac{1}{1200} + \frac{1}{800} + \frac{1}{720}$$


$$R_{\text{res}} = 288 \Omega$$

XMM1

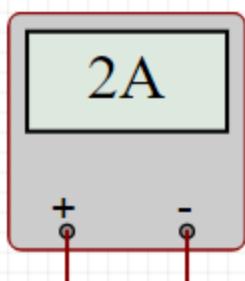

$$V = i \cdot R$$
$$V = 144$$
$$i = 2 \text{ A}$$
$$R = 72$$

For the circuit (a) in 3.8

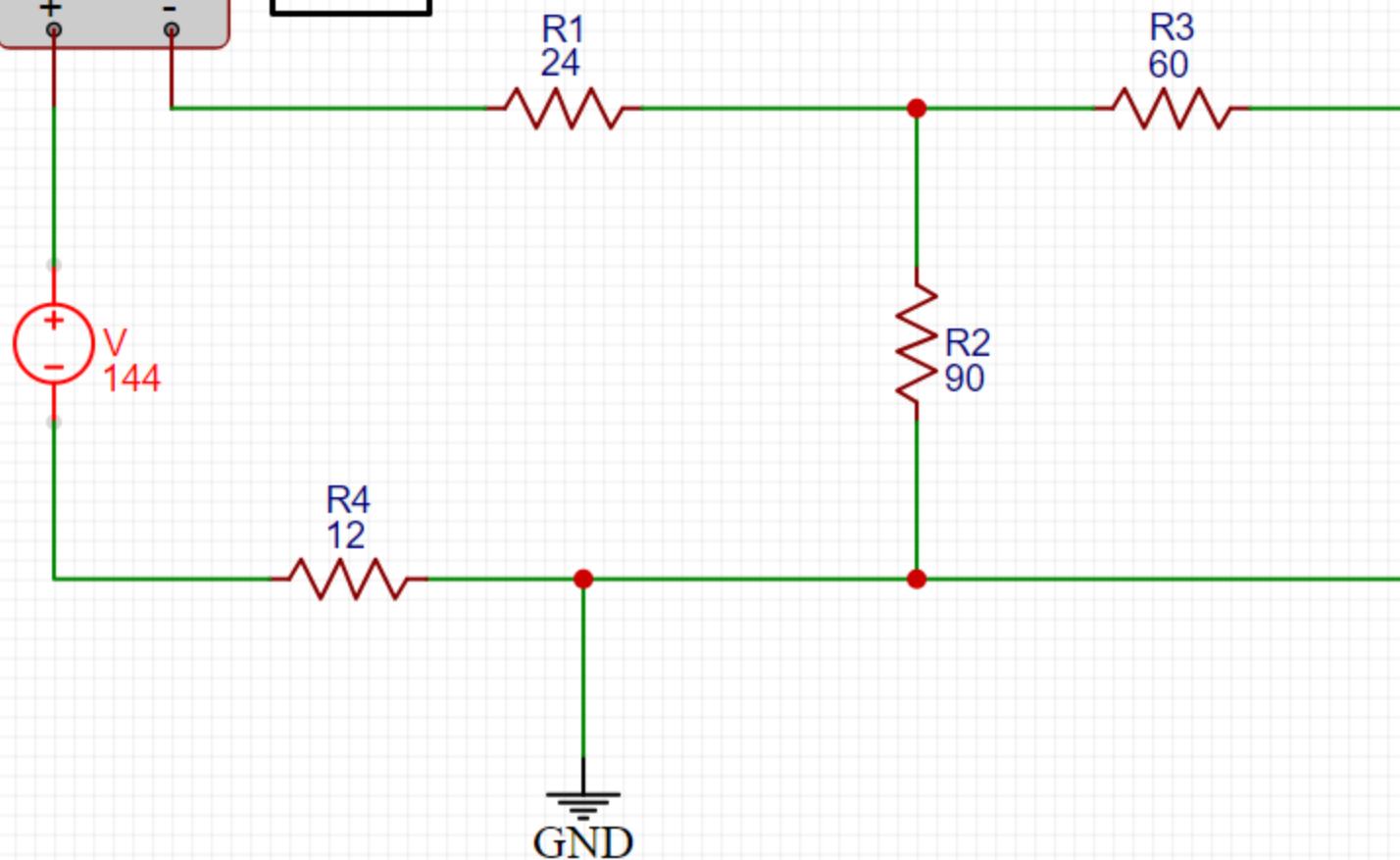

XMM1



For circuit (b) in question 3.8

$$V = i \cdot R$$

$$V = 100$$

$$i = 0.01 \text{ A}$$
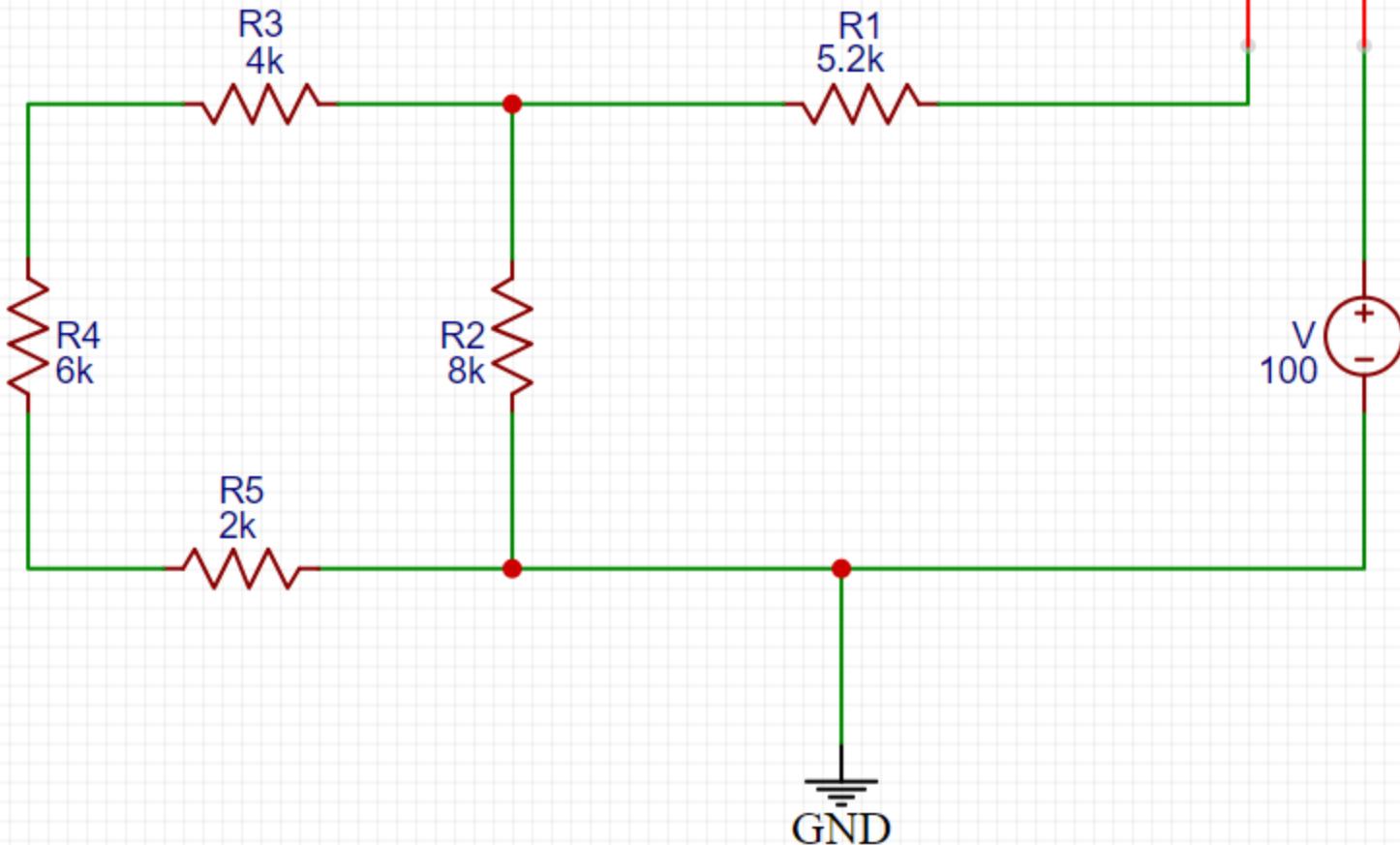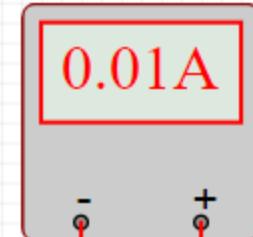
$$R = 100 / (1/100) = 10\,000 = 10\text{k}$$




$$\boxed{V = i \cdot R}$$
$$V = 288$$
$$i = 1 \text{ A}$$
$$R = 288 \text{ ohm}$$

$$\boxed{1 \text{ A}}$$

A current source of 1A is shown with the positive terminal at the top.


For the circuit (c) in question 3.8

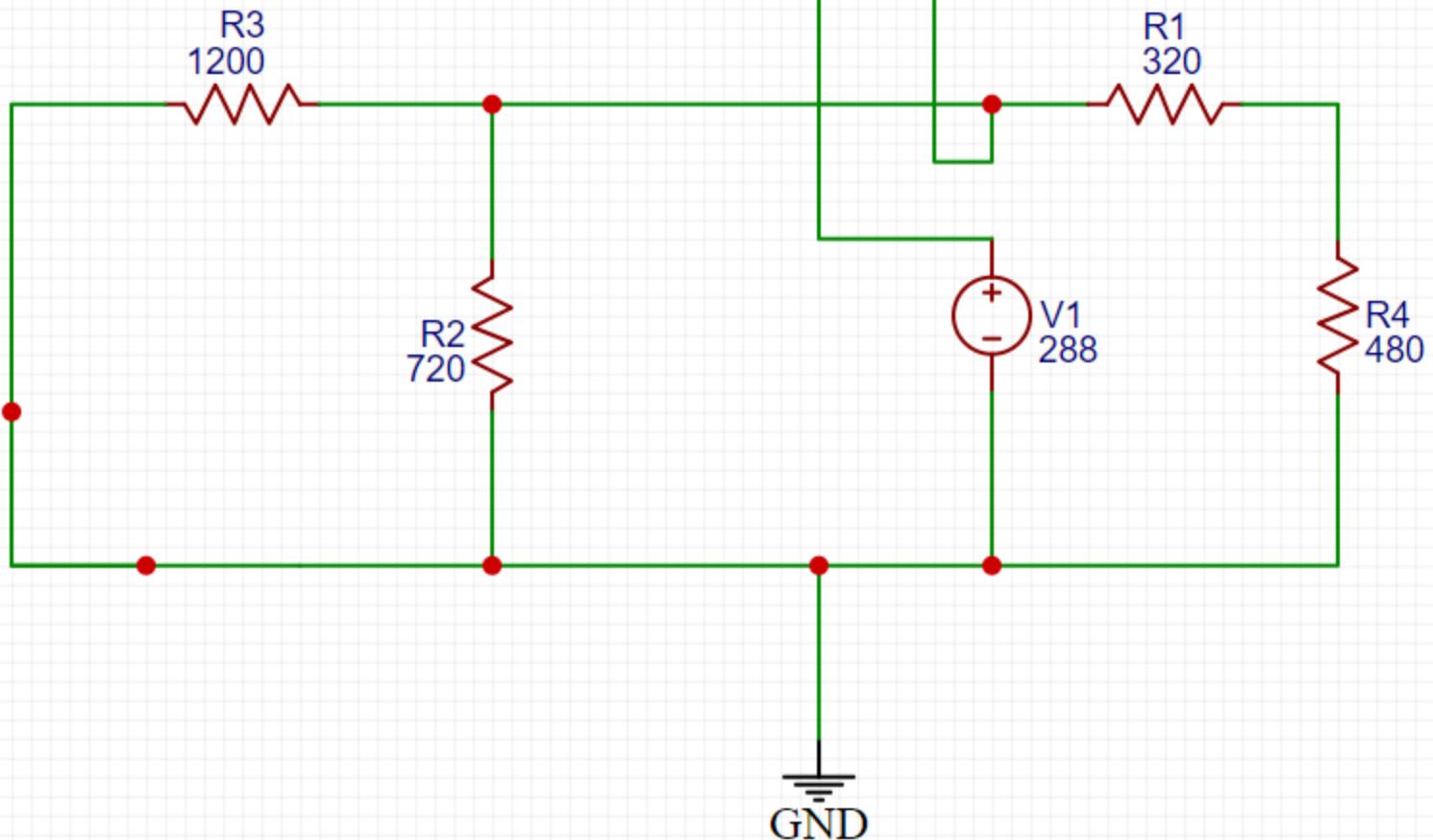



G E E K D A Y

• 3.13

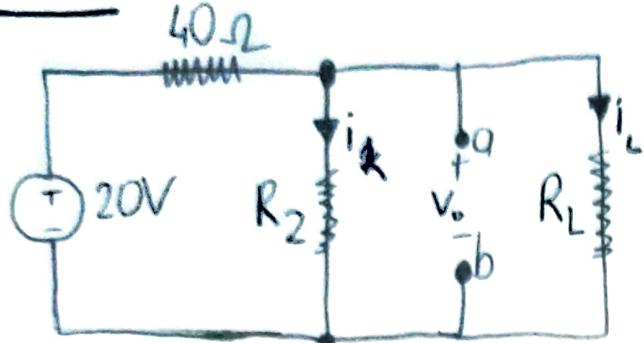

$$* i_2 = i_L + i_L, \quad i_L = \frac{R_2}{R_2 + R_L} \times i_2$$

$$* i_L = \frac{10}{10 + R_L} \times (0,425)$$

$$* 3 = i_L \cdot R_L$$

$$* 3 = \frac{(4,25)}{10 + R_L} \times R_L$$

$$* 30 + 3R_L = (4,25)R_L$$

$$* 30 = 1,25R_L$$

$$* R_L = 24\Omega$$

$$* 20 = (40, i_1) + (R_2, i_1)$$

$$16 = (40, i_1)$$

$$i_1 = 0,4A$$

$$* 20 = (40, i_2) + (R_{2L}, i_2)$$

$$17 = (40, i_2)$$

$$i_2 = 0,425A$$

$$* 4 = R_2 \cdot i_1$$


$$4 = R_2 \cdot (0,4)$$

$$R_2 = 10\Omega$$

Circuit of question 3.13


$R_2 = 10 \text{ ohm}$

$R_L = 24 \text{ ohm}$

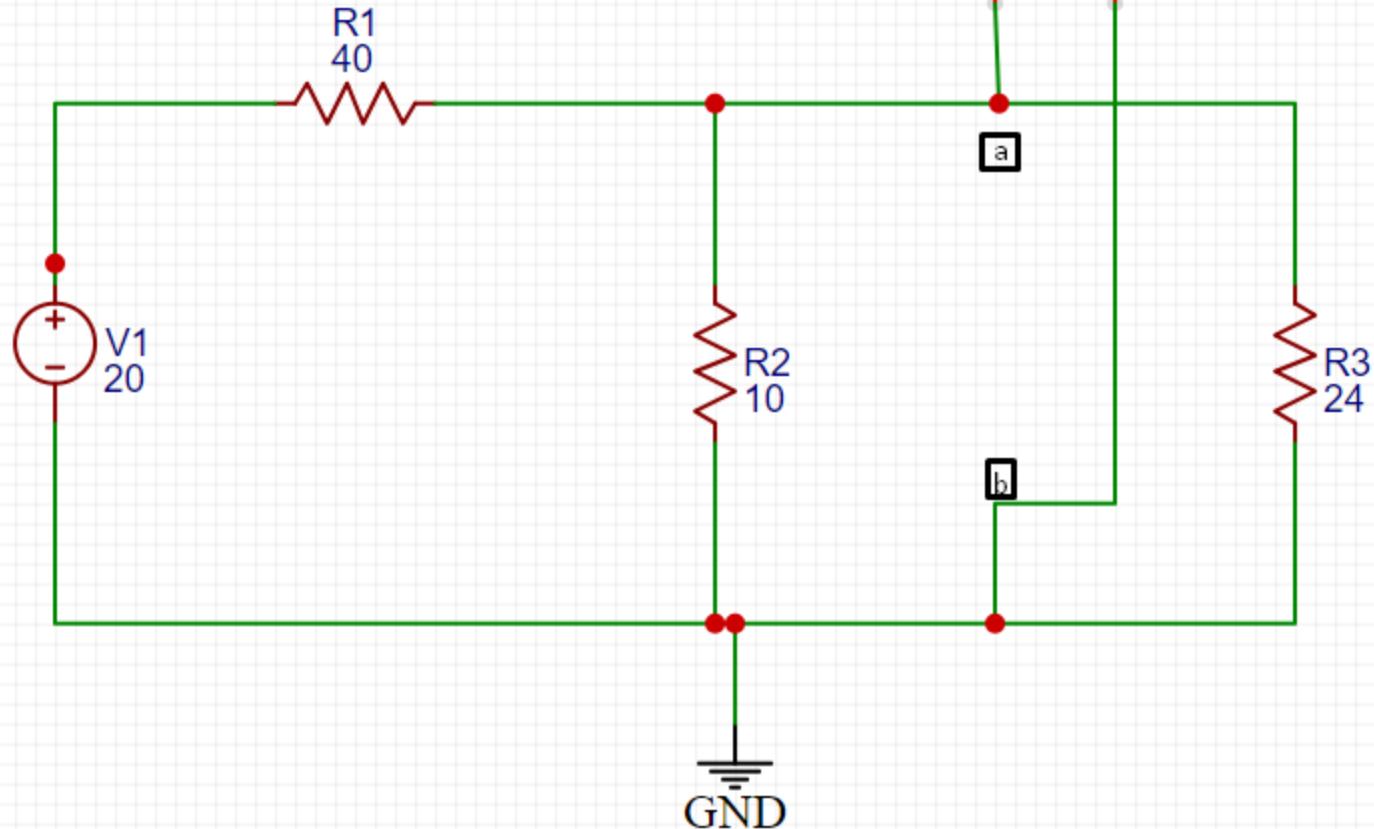

3V

• 3.17

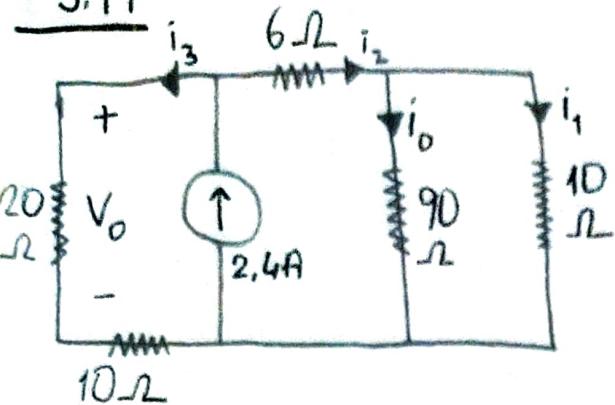

$$a) i_0 = 0,16A$$

$$V_0 = 24V$$

$$b) P = -15,36W$$

$$c) P = 25,6W$$

$$*\frac{1}{R_1} = \frac{1}{10} + \frac{1}{90} = \frac{10}{90}$$

$$*R_1 = 9\Omega$$

$$*R_2 = 9 + 6 = 15\Omega$$

$$*R_3 = 20 + 10 = 30\Omega$$

$$*i_2 = \frac{30}{15+30} \times (2,4) = \frac{2}{3} \cdot \frac{24}{10} = \frac{16}{10} = 1,6A$$

$$*i_0 = \frac{10}{90+10} \times i_2 = \frac{1}{10} \times \frac{16}{10} = 0,16A //$$

$$*2,4 = i_3 + i_2 = i_3 + 1,6$$

$$i_3 = 0,8A$$

$$*V_0 = i_3 \cdot R_3 = (0,8) \cdot (30) = 24V //$$

$$*P = -V \cdot i_2 = -(R \cdot i_2) \cdot i_2$$

$$= -(6 \cdot 1,6) \cdot 1,6$$

$$= -15,36W //$$

$$\frac{1}{R} = \frac{1}{15} + \frac{1}{30} = \frac{3}{30}$$


$$*P = V \cdot i = (R \cdot i) \cdot i = R \cdot i^2$$

$$R = 10\Omega$$


$$P = 10 \cdot (1,6)^2$$

$$= 25,6W$$

VO

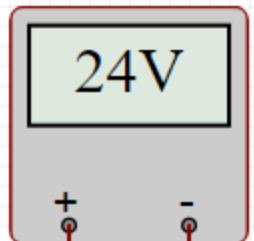


IO

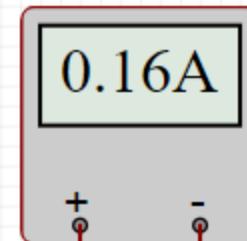


Circuit of question 3.17
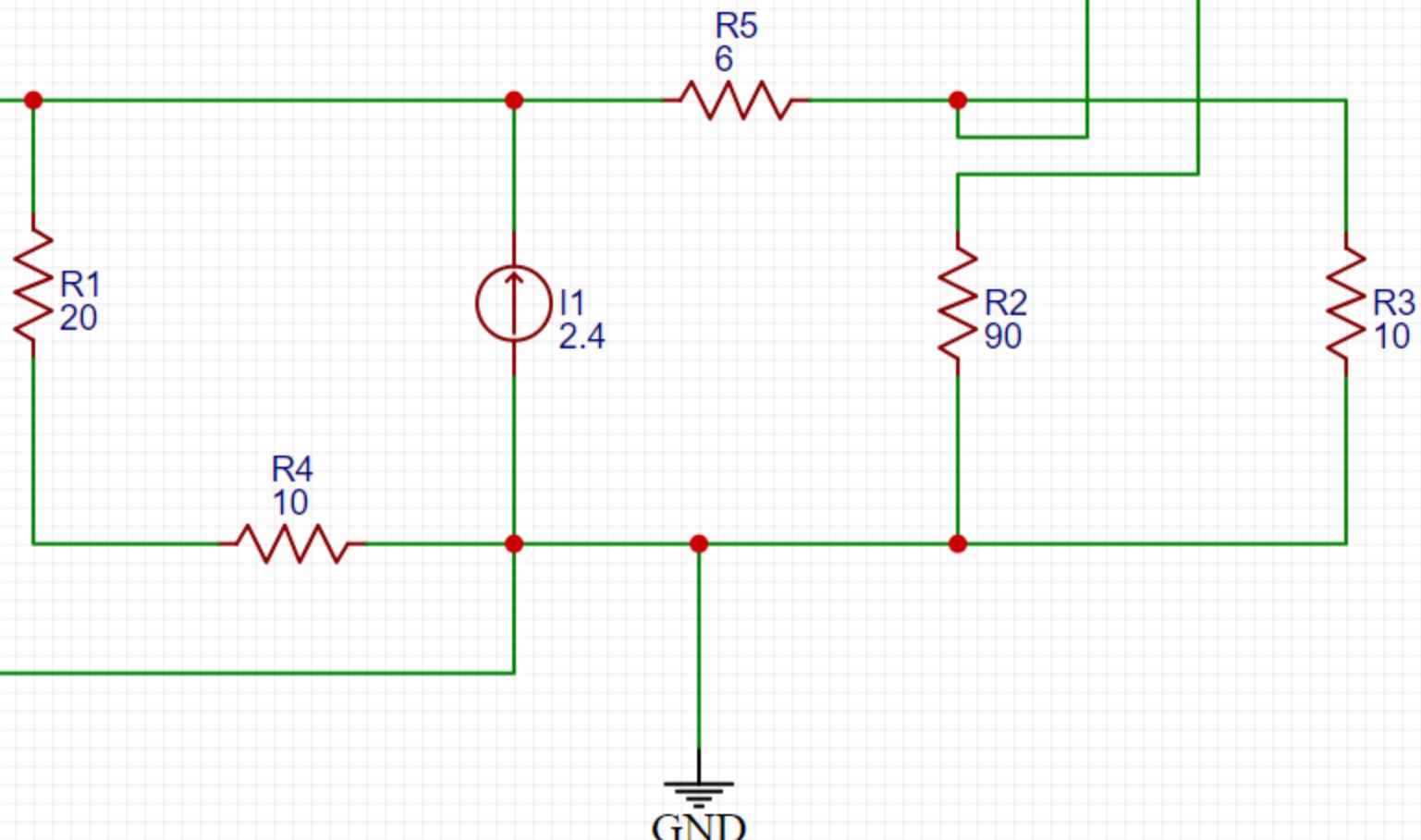
$$io = 0.16 \text{ A}$$
$$Vo = 24 \text{ V}$$



• 3.18

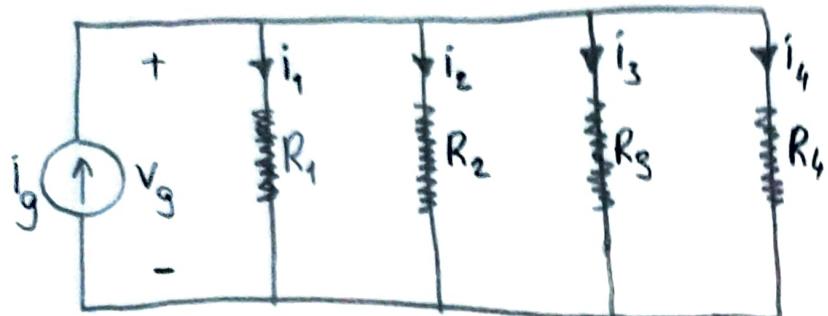

$$* V_g = i_g \cdot R_{es}$$

$$25 = 0,05 \cdot R_{es}$$

$$R_{es} = 500 \Omega$$

$$i_1 = 3x = 5 \text{ mA}$$

$$i_2 = 5x = \frac{25}{3} \text{ mA}$$

$$i_3 = 10x = \frac{50}{3} \text{ mA}$$

$$i_4 = 12x = 20 \text{ mA}$$

$$R_1 = 5000 \Omega$$

$$R_2 = 3000 \Omega$$

$$R_3 = 1500 \Omega$$

$$R_4 = 1250 \Omega$$

$$* i_g = i_1 + i_2 + i_3 + i_4$$

$$50 \text{ mA} = 30x$$


$$x = \frac{5}{3} \text{ mA}$$

$$* R_1 = \frac{V_g}{i_1} = \frac{25}{0,005} = 5000 \Omega$$

$$* R_2 = \frac{V_g}{i_2} = \frac{25}{\frac{25}{3} \cdot 0,001} = 3000 \Omega$$

$$* R_3 = \frac{V_g}{i_3} = \frac{25}{\frac{50}{3} \cdot 0,001} = 1500 \Omega$$
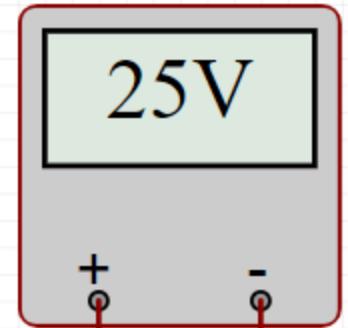
$$* R_4 = \frac{V_g}{i_4} = \frac{25}{0,02} = \frac{2500}{2} = 1250 \Omega$$



Circuit of question 3.18

$R_1 = 5000 \text{ ohm}$


$R_2 = 3000 \text{ ohm}$

$R_3 = 1500 \text{ ohm}$


$R_4 = 1250 \text{ ohm}$

$V_g = 25 \text{ V}$

$i_g = 50 \text{ mA}$

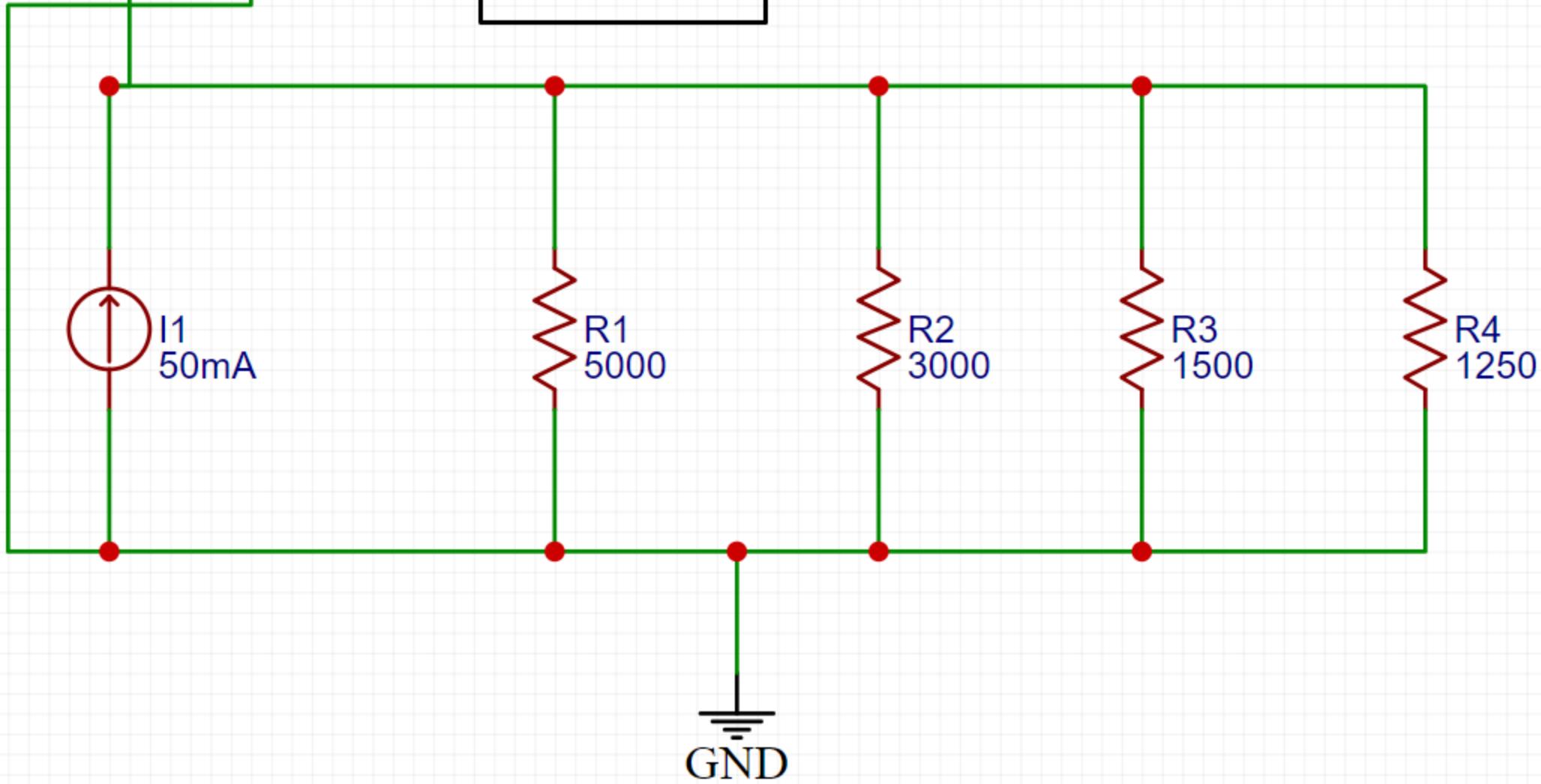

• 3.19

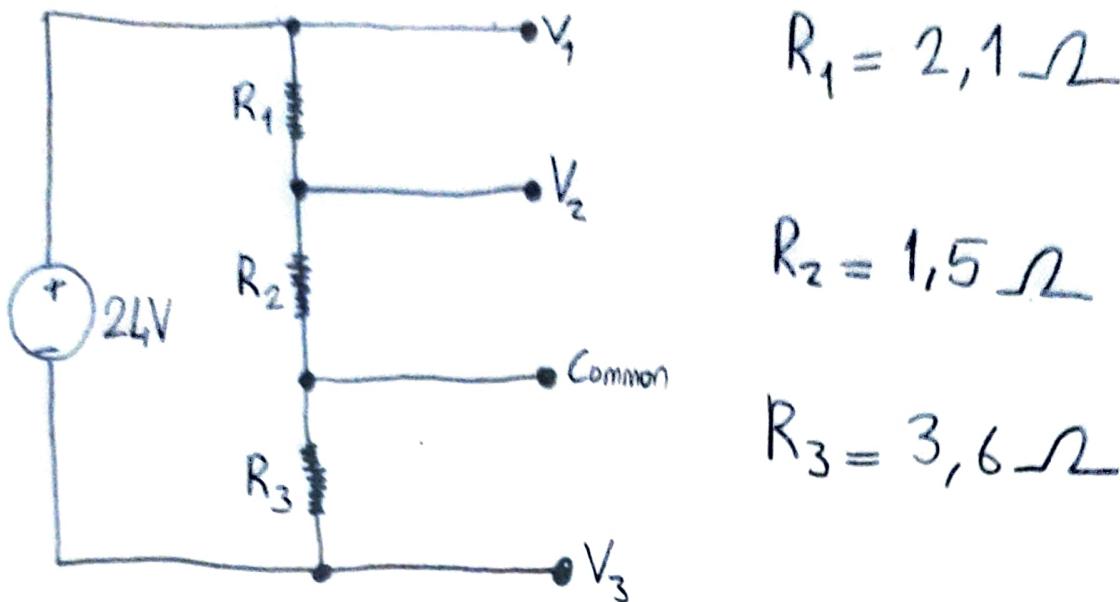

$$R_1 = 2,1 \Omega$$

$$R_2 = 1,5 \Omega$$

$$R_3 = 3,6 \Omega$$

a) $P = V \cdot i$

$$80 = 24 \cdot i$$

$$i = \frac{10}{3} A$$

$$R_{es} = \frac{V}{i} = \frac{24}{\frac{10}{3}} = 7,2 \Omega$$


$$R_{es} = R_1 + R_2 + R_3 = 7,2 \Omega$$

b) $V_1 = i \cdot (R_1 + R_2) \Rightarrow R_1 + R_2 = \frac{12}{\frac{10}{3}} = 3,6 \Omega$

$$V_2 = i \cdot R_1 \Rightarrow R_1 = \frac{5}{\frac{10}{3}} = 1,5 \Omega$$


$$V_3 = i \cdot R_3 \Rightarrow R_3 = \frac{12}{\frac{10}{3}} = 3,6 \Omega$$

AMPERMETER

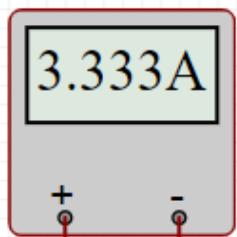

Circuit of question 3.19

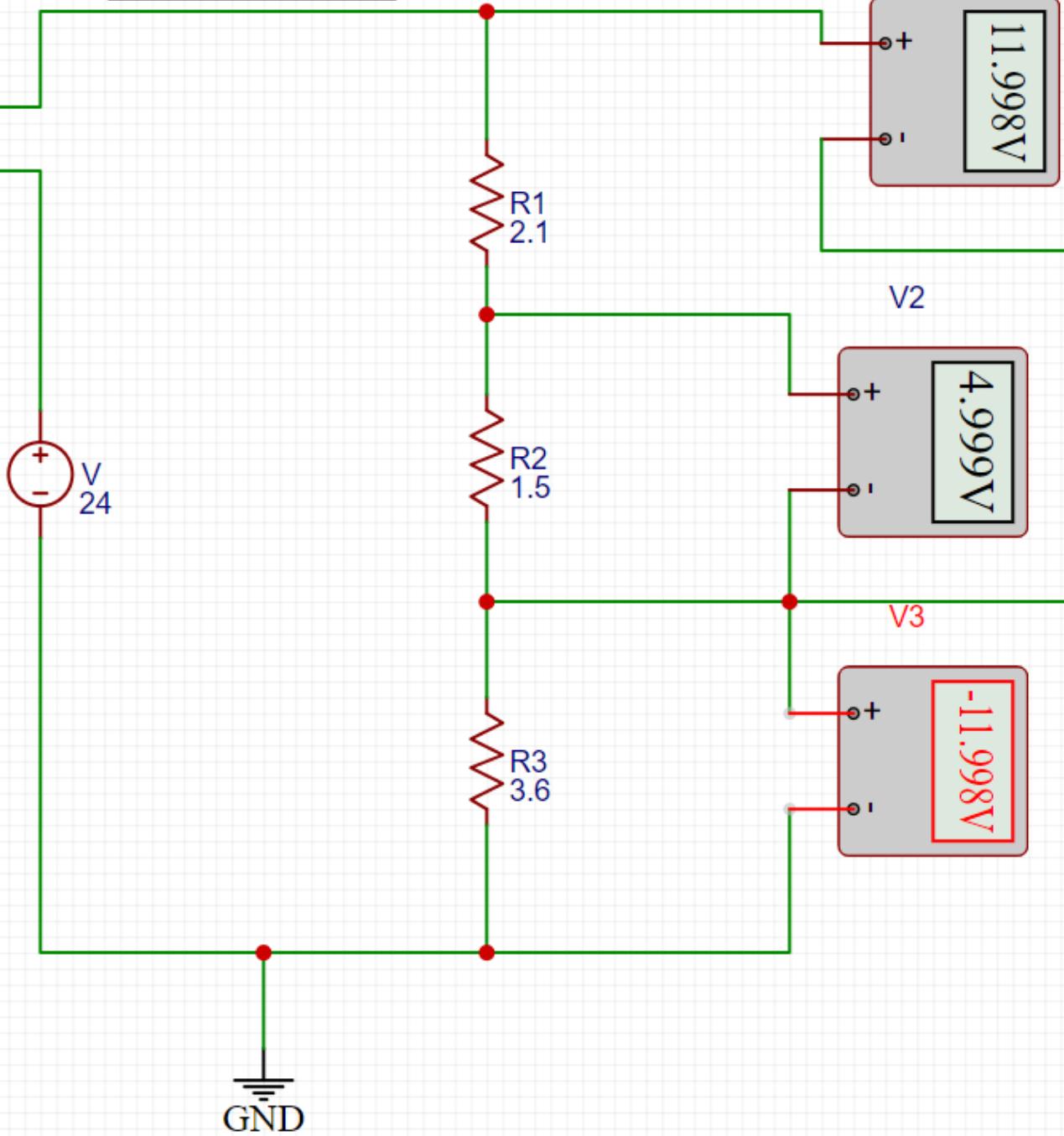$V_1 = 12 \text{ V}$ $R_1 = 2,1 \text{ ohm}$
 $V_2 = 5 \text{ V}$ $R_2 = 1,5 \text{ ohm}$
 $V_3 = -12 \text{ V}$ $R_3 = 3,6 \text{ ohm}$






G E E K D A Y

• 3.22

(b)

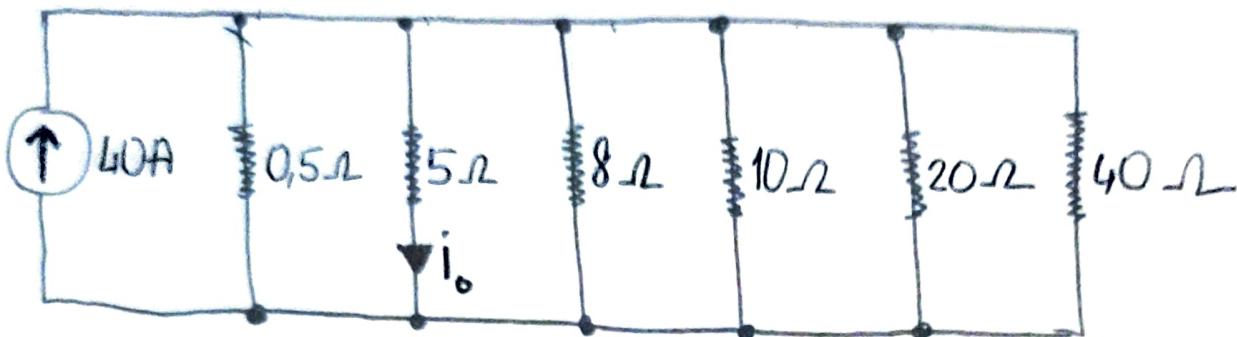

$$a) i_k = \frac{i_g G_k}{G_1 + G_2 + \dots + G_k + \dots + G_N}$$

$$* G_1 + G_2 + \dots + G_k + \dots + G_N = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = \frac{1}{R_{\text{res}}} = \frac{1}{V_g / i_g} = \frac{i_g}{V_g}$$

$$* i_k = \frac{i_g \cdot G_k}{i_g / V_g} = G_k \cdot V_g = \left(\frac{V_g}{R_k} \right) \quad V_g = i_k \cdot R_k$$

$$b) i_0 = \frac{i \cdot G_0}{\underbrace{G_1 + G_2 + \dots + G_6}_{R_{\text{res}}}}$$

$$i = 40A$$

$$G_0 = \frac{1}{5}$$

$$i_0 = \frac{40 \cdot \frac{1}{5}}{\frac{25}{10}} = \frac{8.0}{2.5}$$

$$R_{\text{res}} = 2,5 \Omega$$


$$i_0 = 3,2 A$$

$$\frac{1}{R_{\text{res}}} = \frac{1}{0.5} + \frac{1}{5} + \frac{1}{8} + \frac{1}{10} + \frac{1}{20} + \frac{1}{40}$$

$$= \frac{80 + 8 + 5 + 4 + 2 + 1}{40}$$

$$= \frac{100}{40} = 2,5 \Omega$$


AMPERMETRE

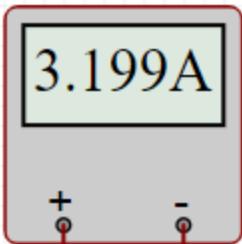


Circuit of question 3.22 part (b)

$$i_0 = 3,2 \text{ A}$$

$$R_{\text{es}} = 2,5 \text{ ohm}$$

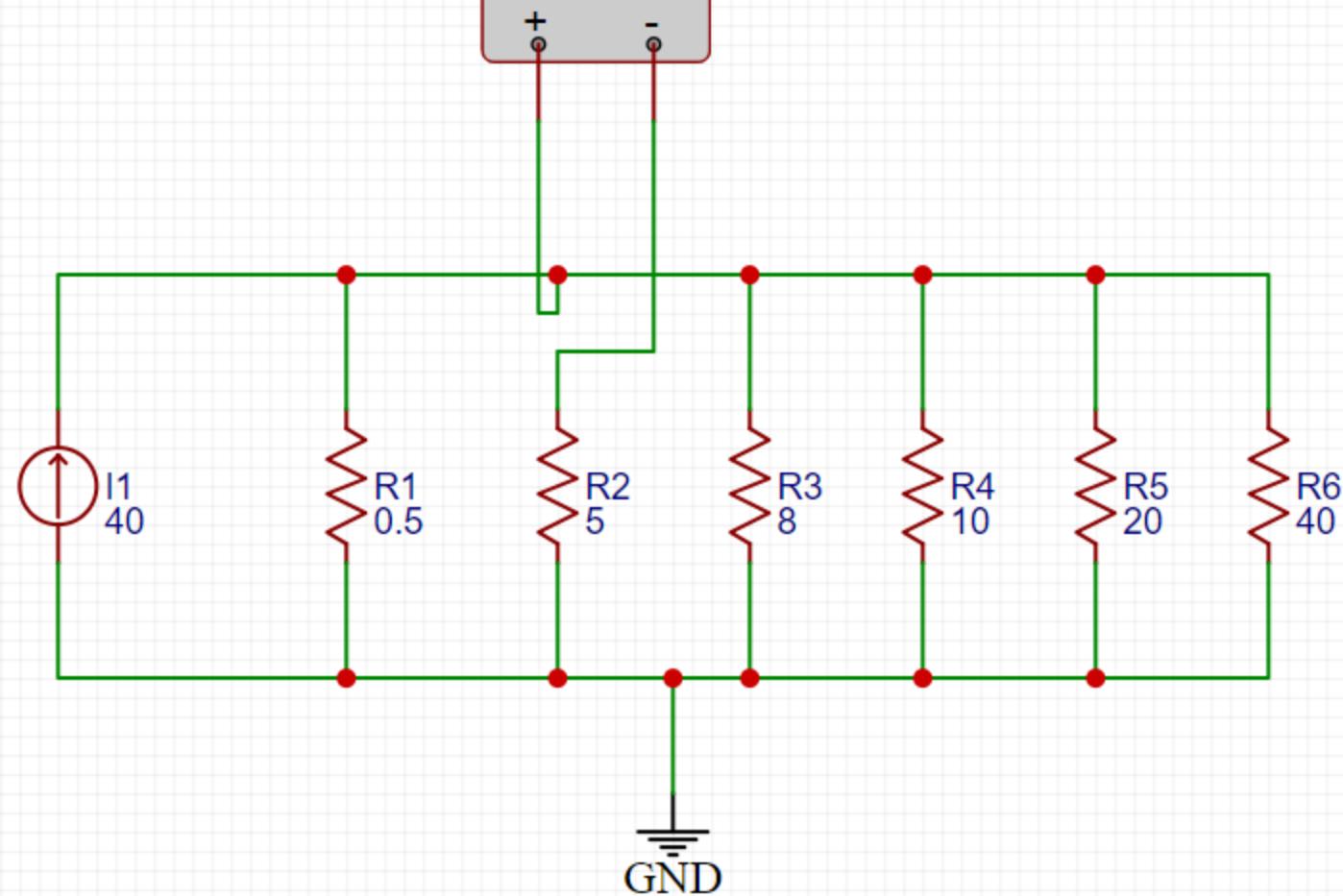

• 3.28

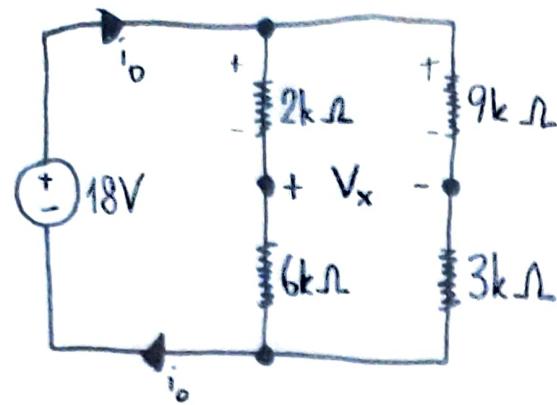

$$a) * R_2 = 9k + 3k \\ = 12k \Omega$$

$$* i = \frac{V}{R} \Rightarrow i_0 = \frac{18}{4,8k} = \frac{180}{48k} = 3,75 \text{ mA}$$

$$* R_1 = 2k + 6k \\ = 8k$$

$$* i_1 = \frac{R_2}{R_1 + R_2} \cdot i_0 = \frac{12k}{20k} \cdot 3,75 = 2,25 \text{ mA}$$

$$* \frac{1}{R_{es}} = \frac{1}{12k} + \frac{1}{8k} = \frac{5}{24k}$$

$$* i_2 = i_0 - i_1 = 3,75 - 2,25 = 1,5 \text{ mA}$$

$$R_{es} = 4,8 \Omega$$

$$* V_x + (2k \cdot i_1) - (9k \cdot i_2) = 0$$

$$(2k \cdot i_1) = 2 \cdot (2,25) = 4,5 \text{ V}$$

$$(9k \cdot i_2) = 9 \cdot (1,5) = 13,5 \text{ V}$$

$$V_x = 13,5 - 4,5 = 9 \text{ V}$$

b) $V_x + (2k \cdot i_1) - (9k \cdot i_2) = 0$

$$* V_x = \frac{16V_s - 3V_s}{12} = \frac{13V_s}{12}$$

$$* V_s - (2k \cdot i_1) - (6k \cdot i_1) = 0$$

$$V_x = \frac{13V_s}{12}$$

$$V_s = 8k \cdot i_1 \Rightarrow \frac{V_s}{4} = 2k \cdot i_1 //$$


$$* V_s - (9k \cdot i_2) - (3k \cdot i_2) = 0$$

$$V_s = 12k \cdot i_2 \Rightarrow \frac{4V_s}{3} = 9k \cdot i_2 //$$

$$* V_x + (2k \cdot i_1) - (9k \cdot i_2) = 0$$

$$V_x + \frac{V_s}{4} - \frac{4V_s}{3} = 0$$


Circuit of question 3.28 part (a)

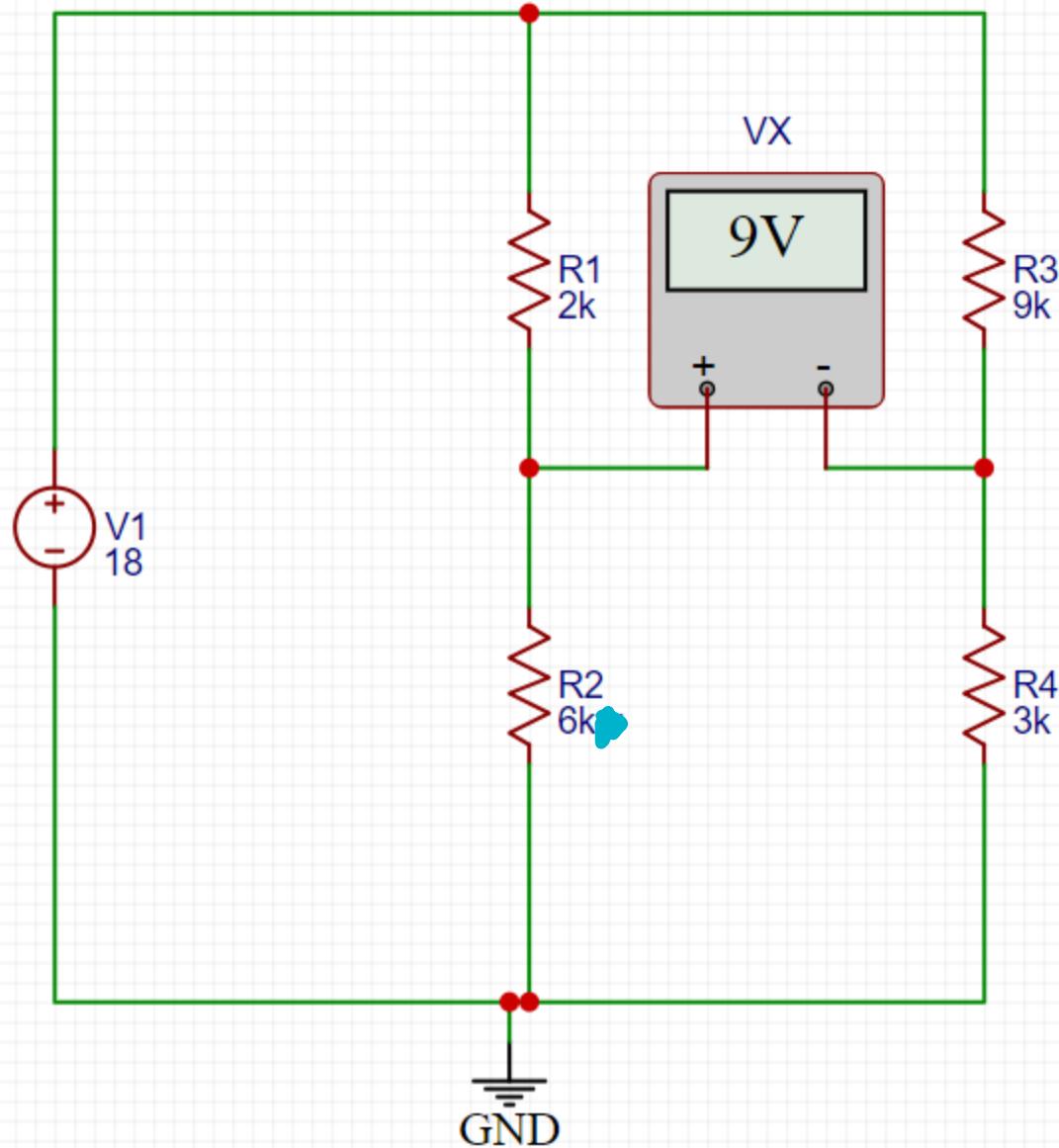




GEEKDAY

• 3.32

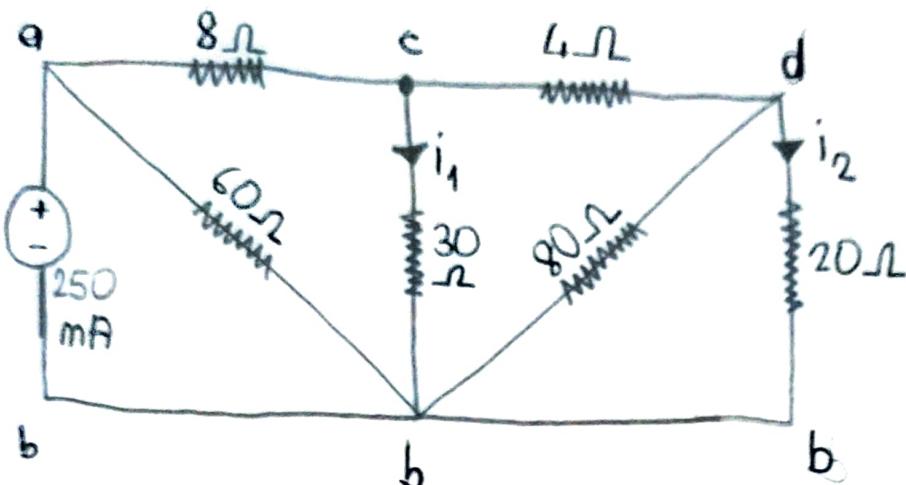

$$i_1 = 75 \text{ mA}$$

$$i_2 = 90 \text{ mA}$$

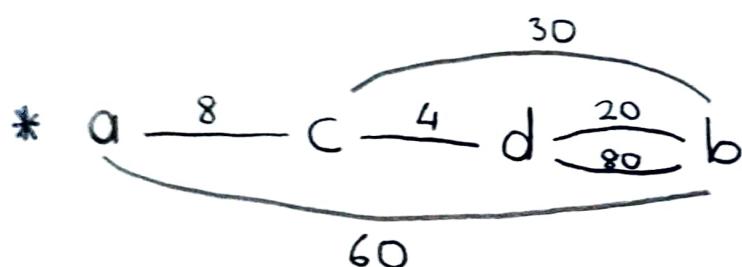

$$* R_{db} = \frac{20 \cdot 80}{100} = 16 \Omega$$


$$* R_{cb} = \frac{30 \cdot (16+4)}{30 + (16+4)} = \frac{30 \cdot 20}{50} = 12 \Omega$$

$$* i_{ac} = \frac{60}{60 + (12+8)} \cdot 250 = \frac{3}{4} \cdot 250 = 187,5 \text{ mA}$$


$$* i_1 = \frac{20}{30+20} \cdot \frac{187,5}{10} = \frac{2 \cdot 187,5}{50} = 75 \text{ mA} //$$

$$* i_{cd} = 187,5 - 75 = 112,5 \text{ mA}$$
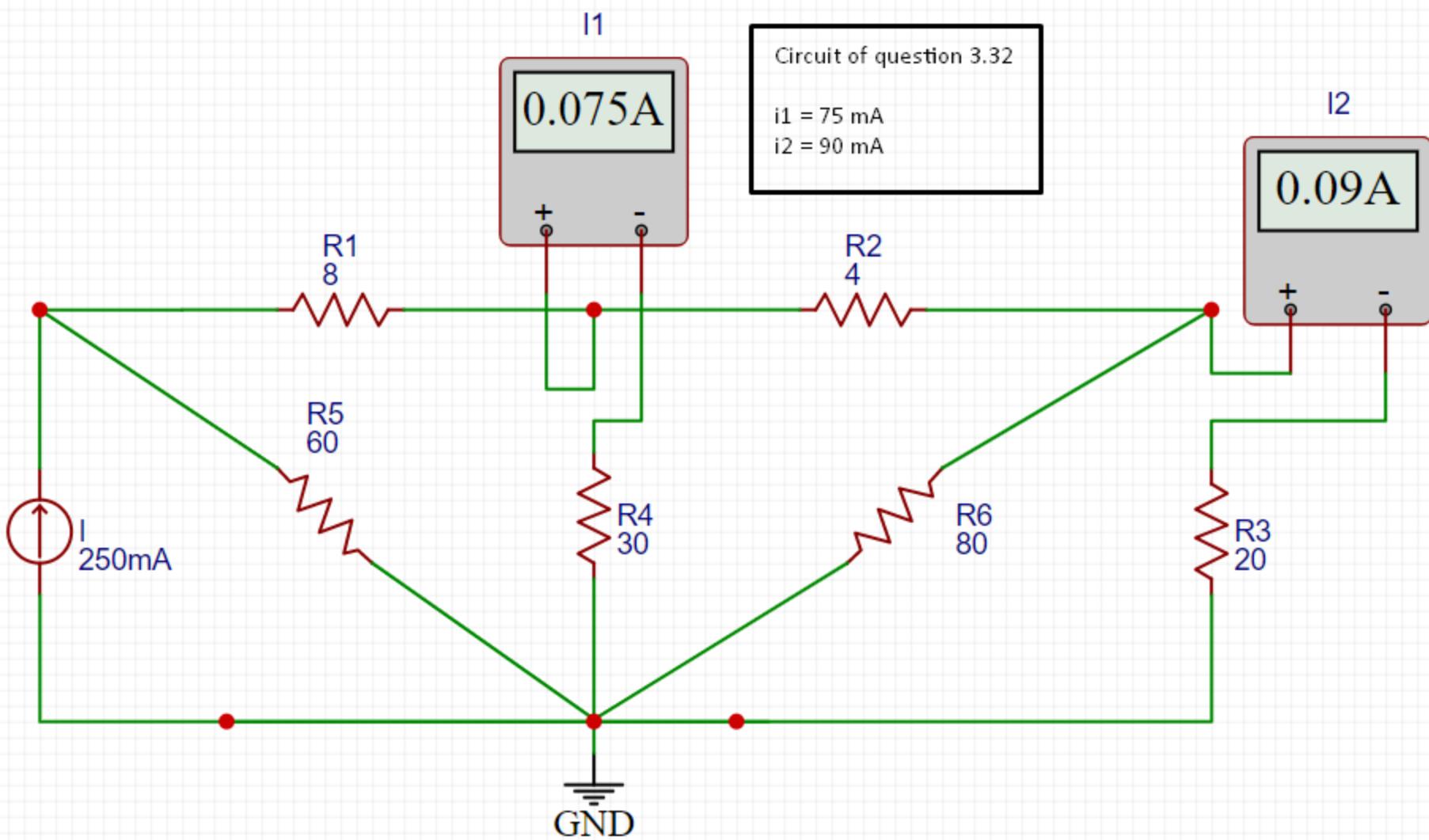
$$* i_2 = \frac{80}{20+80} \cdot (112,5) = \frac{8}{10} \cdot \frac{112,5}{10} = 90 \text{ mA} //$$



• 3.52

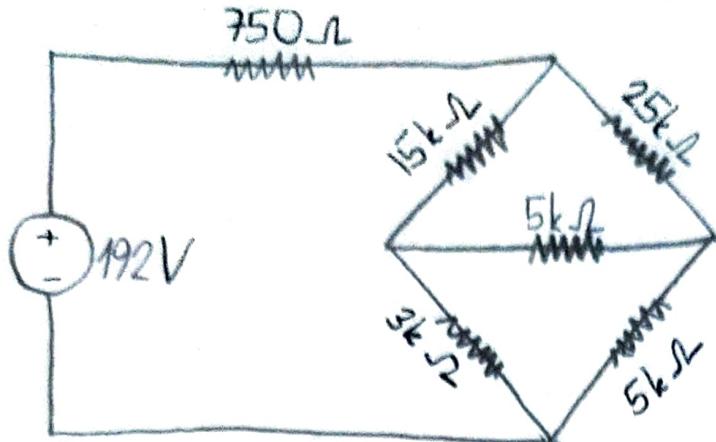

$$* R_1 = 25k + 5k = 30k \Omega$$

$$* R_2 = 15k + 3k = 18k \Omega$$

$$* R_{12} = \frac{18 \cdot 30}{18 + 30} = \frac{3 \cdot 30}{8} = 11,25k \Omega$$

$$* R_{\text{es}} = 0,75k + 11,25k = 12k \Omega$$

$$* i = \frac{V}{R} = \frac{192}{12k} = 16 \text{ mA}$$

$$* i_2 = \frac{30k}{18k + 30k} \cdot 16 \text{ mA} = \frac{30 \cdot 16}{48} \text{ mA} = 10 \text{ mA}$$

$$* V = i_2 \cdot R = (10 \text{ mA}) \cdot (3k \Omega)$$

$$V = 30$$

$$* P = -V \cdot i$$

$$= -30 \cdot 10 \text{ mA}$$

$$= -300 \text{ mW}$$

$$= -0,3 \text{ W} //$$


Circuit of question 3.52

$$V = i \cdot R$$


$$V = 0.01 \cdot 3k = 30 v$$

R1
750
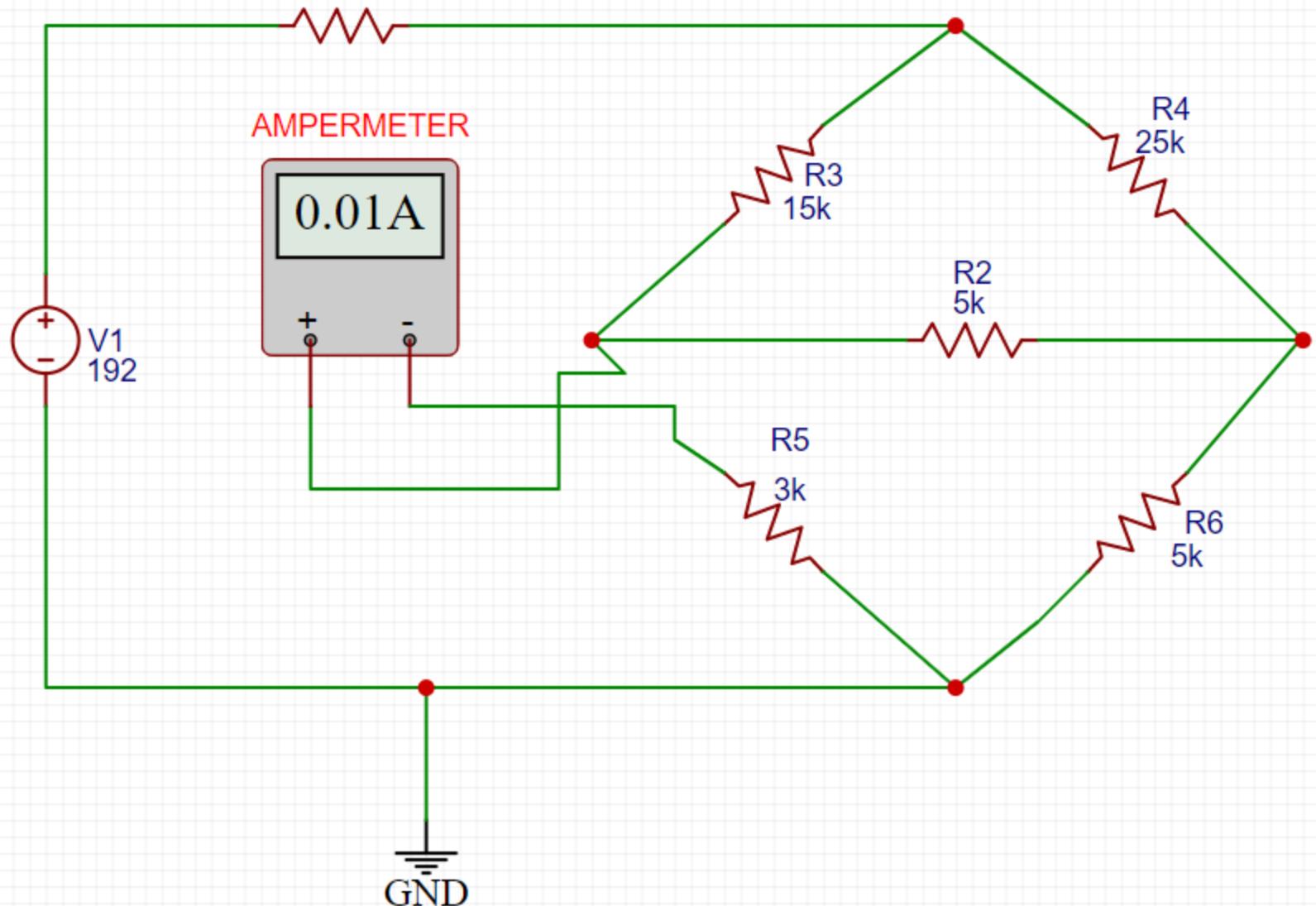
$$p = -V \cdot i = 30 \cdot 0.01 = -0.3 W$$



• 3.53

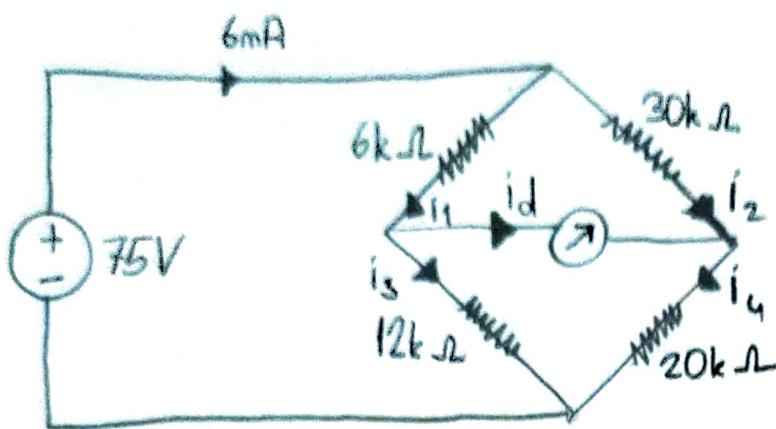

$$i_1 = 5 \text{ mA}$$

$$i_2 = 1 \text{ mA}$$

$$i_3 = 3,75 \text{ A}$$

$$i_4 = 2,25 \text{ A}$$

$$i_d = i_1 - i_3 = i_4 - i_2$$

$$i_d = 1,25 \text{ mA}$$

$$* R_1 = \frac{6 \cdot 30}{6+30} = \frac{180}{36} = 5 \text{ k}\Omega$$

$$* R_2 = \frac{12 \cdot 20}{12+20} = \frac{240}{32} = 7,5 \text{ k}\Omega$$

$$* R_{es} = 5 \text{ k} + 7,5 \text{ k} = 12,5 \text{ k}\Omega$$

$$* i = \frac{V}{R} = \frac{75}{12,5 \text{ k}} = 6 \text{ mA}$$

$$* i_1 = \frac{30 \text{ k}}{30 \text{ k} + 6 \text{ k}} \cdot 6 \text{ mA} = \frac{180}{36} = 5 \text{ mA}_{\parallel}$$

$$* i_3 = \frac{20 \text{ k}}{20 \text{ k} + 12 \text{ k}} \cdot 6 \text{ mA} = \frac{120}{32} \text{ mA} = 3,75 \text{ mA}$$

• 3.58

$$R_1 = 50 \Omega$$

$$R_2 = 25 \Omega$$

$$R_3 = 50 \Omega$$

$$R_4 = 20 \Omega$$

$$R_5 = 30 \Omega$$

a)

$$* R_A = \frac{R_3 \cdot R_2 + R_3 \cdot R_5 + R_2 \cdot R_5}{R_3} = \frac{50 \cdot 25 + 50 \cdot 30 + 25 \cdot 30}{50}$$

$$R_A = 25 + 30 + 15 = 70 \Omega //$$


$$* R_B = \frac{R_3 \cdot R_2 + R_3 \cdot R_5 + R_2 \cdot R_5}{R_2} = \frac{50 \cdot 25 + 50 \cdot 30 + 25 \cdot 30}{25}$$

$$R_B = 50 + 60 + 30 = 140 \Omega //$$

$$* R_C = \frac{R_3 \cdot R_2 + R_3 \cdot R_5 + R_2 \cdot R_5}{R_5} = \frac{50 \cdot 25 + 50 \cdot 30 + 25 \cdot 30}{30}$$

$$R_C = 116,7 \Omega$$
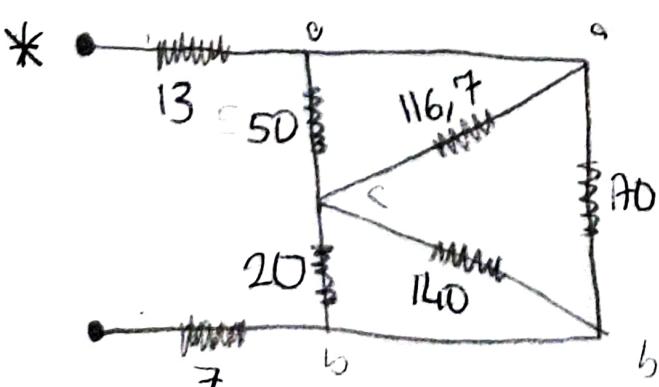
$$* \frac{50 \cdot 116,7}{166,7} = 35 \Omega$$




$$* \frac{20 \cdot 140}{160} = 17,5 \Omega$$

$$* \frac{52,5 \cdot 70}{122,5} = 30 \Omega$$

$$* R_{AB} = 13 + 30 + 7 = \boxed{50 \Omega}$$



GEEKDAY

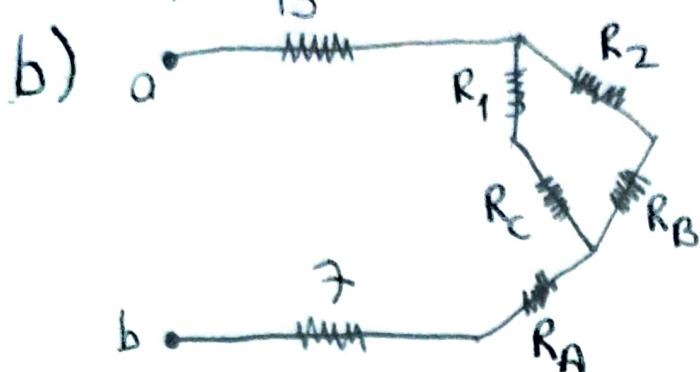

$$* R_A = \frac{20 \cdot 30}{20 + 30 + 50} = 6 \Omega$$

$$* R_B = \frac{50 \cdot 30}{100} = 15 \Omega$$


$$* R_C = \frac{20 \cdot 50}{100} = 10 \Omega$$

$$* R_1 + R_C = 50 + 10 = 60 \Omega$$

$$* R_2 + R_B = 25 + 15 = 40 \Omega$$

$$* \frac{40 \cdot 60}{100} = 24 \Omega$$

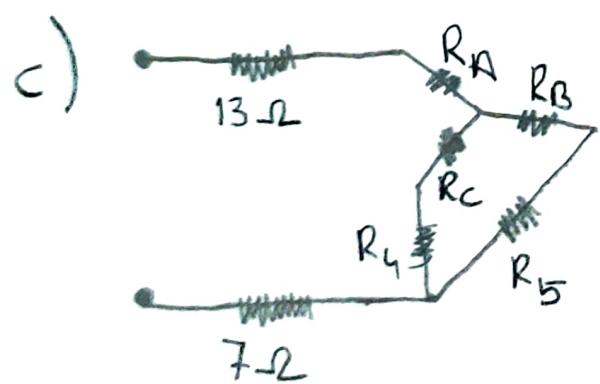
$$* R_{ab} = 24 + 6 + 13 + 7 = 50 \Omega //$$



$$* R_A = \frac{50 \cdot 25}{125} = 10 \Omega$$

$$* R_B = \frac{25 \cdot 50}{125} = 10 \Omega$$
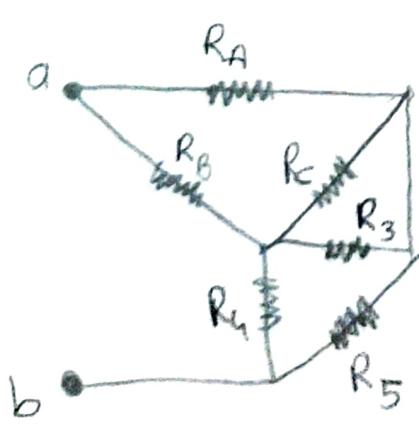
$$* R_C = \frac{50 \cdot 50}{125} = 20 \Omega$$




$$* R_A = \frac{13.50 + 13.25 + 25.50}{50} = 44.5 \Omega$$

$$* R_B = \frac{13.50 + 13.25 + 25.30}{25} = 69 \Omega$$

$$* R_C = \frac{13.50 + 13.25 + 25.30}{13} = 132.7 \Omega$$


AMPERMETER

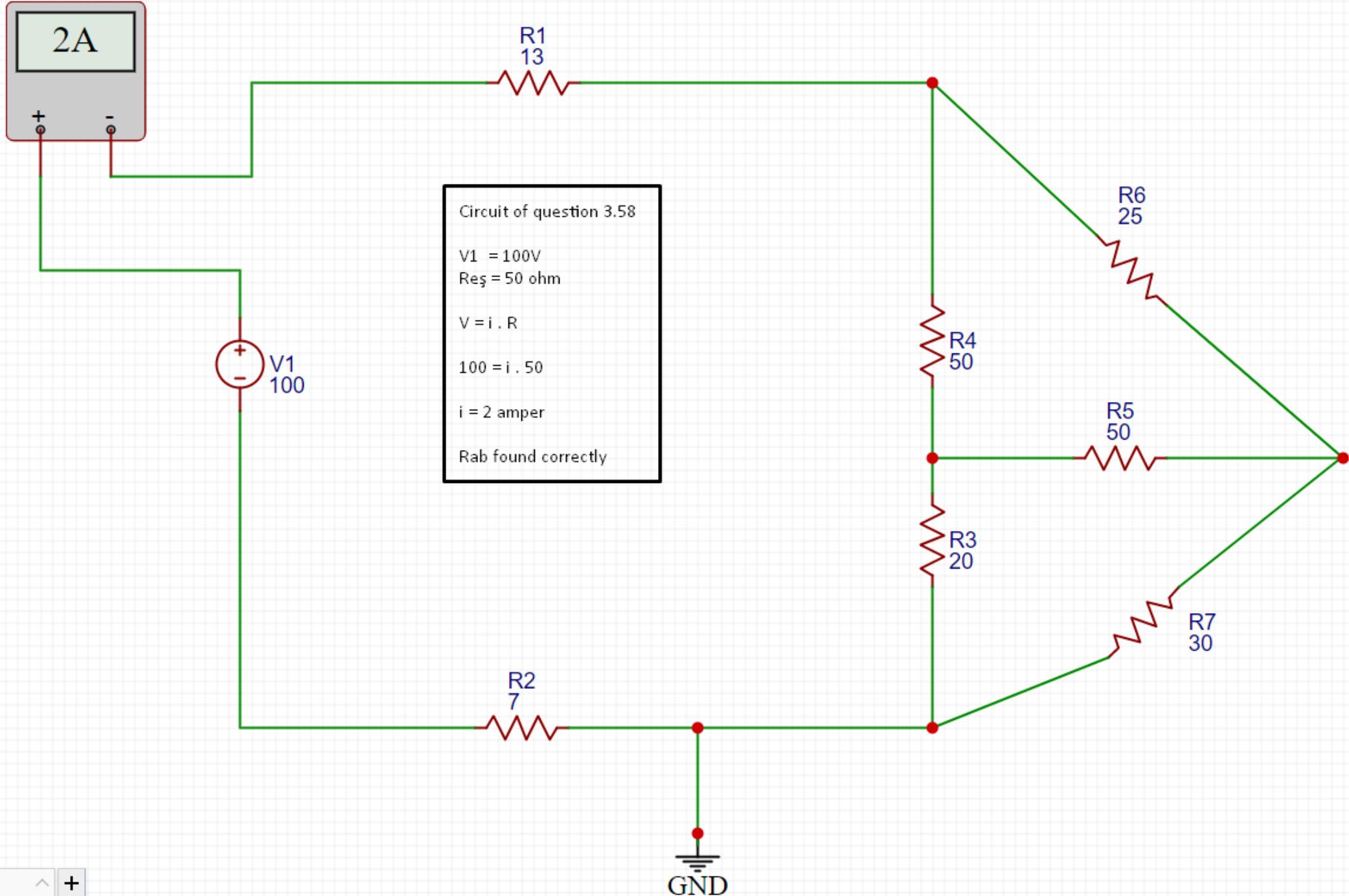




GEEK DAY

• 3.62

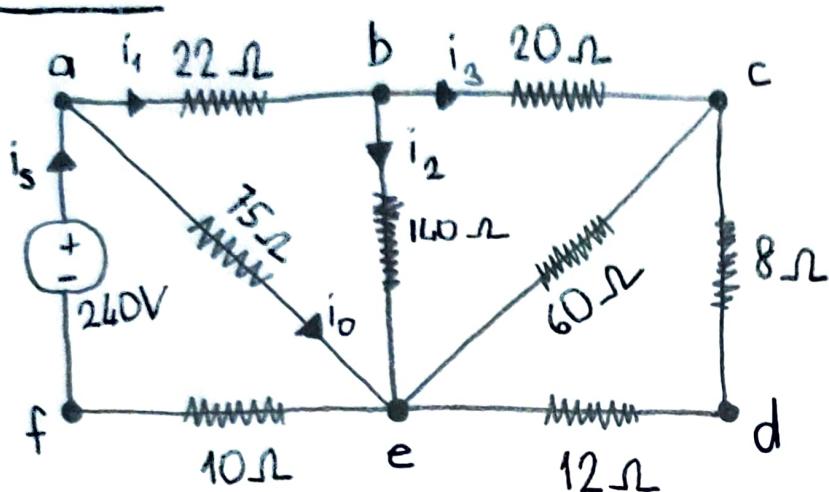

$$i_0 = 2,4 \text{ A}$$

$$P_{be} = -72,6 \text{ W}$$

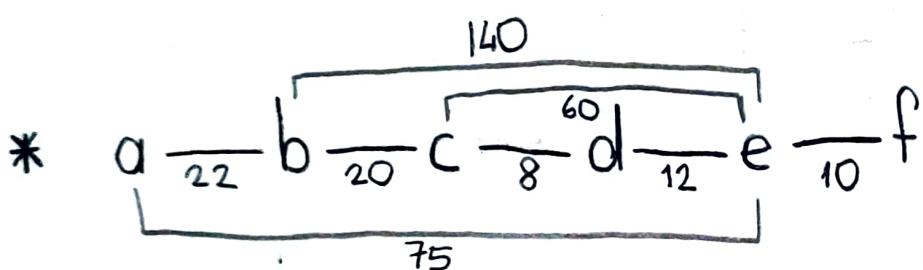

$$* R = 8 + 2 = 20$$

$$* i_0 = \frac{R_1}{R_0 + R_1} \cdot i_s = \frac{50}{125} \cdot 6 = 2,4 \text{ A}$$

$$R_{ce} = \frac{20 \cdot 60}{80} = 15 \Omega /$$

$$* R_0 = 75 \Omega$$

$$* R = 20 + 15 = 35 \Omega$$

$$R_1 = 50 \Omega$$

$$R_{be} = \frac{35 \cdot 140}{175} = 28 \Omega /$$

$$* i_2 = \frac{R_3}{R_2 + R_3} \cdot i_1 = \frac{35}{175} \cdot \frac{36}{10} = 0,72 \text{ A}$$

$$* R = 28 + 22 = 50 \Omega$$

$$R_2 = 140 \Omega$$

$$R_{de} = \frac{50 \cdot 75}{125} = 30 \Omega /$$

$$R_3 = 35 \Omega$$

$$* R_{\text{eq}} = 30 + 10 = 40 \Omega //$$

$$i_1 = i_s - i_0 = 6 - (2,4) = 3,6 \text{ A}$$

$$* i_s = i_1 + i_0 //$$


$$* P = -V \cdot i = -R \cdot i^2$$

$$= -140 \cdot (0,72)^2$$


$$= -72,6 \text{ W}$$

$$* i_1 = i_2 + i_3$$


I0

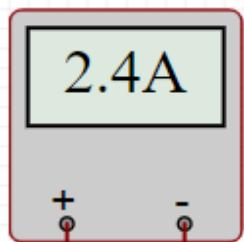


PBE

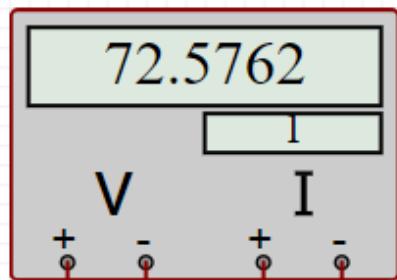

Circuit of question 3.62

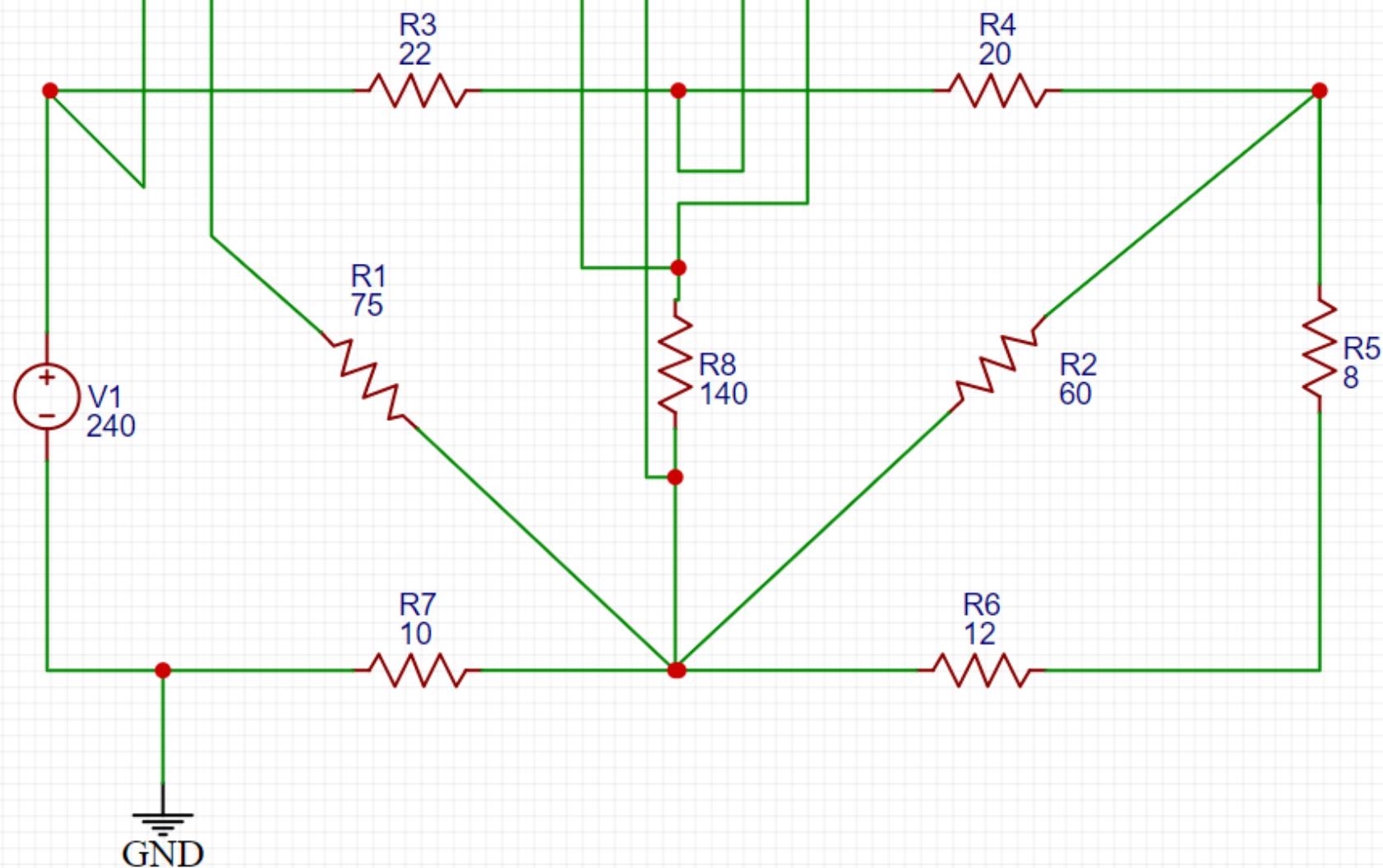


• 3.67

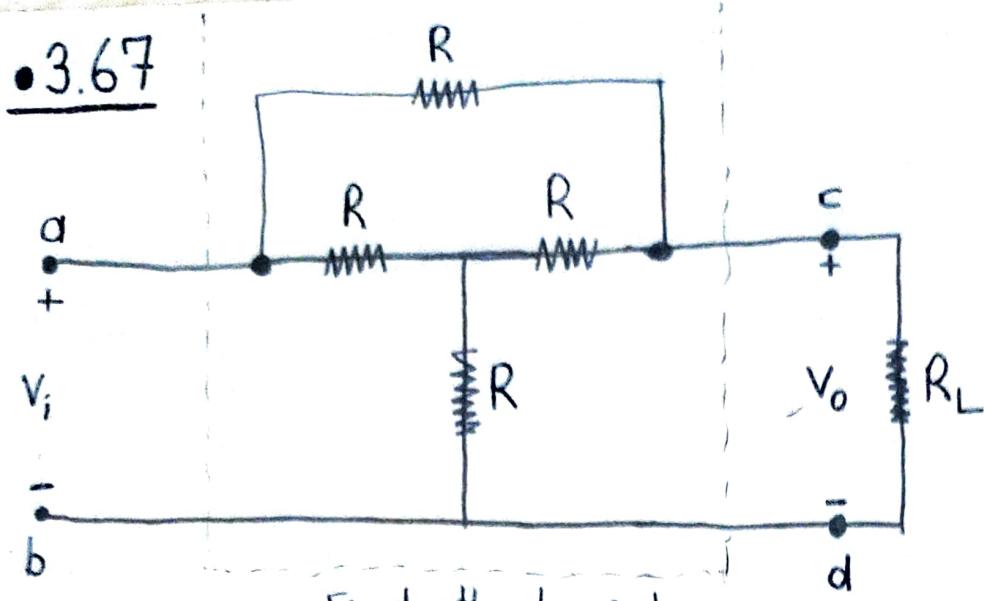

Fixed attenuator pad


a)

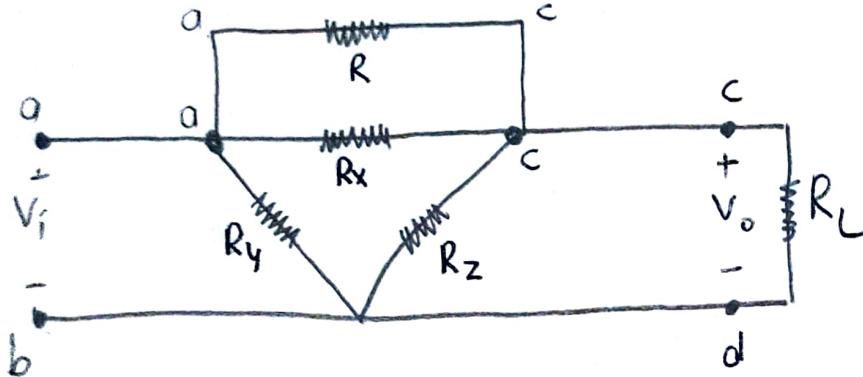

$$*R_x = \frac{(R, R) + (R, R) + (R, R)}{R} = 3R$$

$$*R_y = \frac{3R^2}{R} = 3R$$

$$*R_z = \frac{3R^2}{R} = 3R$$

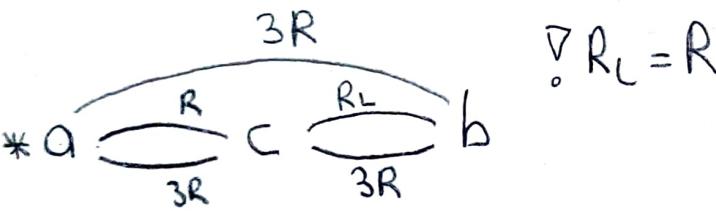


$$* \frac{R, 3R}{4R} + \frac{R, 3R}{4R}$$

$$* \frac{6R^2}{4R} = \frac{3R}{2}$$

$$* \frac{\frac{3R}{2} \cdot 3R}{\frac{3R}{2} + 3R} = \frac{\frac{9R^2}{2}}{\frac{9R}{2}} = R = R_{AB}$$

$$b) V_i = i \cdot R_{ab}$$

$$V_o = i \cdot R_{cb}$$

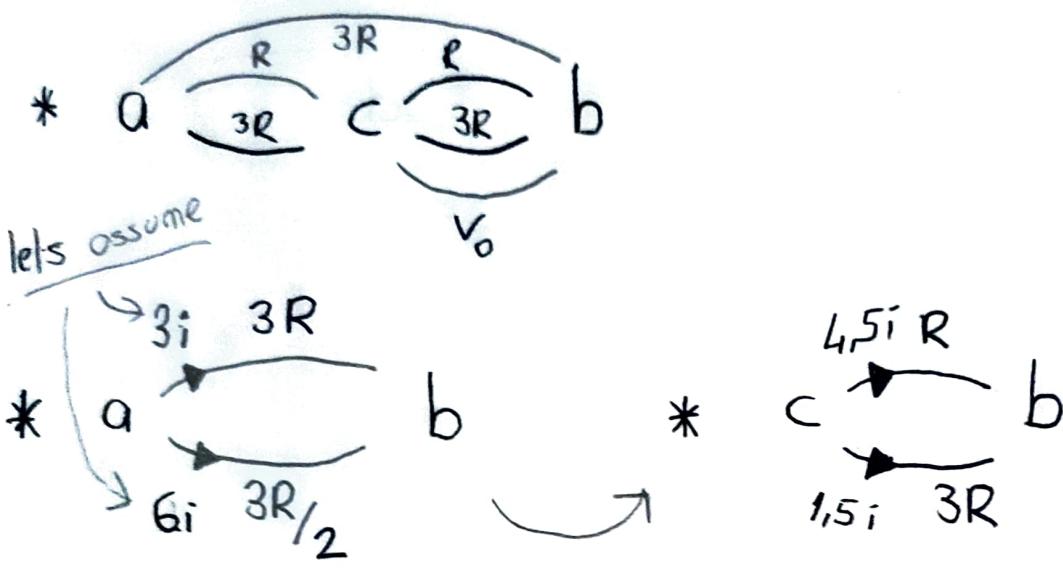

$$* V_i = 3i \cdot 3R = 9 \cdot i \cdot R$$


$$* V_o = 1.5i \cdot 3R = 4.5 \cdot i \cdot R$$

$$* \frac{V_o}{V_i} = \frac{4.5 \cdot i \cdot R}{9 \cdot i \cdot R} = \frac{1}{2} //$$

Circuit of question 3.67


To see if $V_0/V_1 = 1/2$ true when $R_L = R$
i gave 100 V to the system. And read 50V
from the voltmeter.

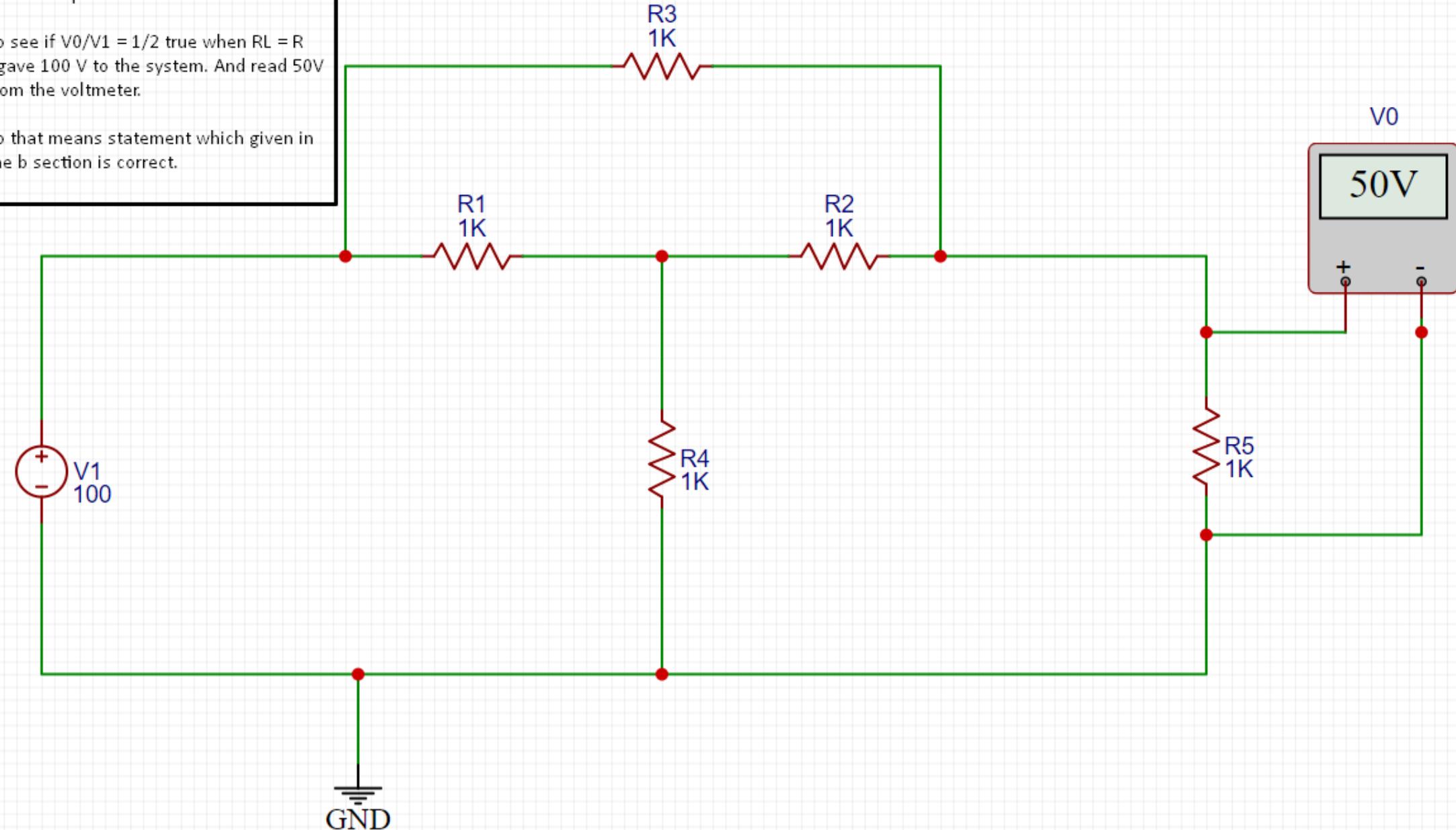So that means statement which given in
the b section is correct.





GEEK DAY

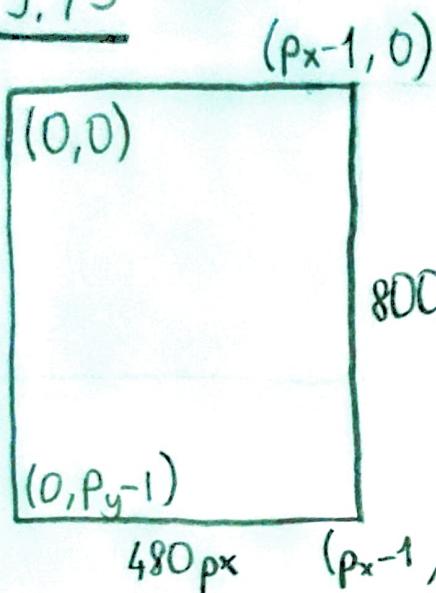• 3.73

$$a) \alpha = \frac{V_x}{V_s} , \beta = \frac{V_y}{V_s}$$

$$* V_s = 5V$$

$$V_x = 1V$$

$$V_y = 3,75V$$

$$* \alpha = \frac{1V}{5V} = \frac{1}{5}$$


$$\beta = \frac{3,75V}{5V} = 0,75$$


$$b) x = (1 - \alpha) p_x$$

$$y = (1 - \beta) p_y$$


$$* x = (1 - 0,2) \cdot 480 = \frac{8}{10} \cdot 480 = 384 //$$
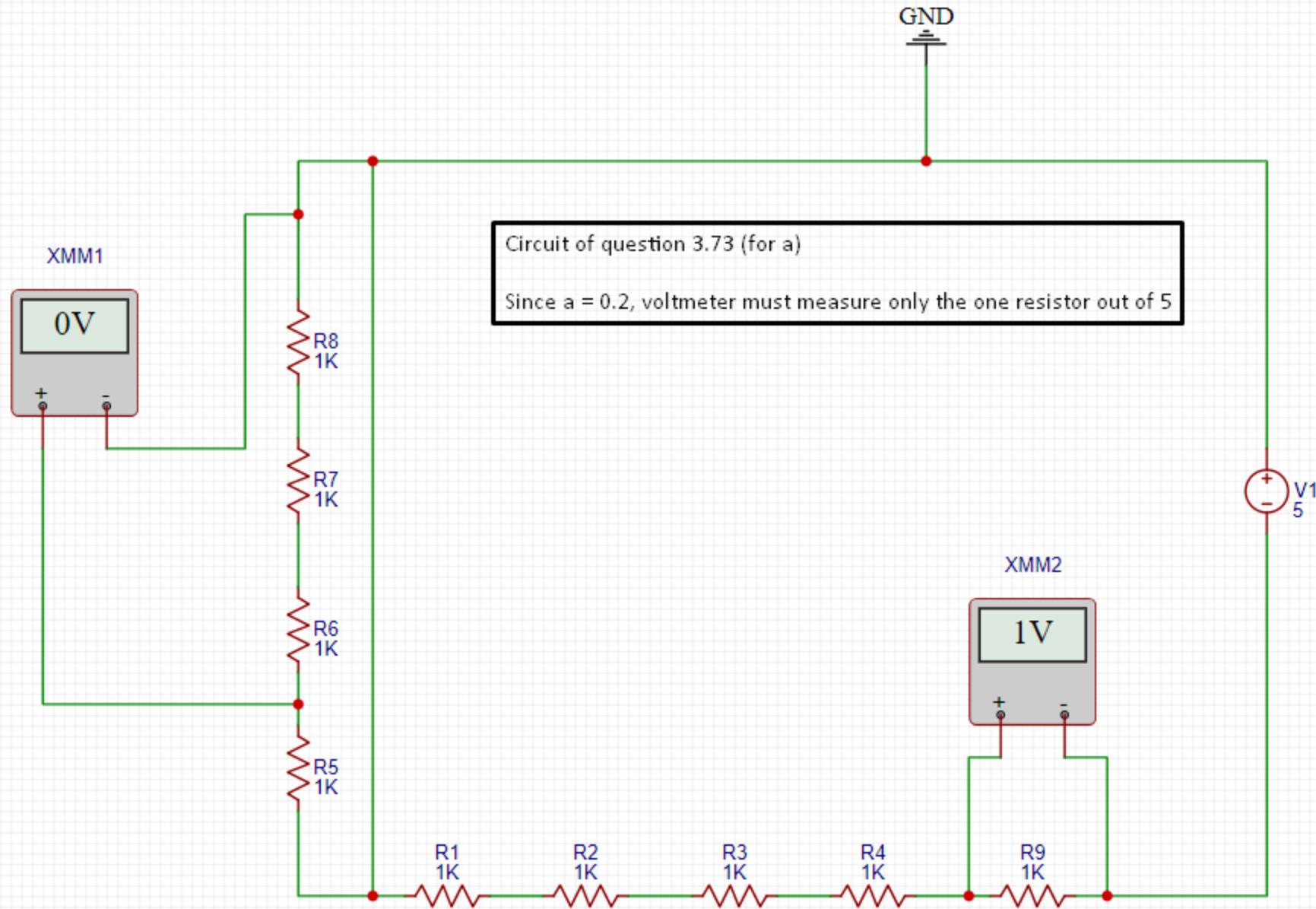
$$* y = (1 - 0,75) \cdot 800 = \frac{1}{4} \cdot 800 = 200 //$$



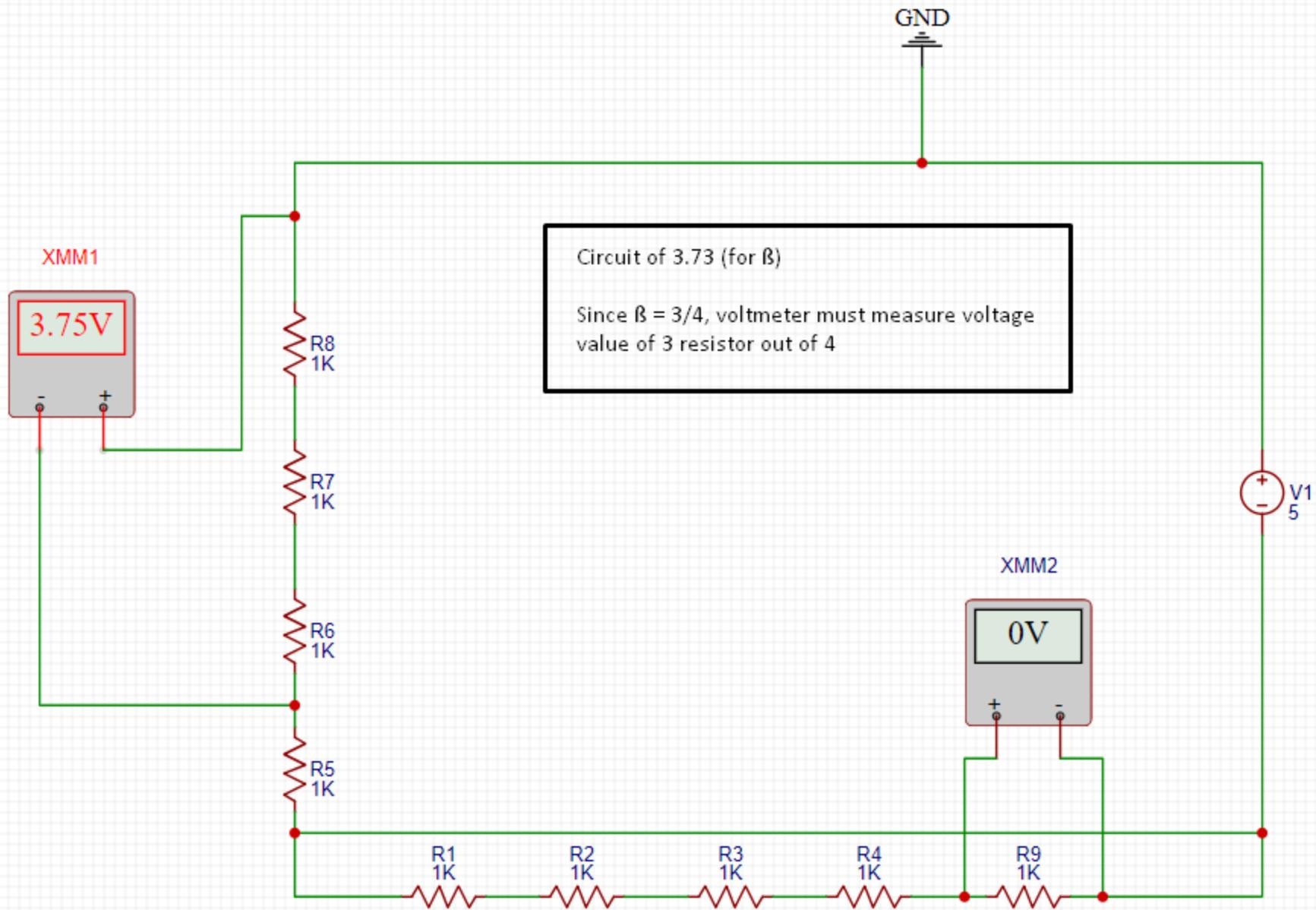

• 3.74

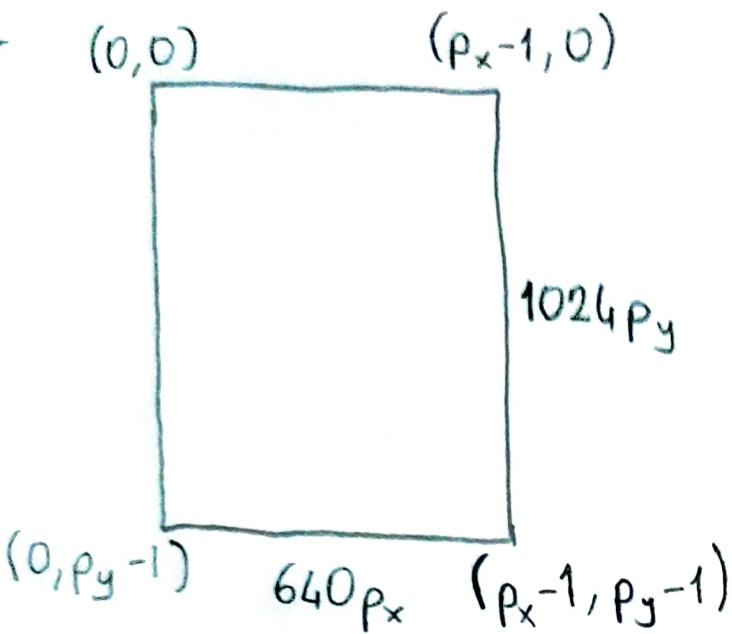

$$\left. \begin{array}{l} * V_s = 8V \\ x = 480 \\ y = 192 \end{array} \right\} \text{known values}$$

$$p_x = 640$$

$$p_y = 1024$$

$$* x = (1-a) \cdot p_x$$

$$* a = \frac{V_x}{V_s}$$

$$* 480 = (1-a) \cdot 640$$

$$* (1-a) = 0,75$$

$$* a = 0,25,$$

$$* \frac{1}{4} = \frac{V_x}{8}$$

$$* \boxed{V_x = 2V}$$

$$* y = (1-\beta) \cdot p_y$$

$$* \beta = \frac{V_y}{V_s}$$

$$* 192 = (1-\beta) \cdot 1024$$

$$* \frac{8125}{10000} = \frac{V_y}{8}$$

$$* \beta = 0,8125$$

$$* \boxed{V_y = 6,5V}$$

